

$$\text{Node 1: } \frac{v_1 - 20}{2} + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0 \quad (1)$$

$$\text{Node 2: } \frac{v_2}{10} + \frac{v_2 - 8i_\phi}{2 \cdot 5} + \frac{v_2 - v_1}{5} = 0 \quad (2)$$


$$\text{We have } i_\phi = \frac{v_2 - v_1}{5}$$

$$8i_\phi = 8 \left(\frac{v_1 - v_2}{5} \right) = \frac{8v_1 - 8v_2}{5}$$

$$\text{Node 2: } \frac{v_2}{10} + \frac{v_2 - v_1}{5} + \frac{13v_2 - 8v_1}{2} = 0$$

$$(1)(2) \left\{ \begin{array}{l} v_1 \left(\frac{1}{2} + \frac{1}{20} + \frac{1}{5} \right) + v_2 \left(-\frac{1}{5} \right) = 10 \\ v_1 \left(-\frac{1}{5} - \frac{8}{2} \right) + v_2 \left(\frac{1}{5} + \frac{13}{2} \right) = 0 \end{array} \right.$$
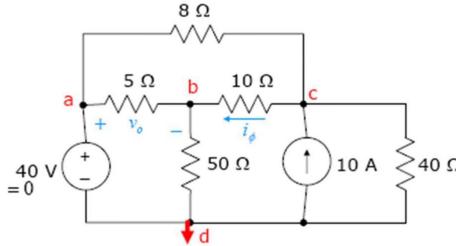
$$\left\{ \begin{array}{l} v_1 = 16 \\ v_2 = 10 \end{array} \right. \Rightarrow i_\phi = \frac{16 - 10}{5} = 1.2 \text{ A}$$



$$V_a = 40 \text{ V}$$

$$\text{Node B: } \frac{V_B - 40}{5} + \frac{V_B}{50} + \frac{V_B - V_C}{10} = 0 \quad (1)$$


$$\text{Node C: } \frac{V_C - 40}{8} + \frac{V_C - V_B}{10} + \frac{V_C}{40} = 10 \quad (2)$$

$$\left\{ \begin{array}{l} V_B \left(\frac{1}{5} + \frac{1}{50} + \frac{1}{10} \right) + V_C \left(-\frac{1}{10} \right) = 8 \end{array} \right.$$

$$\left. \begin{array}{l} V_B \left(-\frac{1}{10} \right) + V_C \left(\frac{1}{8} + \frac{1}{10} + \frac{1}{40} \right) = 15 \end{array} \right.$$

$$\Rightarrow \left\{ \begin{array}{l} V_B = 50 \text{ V} \\ V_C = 80 \text{ V} \end{array} \right. \quad i_o = \frac{40 - V_B}{5} = \frac{40 - 50}{5} = -2 \text{ V}$$
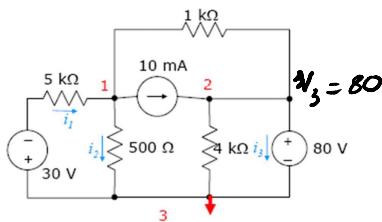
$$i_o = \frac{V_C - V_B}{10} = \frac{80 - 50}{10} = 3 \text{ A}$$




$$\text{Node 1: } \frac{V_1 + 30}{5000} + \frac{V_1 - 80}{1000} + \frac{V_1}{500} + 10 \times 10^{-3} = 0$$

$$\Rightarrow V_1 = 20 \text{ V}$$

$$i_1 = \frac{30 - V_1}{5000} = 0.002 \text{ A}$$

$$i_2 = \frac{V_1 - 0}{500} = \frac{20}{500} = 0.04 \text{ A}$$
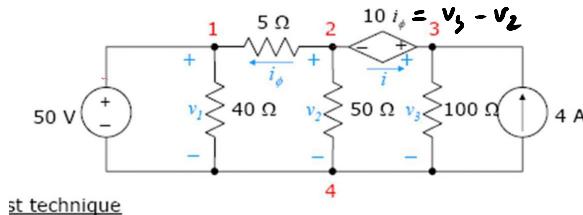
$$i_3 = \frac{80 - 0}{4000} = 0.02 \text{ A}$$



$$\dot{V} = \frac{V}{R}$$

$$\Rightarrow V = iR$$

$$v_1 = 50V$$


$$\text{Supernode at (2)(3)}: \frac{v_2 - 50}{5} + \frac{v_2}{50} + \frac{v_3}{100} = 14 \quad (4)$$

$$i_\phi = \frac{v_2 - 50}{5} \Rightarrow 10i_\phi = \frac{10v_2 - 500}{5} = 2v_2 - 100$$

$$v_3 = v_2 + 10i_\phi \Leftrightarrow v_2 - v_3 + 2v_2 - 100 \Leftrightarrow 3v_2 - v_3 = 100$$

$$\begin{cases} v_2 \left(\frac{1}{5} + \frac{1}{50} \right) + v_3 \left(\frac{1}{100} \right) = 14 \\ 3v_2 - v_3 = 100 \end{cases}$$
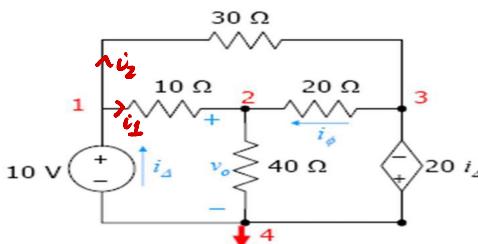
$$\Rightarrow \begin{cases} v_2 = 60 & i_\phi = \frac{60 - 50}{5} = 2A \\ v_3 = 80 & \dot{V} = \dot{v}_2 - \dot{v}_3 = \end{cases}$$



$$V_L = 10 \text{ V}$$

$$\text{Node 2: } \frac{V_2}{40} + \frac{V_2 - 10}{10} + \frac{V_2 + 20i_\Delta}{20} \quad (1)$$

$$i_\Delta = i_1 + i_2 = \frac{10 - V_2}{10} + \frac{10 + 20i_\Delta}{30} \quad (2)$$

$$\begin{cases} V_2 \left(\frac{1}{40} + \frac{1}{10} + \frac{1}{20} \right) + i_\Delta \left(\frac{20}{20} \right) = 1 \\ V_2 \left(-\frac{1}{10} \right) + i_\Delta \left(\frac{20}{30} \right) = -\frac{4}{3} \end{cases}$$

$$\begin{cases} V_2 = \\ i_\Delta = \end{cases}$$

$$\text{Node 1: } \frac{v_A - 15}{2} + \frac{v_A}{10} + \frac{v_A - v_B}{6} = 0$$

$$\Leftrightarrow v_A \left(\frac{1}{2} + \frac{1}{10} + \frac{1}{6} \right) + v_B \left(-\frac{1}{6} \right) = \frac{15}{2}$$

$$\text{Node 2: } \frac{v_B}{10} + \frac{v_B - v_A}{6} + \frac{v_B - 3i_a}{2} = 0$$

$$3i_a = 3 \times \frac{(v_A - v_B)}{6} = \frac{v_A - v_B}{2}$$

$$\frac{v_B}{10} + \frac{v_B - v_A}{6} + \frac{3v_B - v_A}{4}$$

$$\Leftrightarrow v_A \left(\frac{-1}{6} - \frac{1}{4} \right) + v_B \left(\frac{1}{10} + \frac{1}{6} + \frac{3}{4} \right) = 0$$

$$\Rightarrow \begin{cases} v_A = \frac{1525}{142} \\ v_B = \frac{625}{142} \end{cases} \quad i_a = \frac{75}{71}$$

$$P_{6\text{W}} = 6.6951 \approx 6.70$$

$$\bullet \Rightarrow \frac{v_B - \frac{v_A - v_B}{2}}{2} = \frac{\frac{2v_B - v_A + v_B}{2}}{2} = \frac{3v_B - v_A}{4}$$

Use the node-voltage method to find the v_A , v_B , i_A , $P_{6\Omega}$, $P_{10\Omega(\text{left})}$, $P_{10\Omega(\text{right})}$ in the circuit shown in Fig. 7 and fill in the blanks
(Round your answer to 2 decimal places).


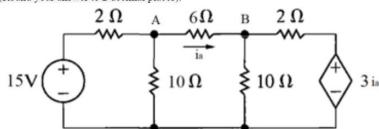


Fig. 7.


$v_A = 10.74$	V
$v_B = 4.40$	V
$i_A = 1.05$	A
$P_{6\Omega} = 6.7$	W
$P_{10\Omega(\text{left})} = 11.53$	W
$P_{10\Omega(\text{right})} = 1.93$	W

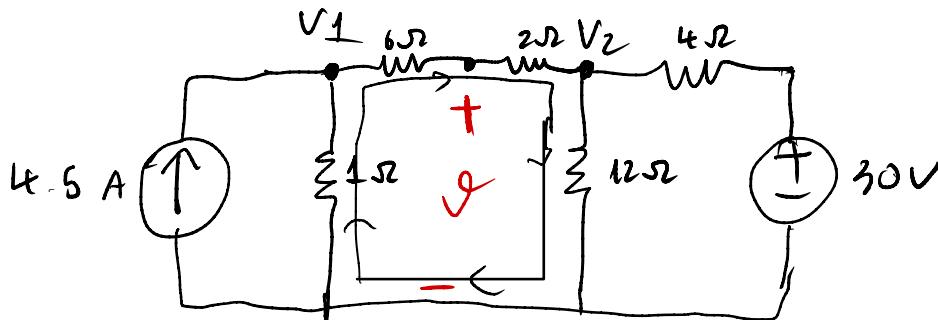

$$\text{Nod1: } \frac{v_1 - v_2}{8} + v_1 = 4.5$$

$$\text{Node 2: } \frac{v_2 - v_1}{8} + \frac{v_2 - 30}{4} + \frac{v_2}{12} = 0$$

$$\begin{cases} v_1 \left(\frac{1}{8} + 1 \right) + v_2 \left(-\frac{1}{8} \right) = 4.5 \\ v_1 \left(-\frac{1}{8} \right) + v_2 \left(\frac{1}{8} + \frac{1}{4} + \frac{1}{12} \right) = 7.5 \end{cases} \Rightarrow \begin{cases} v_1 = 6 \\ v_2 = 18 \end{cases}$$

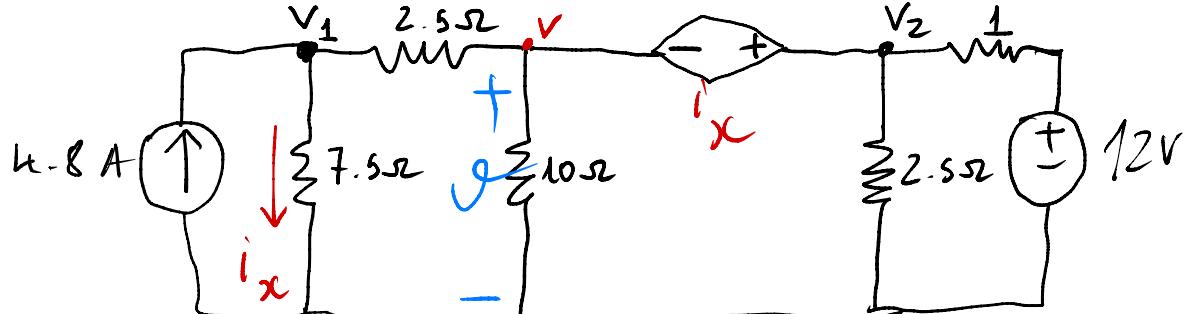


Find V : $i_x = V_2 - V = \frac{V_1}{7.5}$ (1)

Node 1: $\frac{V_1}{7.5} + \frac{V_1 - V}{2.5} - 4.8 = 0$ (2)

Super node $(V)(V_2)$: $\frac{V}{10} + \frac{V - V_1}{2.5} + \frac{V_2}{2.5} + \frac{V_2 - 12}{1} = 0$

$$\begin{cases} V_1(-1) + 7.5V_2 - 7.5V = 0 \\ V_1\left(\frac{1}{7.5} + \frac{1}{2.5}\right) + V\left(-\frac{1}{2.5}\right) = 4.8 \\ V_1\left(-\frac{1}{2.5}\right) + V_2\left(\frac{1}{2.5} + \frac{1}{10}\right) + V\left(\frac{1}{10} + \frac{1}{2.5}\right) = 12 \end{cases} \Rightarrow \begin{cases} V_1 = 15 \\ V_2 = 10 \\ V = 8 \end{cases}$$

$\Rightarrow i_x = 2 \text{ A}$ $\vartheta = ?$

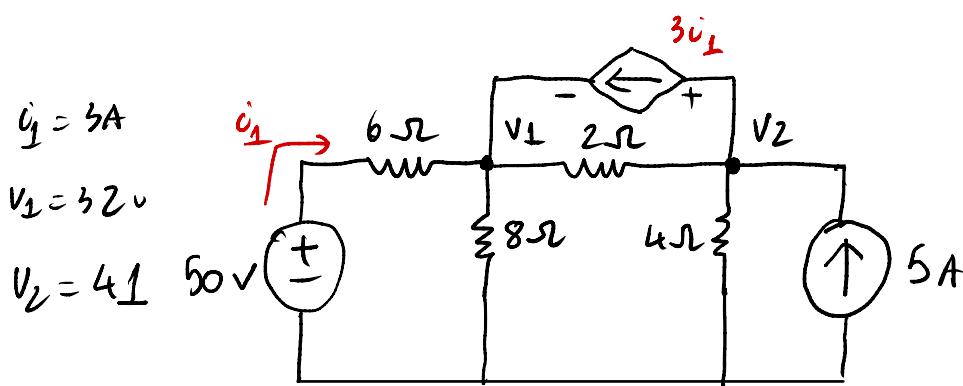

Node 1:

$$\frac{V_1 - 50}{6} + \frac{V_1}{8} + \frac{V_1 - V_2}{2} - 3i_1 = 0 \quad (1)$$

Node 2:

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + 3i_1 - 5 = 0 \quad (2)$$

$$i_1 = \frac{50 - V_1}{6}; \quad 3i_1 = V_2 - V_1$$