

$$\omega = 1000$$

$$Z_1 = j100 \times 10^3$$

$$Z_3 = 10^4 + j100 \times 10^3$$

$$\text{loop 1: } I_1 (j100 \times 10^3 + 22 \times 10^3) + I_2 (-22 \times 10^3) = 5 \quad \text{E}$$

$$\text{loop 2: } 3 \angle -46 + I_2 (10^4 + j100 \times 10^3 + 22 \times 10^3) +$$

$$\Rightarrow -I_2 (10^4 + j100 \times 10^3 + 22 \times 10^3) - I_1 (22 \times 10^3) \quad \text{B}$$

$$\Rightarrow I_1 (-22 \times 10^3) + I_2 (-32 \times 10^3 - j100 \times 10^3) \quad \text{C}$$

$$D = D \quad D_x = E \quad D_y = F \quad \text{D} \quad = 3 \angle -46 \quad \text{F}$$

$$x = \frac{D_x}{D} = 4 \cdot 10^4 \times 10^{-5} \angle -177^\circ$$

$$y = \frac{D_y}{D} = 0.178 \angle -75.61^\circ$$

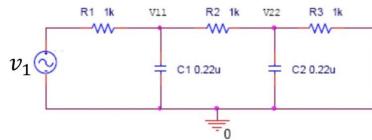


Figure 2. AC circuit used in the Node -voltage Analysis

$$1 \leftarrow: N_{10} - \theta_{en} - \theta_0' \\ 1 \quad 0 \quad \times 10^2$$

$$10 \leftarrow: N_{00} - \theta_{en} - C_{en} \\ 1 \quad 0 \quad \times 10^3$$

$$22 \leftarrow: \theta_0' - \theta_0' - C_{en} \\ 2 \quad 2 \quad \times 10^3$$

Math  $\rightarrow$  Operation



Subtract

$$v_1 - v_2$$



Red line

$$v_{2,1}$$



Find  $\alpha \angle 0^\circ$

$$\phi_{22} - \phi_{12} \geq 0$$

Loop 1:

$$-5 \angle 0 + I_1 (-j 15915.5) + 22 \times 10^3 (I_1 - I_2) = 0$$

$$\text{C) } I_1 (22 \times 10^3 - j 15915.5) + I_2 (-22 \times 10^3) = 5 \text{ E}$$

Loop 2

$$22 \times 10^3 (I_2 - I_1) + I_2 (10^4 - j 15915.5) + 3 \angle -46 = 0$$

$$\text{C) } I_1 (-22 \times 10^3) + I_2 (32 \times 10^3 - j 15915.5) = j 2.160 - 2.084 \text{ F}$$

$$\Delta = AD - BC = M$$

$$Rx = BF - ED \Rightarrow x = \frac{Rx}{\Delta} = 1.323 \times 10^{-4} \angle -50.32$$

$$Dy = AF - EC \Rightarrow y = \frac{Dy}{\Delta} = 1.653 \times 10^{-4} \angle 158.303$$

Loop 1:  $I_1 = 1.37871 \times 10^{-4} \angle -103.488^\circ$

$$I_2 = 1.4801 \times 10^{-4} \angle -48.4726^\circ$$

Web:  $I_1 = 1.37857 \times 10^{-4} \angle 76.53^\circ$

$$I_2 = 1.48070 \times 10^{-4} \angle 131.53^\circ$$

$$V_{Z_1} = I_1 Z_{C_1} = 2.19 \angle -13.47^\circ$$

$$V_{Z_2} =$$

$$V_R = \varphi_{in} + \frac{R}{Z_L + R}$$

$$\Leftrightarrow Z_L + R = \frac{\varphi_{in}}{vR} \times R$$

$$\Leftrightarrow 2 \pi f L = R \left( \frac{\varphi_{in}}{vR} - 1 \right)$$

$$\Rightarrow L = \frac{R \left( \frac{\varphi_{in}}{vR} - 1 \right)}{2 \pi f}$$

$$z_c = \frac{1}{0.01 \times 10^{-6} \times 2\pi \times 10000j} = -j15915.49431$$



loop 1:

$$I_1(z_c + 22000) + I_2(-22000) = 5 \angle 0$$

loop 2:

$$I_1(-22000) + I_2(22000 + 10000 + z_c) = -3 \angle 46^\circ$$

$$3 \angle -46^\circ = 2.084 - j2.16$$

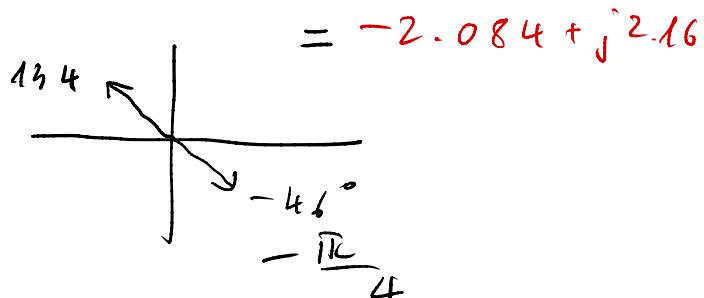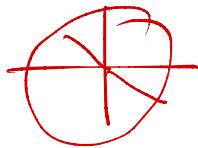

$$z_1 = 2.13 \angle 166.512^\circ$$

$$z_2 = -a - j b$$

At  $50\text{Hz}$   $I_1 = 1.37871 \times 10^{-4} \angle -103.48^\circ$

$$I_2 = 1.4801 \times 10^{-4} \angle -48.4726^\circ$$

Web:  $I_1 = 1.37857 \times 10^{-4} \angle 76.53^\circ$

$$I_2 = 1.48070 \times 10^{-4} \angle 131.53^\circ$$

$$V_{z_2} = 2.19 \angle -13.47^\circ - a + j b$$

$$Z_C = -j723.43$$

$$V_1 = 3.772 \angle 60.05^\circ$$

$$\text{Node 1: } V_2 = 1.55 \angle 25.40^\circ$$

$$\frac{V_1 - 5}{1000} + \frac{V_1 - V_C}{Z_C} + \frac{V_1 - V_2}{1000} = 0$$

$$\Rightarrow V_1 \left( \frac{100}{723.43} j \right) + V_2 \left( -\frac{100}{723.43} j - \frac{1}{1000} \right) = \frac{E_1}{Z_C}$$

Node 2:

$$\frac{V_2 - V_1}{1000} + \frac{V_2}{Z_C} + \frac{V_2}{1000} = 0$$

$$\Rightarrow V_1 \left( -\frac{1}{1000} \right) + V_2 \left( \frac{1}{1000} + \frac{1}{1000} + \frac{100}{723.43} j \right) = 0$$
$$\Rightarrow V_1 \left( -\frac{1}{1000} \right) + V_2 \left( \frac{1}{500} + \frac{100}{723.43} j \right) = 0$$

$$D = 3.22 \times 10^{-6} \angle 154.597^\circ = z$$

$$D_x = 1.22 \times 10^{-5} \angle 34.65^\circ = x$$

$$D_y = 5 \times 10^{-6} \angle 180^\circ = y$$

$$\Rightarrow V_1 = \frac{Dx}{\Theta} = 3.77 \angle -119.95^\circ$$

$$V_2 = \frac{Dy}{\Theta} = 1.55 \angle 25.40^\circ$$

$$I_{c_1} = \frac{3.772 \angle 60.05^\circ}{5.21 \times 10^{-3}} = 5.21 \times 10^{-3} \angle 150.05^\circ$$

$$5.21 \times 10^{-3} \angle -29.95^\circ$$

$$V_1 = I_{c_1} \cdot Z_{c_1} =$$

