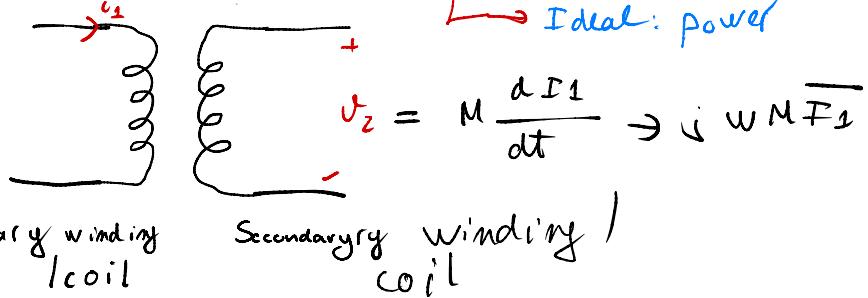





Transformer



Use to match impedance  $\rightarrow$  Max power transform


Linear Transformer :

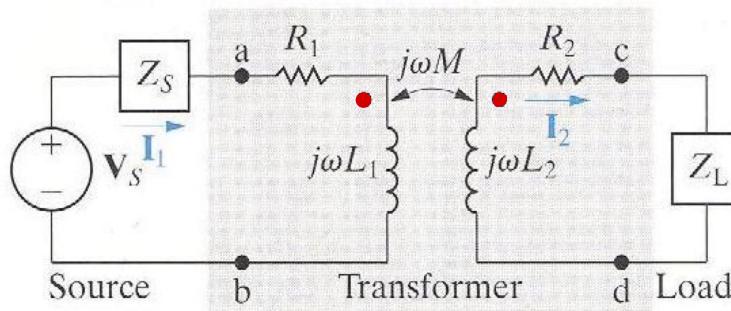

$$\bar{Z}_{ab} = \frac{\bar{V}_{Ab}}{\bar{I}_1} = \frac{\bar{V}_S - \bar{F}_1 \bar{z}_s}{\bar{I}_1}$$

$$\bar{z}_{Ab} = R_1 + j\omega L_1 + z_R$$

$$z_R = \frac{\omega^2 N^2}{R_2 + j\omega L_2 + z_L} = \frac{\omega^2 N^2}{|z_{22}|^2} z_{22}$$

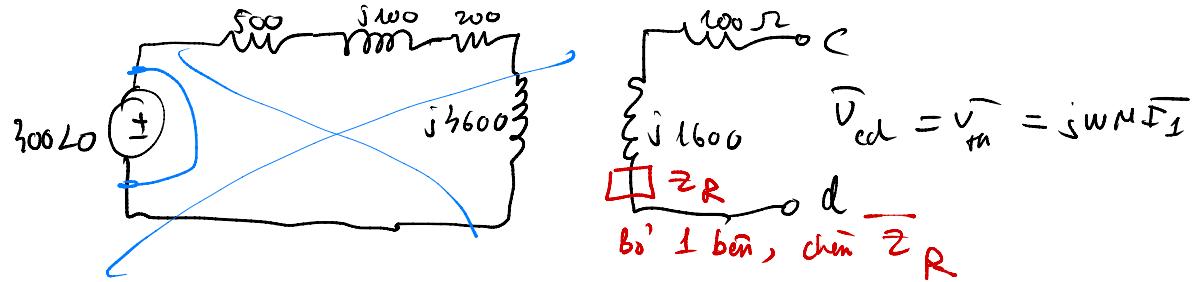


$$\underline{I}_1 = \frac{500 \angle 0^\circ}{500 + j1600 + 200 + j3600}$$

$$\underline{\underline{Z}}_{th} = \underline{\underline{Z}}_{cd} = 100 + j1600 + \frac{(w_m)^2}{|Z_{11}|^2} \underline{\underline{Z}}_{11}$$

$$\underline{\underline{Z}}_{in} = 500 + 200 + j1600 + j3600 = 700 + j3700$$

Ideal Transformer:

Question 1:

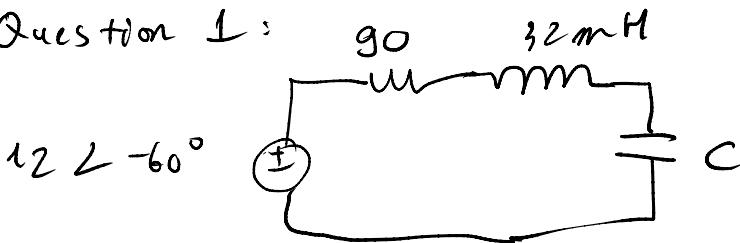

Find  $C$  to obtain  $I = |I| \angle -105^\circ$

$$|I| = \frac{12 \angle -60^\circ}{|Z| \angle \theta_Z} \Rightarrow |I| \angle -60^\circ - \theta_Z$$

$$a) -60^\circ - \theta_Z = -105^\circ \Rightarrow \theta_Z = 45^\circ$$


$$Z = 9\Omega + j\omega L + \frac{1}{j\omega C} = 9\Omega + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\Rightarrow \theta_Z = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{9\Omega}\right)$$

$$\Rightarrow \tan(45^\circ) = 1 = \frac{\omega L - \frac{1}{\omega C}}{9\Omega} \Rightarrow C = 2.86 \mu F$$

$$b) |I| = \frac{12}{\sqrt{9\Omega^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = 0.982(A)$$

Question 2:

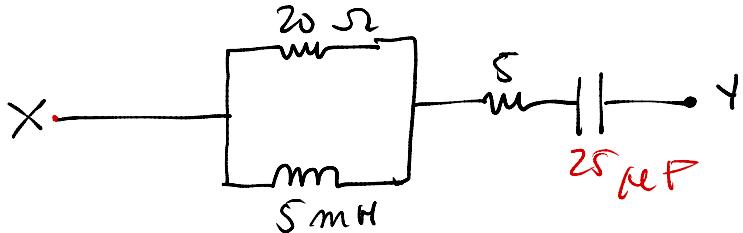

- a)  $\omega = 2000 \text{ rad/s}$ , compute  $\bar{Z}_{xy}$
- b) At what finite  $f$ , does the impedance of  $\bar{Z}_{xy}$  becomes purely positive?
- c)  $\bar{Z}_{xy} = ?$  if  $w$  found in b

$$a) Z_L = \frac{20 \times j\omega}{20 + j\omega} = 4 + j8$$

$$Z_C = 5 - j20$$


$$Z_{xy} = 9 - j12$$

$$b) \frac{20 \times j\omega L}{20 + j\omega L} \times \frac{20 - j\omega L}{20 - j\omega L} + 5 - \frac{1}{\omega C}$$

$$\dots = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j 400\omega L}{400 + \omega^2 L^2} + 5 - j \frac{10^6}{25\omega}$$

c)

$$10 + 5 = 15$$

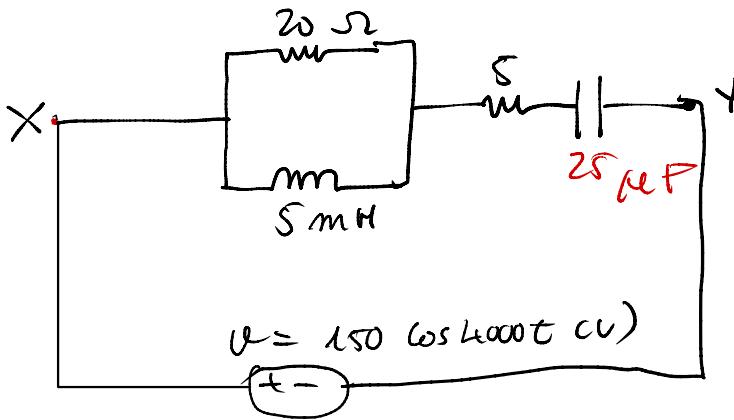


What is the max amplitude of the current in the  $5 \text{ mH}$  inductor?

$$I = \frac{150 \angle 0}{15} = 10 \text{ A}$$

$$I_v = \frac{10 \times 10}{20 + j\omega L} = 7.07 \angle -45^\circ$$

Question 4:

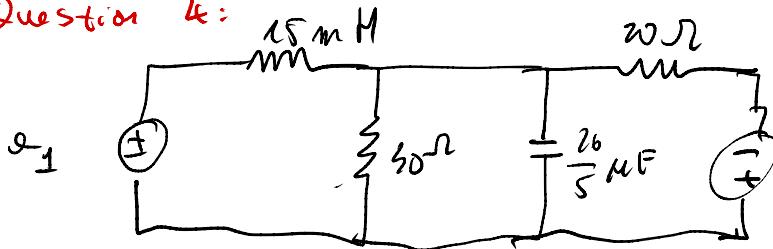

$$v_1 = 240 \cos(4000t + 53.13^\circ)$$


$$v_2 = 96 \sin(4000t) = 96 \angle -90^\circ$$

$$Z_L = j60 \quad \rightarrow I_1 = \frac{240 \angle 53.13^\circ}{j60} = 4.2 - j2.4$$

$$Z_C = -j60$$

$$\Rightarrow I_2 = \frac{96 \angle -90^\circ}{20} = -j4.8$$

$$I_1 - I_2 = 5.2 + j2.4$$

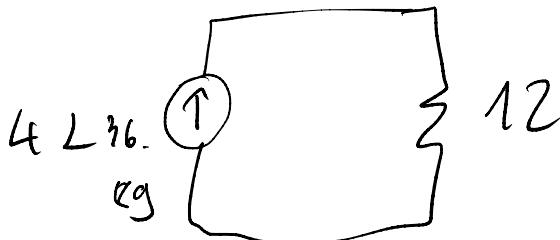

$$V_0 = 48 \angle 36.87^\circ$$