



















Principle of E

✓

l



F, H, C

F, H, C

F

v

live








$$\dot{q} = \frac{dq}{dt}$$

$$q = \int_0^t idt = \int_0^t 5dx = 5t$$

$$q = 5 \times 10 = 50C$$



$$q(t) = \int_0^t i(x) dx$$

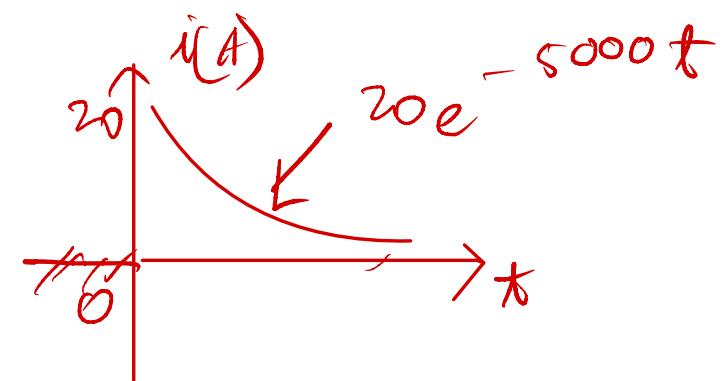





$$\frac{d}{dx} = 0 \Rightarrow i_{\max}$$



$\rho > 0$  { absorbed  
dissipated  
received

$\rho < 0$  { generated  
extracted




current enter

leave



if not  $\rho = -\sigma i$

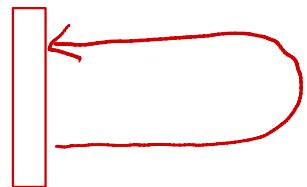



$$P_B = -\vartheta i = -12 \times 30 = 360 \text{ W}$$

$$P_A = +\vartheta i = 360 \text{ W}$$








af

nguồn phèn thuộc

$$J_s = 2V_x$$

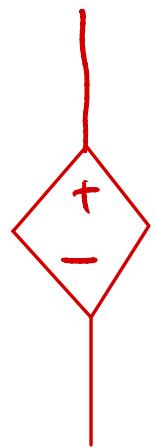

$\vdash_{\text{NOV}}$

$\vdash_{\text{SA}}$

does not violate anything

by theorem

điển áp cho cực tính

]]  
[[  
[]  
]]

current

$$G = \frac{1}{R} (S, \mathcal{U})$$


$$f = i R$$

$$i \nearrow$$

$$\begin{matrix} i \\ \nearrow \end{matrix}$$

$$\nearrow$$

$$\nwarrow$$

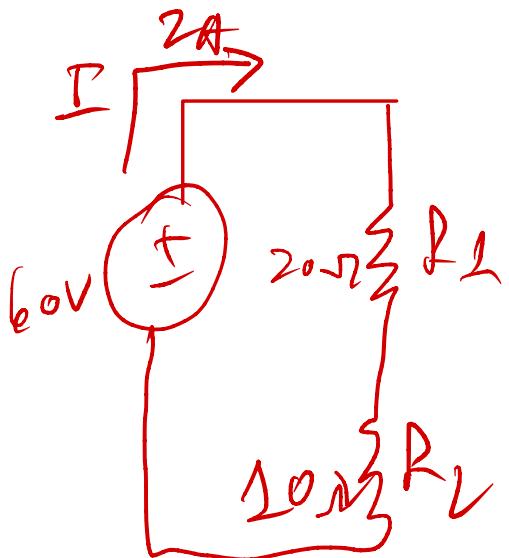

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$R_T = R_1 + R_2 = 20 + 10 = 30\Omega$$


$$I = \frac{V}{R_T} = \frac{60V}{30\Omega} = 2A$$

$$P_1 = I^2 R_1 = 2^2 \cdot 20 = 80W$$

$$P_2 = I^2 R_2 = 2^2 \cdot 10 = 40W$$

$$P = VI = 60(2A) = 120W$$

*correct*

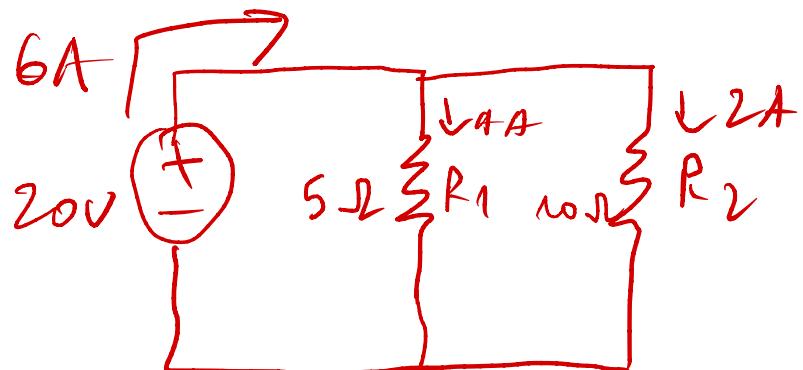

$$V = IR$$

$$I_1 = \frac{V}{R_1} = \frac{20}{5\Omega} = 4A$$

$$I_2 = \frac{V}{R_2} = \frac{20}{10\Omega} = 2A$$

$$\left. \begin{array}{l} I_1 = 4A \\ I_2 = 2A \end{array} \right\} 6A$$

$$P_1 = I_1^2 R = 4^2 (5) = 80W \quad P_2 = I_2^2 R = 2^2 (10) = 40W$$

$$P_B = VI = (20V)(6A) = 120W \text{ (correct)}$$

$\text{I} \nearrow$

$v = i R$

$i = g - g$

$\nearrow$

$g = i R$

$\nearrow$


$i \downarrow$

$\nwarrow$





Loop 3 close path

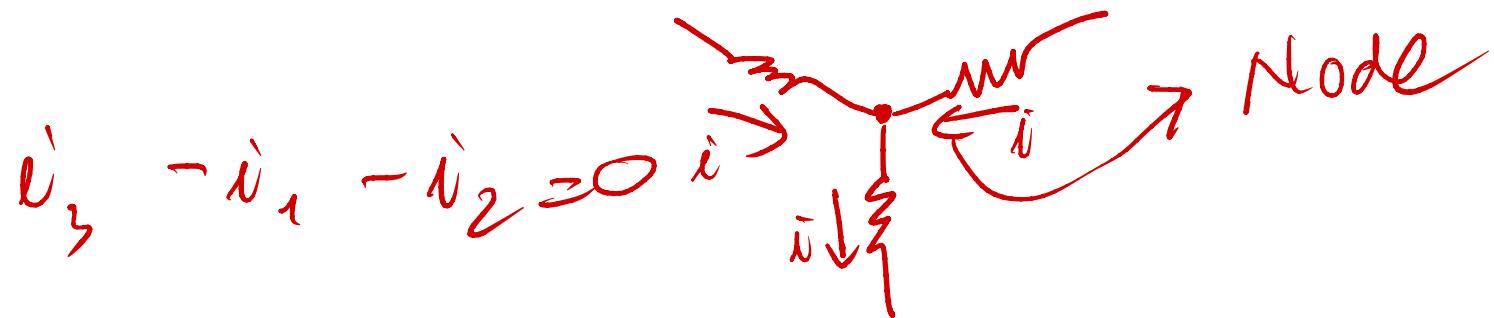

$$\sum_{n=1}^{\infty} i_n = 0$$

$$\sum_{n=1}^{\infty} v_n = 0$$




->


✓ +

<  
+


->

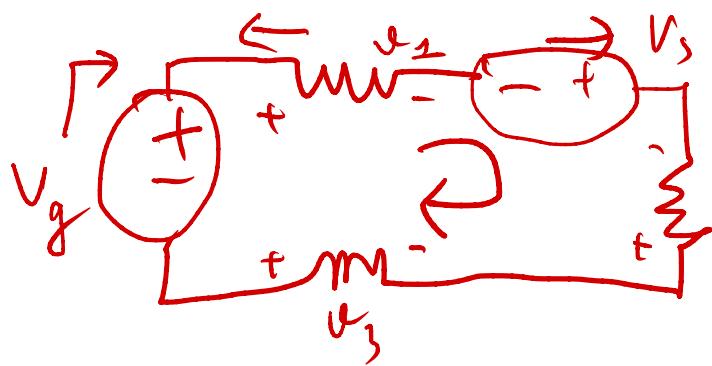

$$v_2 - v_g + v_1 - v_3 = i$$

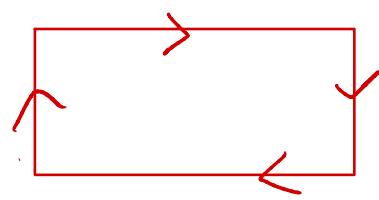



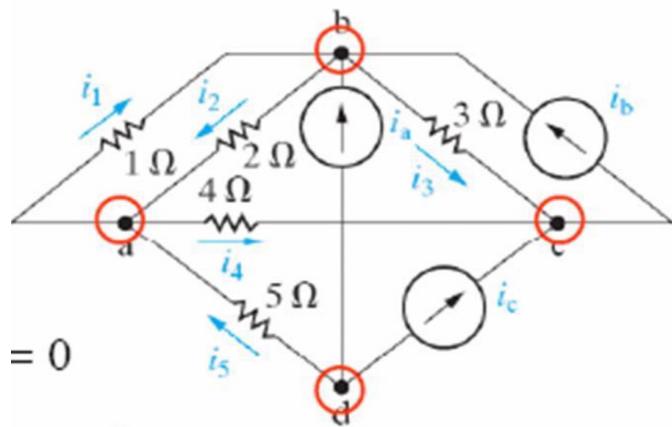

$$\text{Node A: } i_1 + i_4 - i_2 - i_5 = 0$$


$$\text{Node B: } i_3 + i_2 - i_1 - i_a - i_b = 0$$

$$\text{Node C: } i_b - i_3 - i_c - i_4 = 0$$


$$\text{Node D: } i_a + i_c + i_5 = 0$$



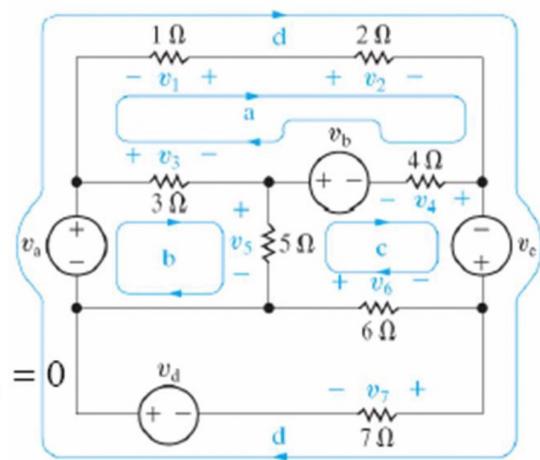- Apply KVL, positive sign and voltage drop.



Follow this loop:

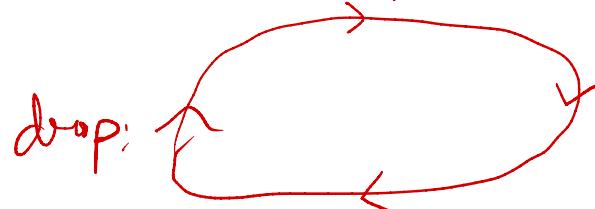

$$\text{Loop a: } v_2 - v_1 - v_3 + v_4 - v_5 = 0$$


$$\text{Loop b: } -v_a + v_3 + v_5 = 0$$

$$\text{Loop c: } v_b - v_4 - v_c - v_6 - v_7 = 0$$

$$\text{Loop d: } v_2 - v_1 - v_c + v_7 - v_d - v_a = 0$$



Resistors have to be  
dis'persed

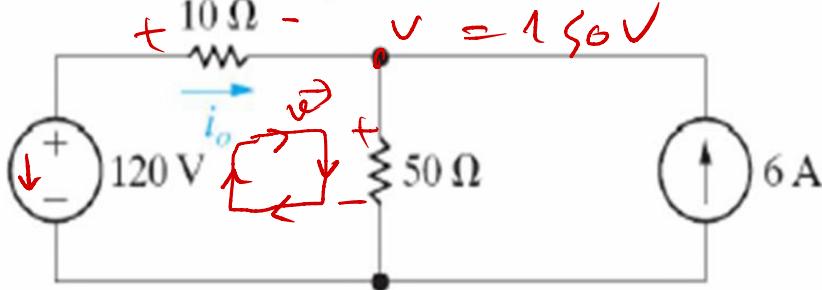

$$KCL: i_1 - i_0 - 6 = 0 \quad (1)$$

$$KVL: v_1 - v_0 - 120 = 0$$

$$\Rightarrow 50i_1 + 10i_0 - 120 = 0$$

$$(1)(2): \begin{cases} i_1 - i_0 = 6 \\ 50i_1 + 10i_0 = 120 \end{cases} \Rightarrow \begin{cases} i_1 = 3A \\ i_0 = -3A \end{cases}$$

• Node Voltage:  $\frac{v - 120}{10} - 6 + \frac{v}{50} = 0 \Rightarrow v = 150$

$$-i_0 = \frac{150 - 120}{10} \Rightarrow i_0 = -3A$$

$$i_1 = \frac{150}{50} = 3A$$

Power:

one source  $\Rightarrow P \propto$

AC




verify

$$P_{120V} =$$





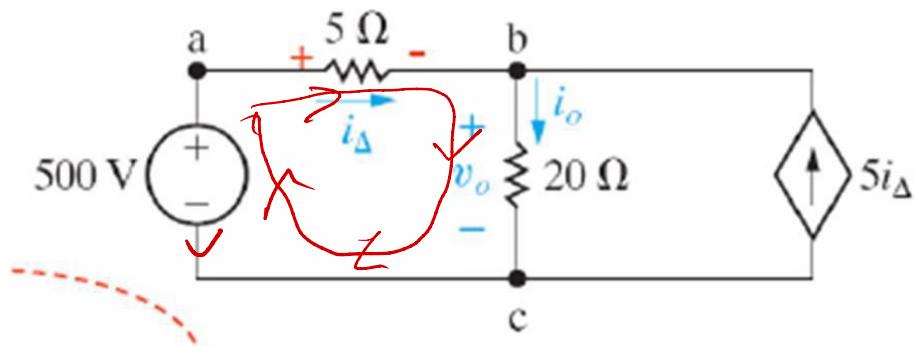

$$v = ir$$

$$i = \frac{v}{R}$$

KCL at b:  $i_o - i_\Delta - 5i_\Delta = 0$

$$\Rightarrow i_o = 6i_\Delta$$


KVL a,b,c:  $5i_\Delta + 20i_o - 500 = 0$

$$\Rightarrow 5i_\Delta + 20 \times 6i_\Delta = 500$$

$$\Rightarrow i_\Delta = 4 \text{ A}$$

$$i_o = 24 \text{ A}$$
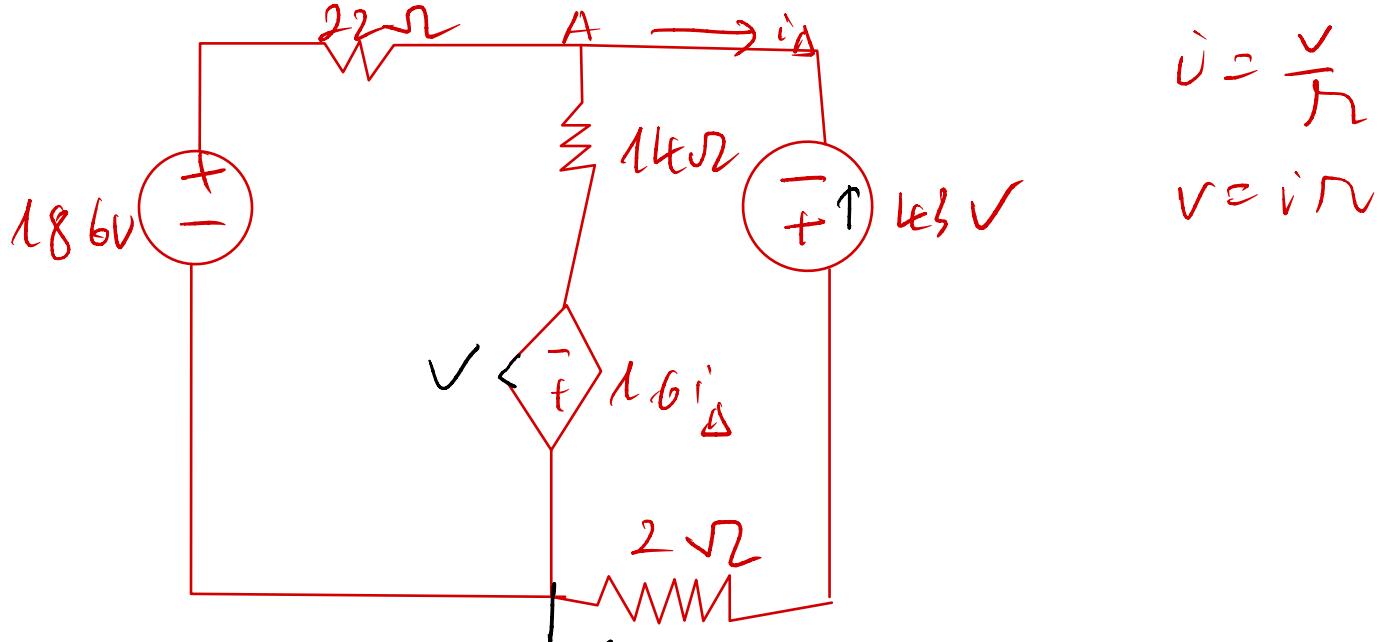
$$v_o = i_o \times 20 = 24 \times 20 = 480 \text{ V}$$



$$i = \frac{v}{R}$$

$$v = ir$$

Node Voltage at A:

$$\frac{v - 18.6}{22} + \frac{v - 1.6i_A}{14} + \frac{v - 4.3}{2\sqrt{2}} \quad (\star)$$


Constraint eq:  $i_A = \frac{v - 4.3}{2\sqrt{2}} = \boxed{\frac{v + 4.3}{2}}$

$$(\star) \frac{v - 18.6}{22} + \frac{v + \left(\frac{v + 4.3}{2}\right)^2}{14} + \frac{v + 4.3}{2\sqrt{2}} = 0$$

$$\Rightarrow v = -23.4$$



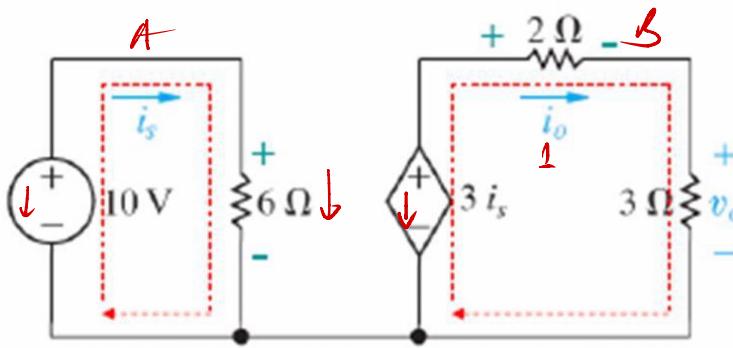Find  $P_{\text{dc's}}$  and  $P_{\text{delivered}}$



$$v = ir$$

$$v = \frac{v}{r}$$

$$P = i^2 r$$

$$P = \frac{v^2}{R}$$

$$\text{KVL path A: } 6i_s - 10 = 0 \Rightarrow i_s = \frac{5}{3} \text{ (A)}$$


$$\text{KVL path B: } (2+3)i_o - 3i_s = 0 \Rightarrow i_o = 1 \text{ (A)}$$

$$\text{Power dissipated: } P_{6\Omega} + P_{2\Omega} + P_{3\Omega} = \frac{5^2}{3} \cdot 6 + 1^2 \cdot 2 + 1^2 \cdot 3 = 21.67 \text{ W}$$

$$\begin{aligned} \text{Power delivered: } P_{10V} + P_{3i_s} &= 10i_s + i_o 3i_s = 10 \cdot \frac{5}{3} + 1 \times 3 \times \frac{5}{3} \\ &= 21.67 \text{ W} \end{aligned}$$

$$P = v^2 \cdot \frac{R}{R}$$



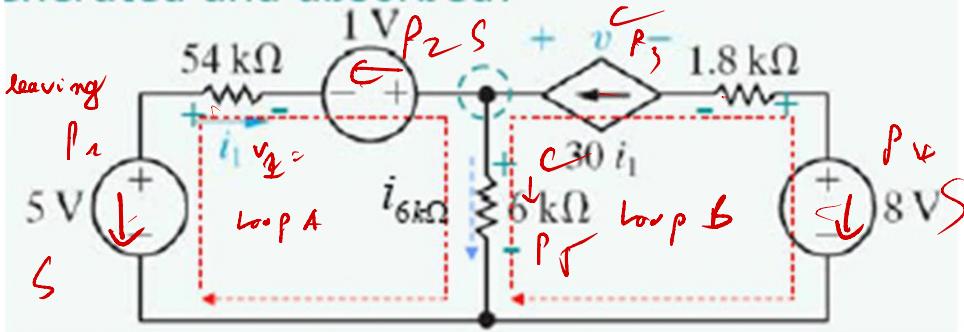

$$i = \frac{v}{R}$$

$$v = iR$$

$$P = i^2 R = \frac{v^2}{R}$$

$$P = iV$$

$$i_{6k\Omega} = 7.8 \times 10^{-4}$$

KCL:  $i_{6k\Omega} - i_1 - 30i_1 \Rightarrow i_{6k\Omega} = 31i_1$

KVL and Ohm's Law at loop A:  $51k\Omega v_1 - 1 + 6k\Omega i_{6k\Omega} - 5 = 0$

$$\Rightarrow 51k\Omega v_1 + 6k\Omega \cdot 31i_1 = 6 \Rightarrow v_1 = 2.53 \times 10^{-5} V$$

KVL and Ohm's Law at loop B:  $-30i_1 \times 1.8k\Omega + 8V - i_{6k\Omega} \times 6k\Omega + 8 = 0$

$$\Rightarrow -30 \times 2.5 \times 10^{-5} \times 1.8 \times 10^3 + 8 - 31 \times 2 \times 10^{-5} \times 6 \times 10^3 = 0$$

$$P_{54k\Omega} = v_1^2 R = 1.35W ; P_{5V} = 1 \times v_1 = 2.5 \times 10^{-5} W ; P_{6k\Omega} = 31i_1 \times 6000 = 3.60375 \times 10^{-3} W$$

$$P_{30i_1} = -(-2 \times 30i_1) = 1.5 \times 10^{-3} W ; P_{8V} = ?$$


$$P_{5V} = i_1 \times -5 = -1.25 \times 10^{-4} W ; P_{1.8k\Omega} = ?$$

EE <sub>2</sub>	Cals	Phy <sub>3</sub>
4	4	4
CNXHHR	Critical	Program
2	3	4

r

$$i_a = 4A \quad v_D = +2$$

Find  $v_g$ ,  $i_g$

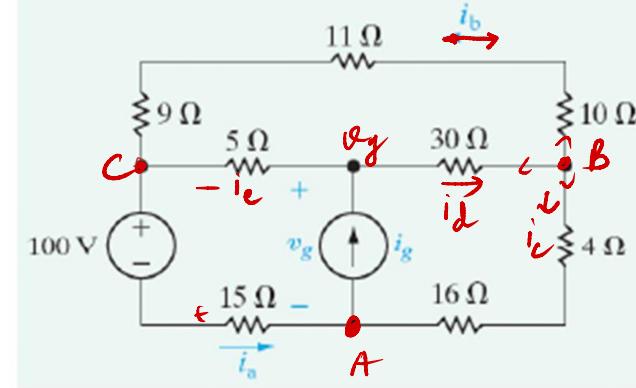

$$i = \frac{v}{r}$$

$$v = ir$$

$$P = i^2 r$$

$$P = vr$$

KVL at bottom left loop:

$$-5i_c + v_g - 15i_a - 100 = 0$$

$$\Rightarrow v_g = 190V$$

Ohm's Law :

KVL outside loop:  $v_{g2} + v_{11\Omega} + v_{10\Omega} + v_{4\Omega} + v_{16\Omega} - v_{15\Omega} - 100 = 0$

$$\Leftrightarrow 9 \times 2 + 11 \times 2 + 10 \times 2 + 4i_c + 16i_c - 15 \times 4 - 100 = 0$$

$$\Rightarrow i_c = 5A$$

KCL at node A:  $i_g - i_a - i_c = 0 \Rightarrow i_g = 5 + 4 = 9A$

KCL at node B:  $i_c - i_a - i_d \Rightarrow i_d = i_c - i_b = 5 - 2 = 3A$

KCL at node C:  $i_a - i_c + i_b \Rightarrow 4 - i_c + 2 \Rightarrow i_c = 6A$

$$P_{9\Omega} = 2^2 \times 9 = 36W, P_{11\Omega} = 2^2 \times 11 = 44W, P_{10\Omega} = 2^2 \times 10 = 40W, P_{4\Omega} = 5^2 \times 4 = 100W$$

$$P_{16\Omega} = 5^2 \times 16 = 400W, P_{15\Omega} = 4^2 \times 15\Omega = 240W, P_{5\Omega} = 6^2 \times 5 = 180W, P_{30\Omega} = 3^2 \times 30 = 270W$$

$$P_{i_g} = -(190)(9) = -1710W \quad P_{100V} = 10 \times 100 = 1000W$$

$$P_{\text{dissipated}} = 1310W \quad P_{\text{generated}} = 1310W$$

