

Q1 : Given a MUX which has X and Y as input signals

In case that T is selected, the control input $C = 1$


In case that X is selected, the control input $C = 0$

a) Create the truth table on the given MUX

b) Write an expression for Z in form of SOP

c) Simplify the expression in part (b) by using k-map

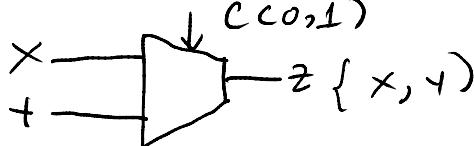d) Design a logical circuit for Z using 2-inputs NOR gate



Q2: Implement the following expression with a MUX

a) $F = \sum(0, 2, 5, 7, 11, 14)$ SOP

b) $F = \pi(3, 8, 12)$ POS

Solution

Q1

Input			Output
X	Y	C	Z
0	0	0	X
0	0	1	Y

Input			Output
X	Y	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

b) $Z = \overline{X} \cdot \overline{Y} \cdot \overline{C} + X \cdot \overline{Y} \cdot C + X \cdot Y \cdot \overline{C} + X \cdot Y \cdot C$


c) $Z = X \cdot \overline{C} + Y \cdot C$

d) $Z = \overline{Y \cdot C} + X \cdot \overline{C}$

$$= \overline{\overline{Y \cdot C}} + \overline{X \cdot \overline{C}}$$

$$= \overline{\overline{X \cdot C}} + \overline{\overline{Y \cdot C}}$$


X	Y	C	0	1
0	0	0	0	0
0	1	0	0	1
1	1	0	1	1
1	0	1	1	0

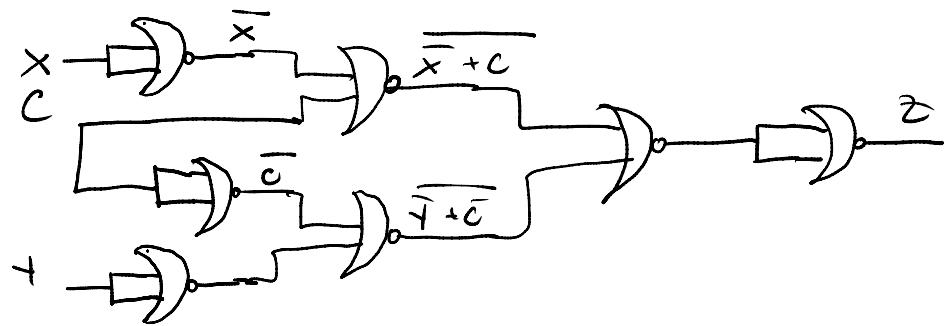

$Q_2 =$

a) $f = \Sigma(0, 2, 5, 7, 11, 14)$ $2^n \geq m$
 $2^n \geq 14 \Rightarrow n = 4$

Input				LSB	Output	
0	0	0	0	1	$F = D'$	<u>I0</u>
1	0	0	1	0	$F = D'$	<u>I1</u>
2	0	0	1	1	$F = D'$	
3	0	0	1	0	$F = D$	
4	0	1	0	0	$F = D$	<u>I2</u>
5	0	1	0	1	$F = D$	
6	0	1	1	0	$F = D$	<u>I3</u>
7	0	1	1	1	$F = D$	
8	1	0	0	0	$F = O$	<u>I4</u>
9	1	0	0	1	$F = O$	
10	1	0	1	0	$F = D$	<u>I5</u>
11	1	0	1	1	$F = D$	
12	1	1	0	0	$F = O$	<u>I6</u>
13	1	1	0	1	$F = O$	
14	1	1	1	0	$F = D'$	<u>I7</u>
15	1	1	1	1	$F = D'$	

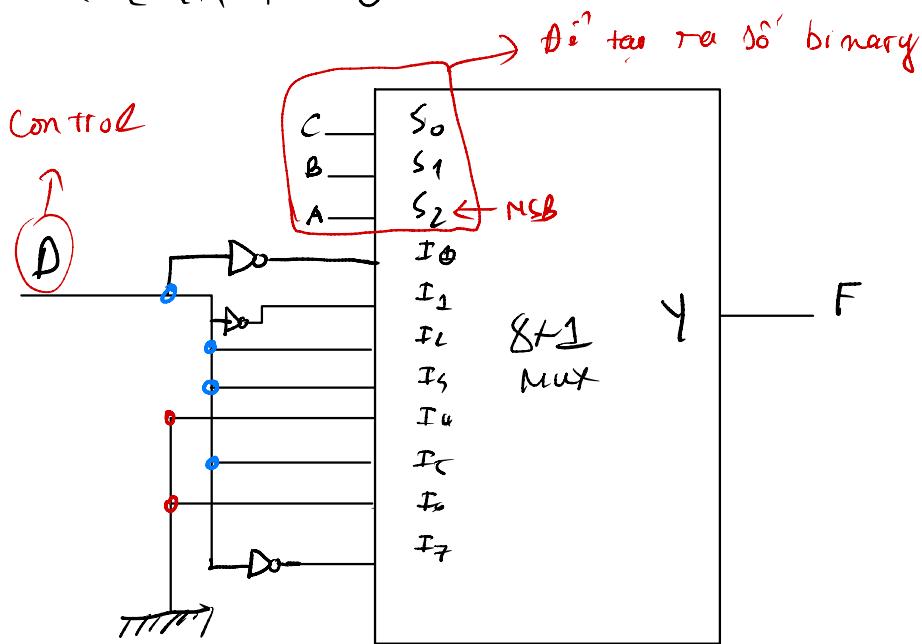

$$b) F = \pi_6(3, 8, 12),$$

	Input				Output
	A	B	C	D	Y
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

$$F = 1$$

$$F = D'$$

$$F = 1$$

$$F = 1$$

$$F = D$$

$$F = 1$$

$$F = D$$

$$F = 1$$

