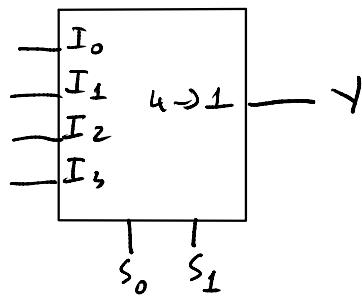


S_0	Y
0	I_0
1	I_1

$$Y = \bar{S}_0 I_0 + S_0 I_1$$


Mux 4 \rightarrow 1



S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Y = \bar{S}_0 \bar{S}_1 I_0 + \bar{S}_0 S_1 I_1 + S_0 \bar{S}_1 I_2 + S_0 S_1 I_3$$

De Mux: 1 \rightarrow 4

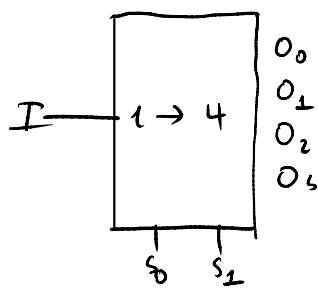


S_0	S_1	O_0	O_1	O_2	O_3
0	0	I	0	0	0
0	1	0	I	0	0
1	0	0	0	I	0
1	1	0	0	0	I

$$O_0 = \bar{S}_0 \bar{S}_1 I, O_1 = \bar{S}_0 S_1 I, O_2 = S_0 \bar{S}_1 I, O_3 = S_0 S_1 I$$

$$O_0 = \bar{S}_0 \bar{S}_1 I$$

Multiplexers:

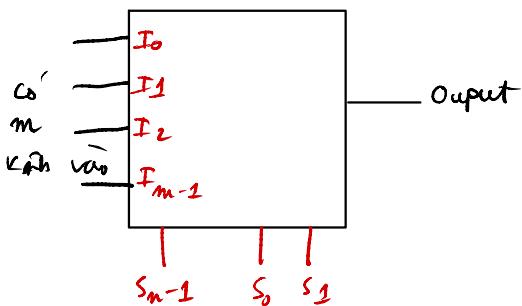


$$2^n \geq m$$

Vd: 8 kênh \Rightarrow 3 bit điều khiển

4 kênh \Rightarrow 2 bit

Có n tín hiệu chọn kênh
Mux 2-1

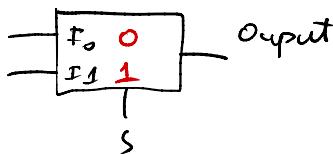

$$S=0, D = I_0$$

$$S=1, D = I_1$$

Input	Output
$I_1 \ 0 \ I_0 \ 0 \ S \ 0$	$D \ 0$
$0 \ 0 \ 0 \ 1 \ S \ 1$	$0 \ 0$
$0 \ 1 \ 0 \ 0 \ S \ 0$	$1 \ 0 \times$
$0 \ 1 \ 1 \ 1 \ S \ 1$	$0 \ 0$
$1 \ 0 \ 0 \ 0 \ S \ 0$	$1 \ 1 \times$
$1 \ 0 \ 1 \ 1 \ S \ 1$	$1 \ 1 \times$
$1 \ 1 \ 0 \ 0 \ S \ 0$	$1 \ 1 \times$
$1 \ 1 \ 1 \ 1 \ S \ 1$	$1 \ 1 \times$


$$D = \overline{I_1} I_0 S + I_1 \overline{I_0} S + I_1 I_0 \overline{S} + I_1 I_0 S$$

$$= I_0 \overline{S} + I_1 S$$



bằng rút gọn

$$\Rightarrow D = I_0 \overline{S} + I_1 S$$

Input	Output
$I_1 \ I_0 \ S$	D
$X \ I_0 \ 0$	I_0
$I_1 \ X \ 1$	I_1

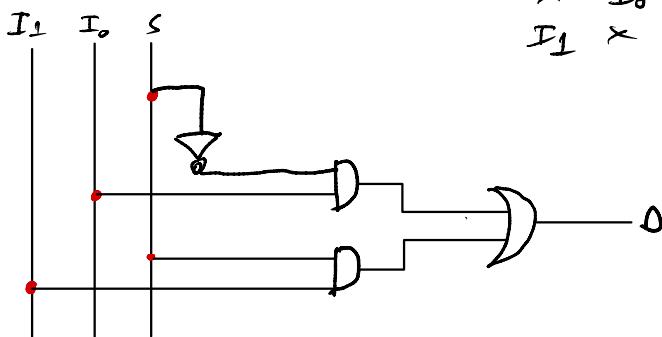



4-1:

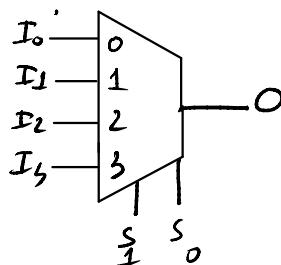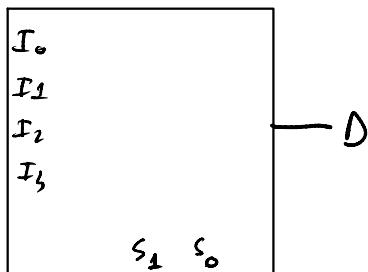

Inputs				Outputs		
I_3	I_2	I_1	I_0	S_1	S_0	D
\times	\times	\times	I_0	0	0	I_0
\times	\times	I_1	\times	0	1	I_1
\times	I_2	\times	\times	1	0	I_2
I_3	\times	\times	\times	1	1	I_3
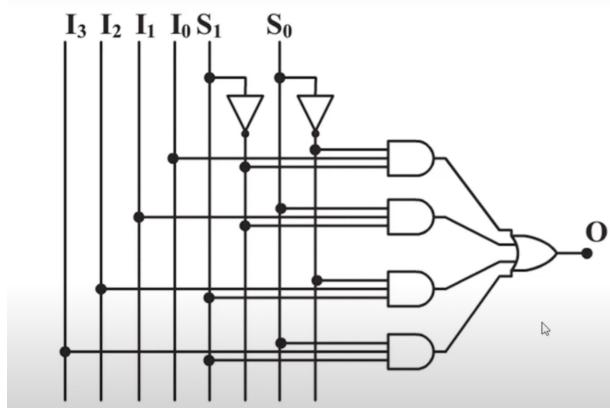
$$D = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$



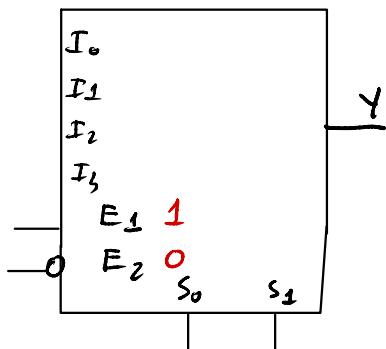


Inputs				Output
E_2	E_1	S_1	S_0	Y
X	0	X	X	0
1	X	X	X	0
0	1	0	0	I_o
0	1	0	1	I_1
0	1	1	0	I_2
0	1	1	1	I_3


E_1 tích cực cao, E_2 tích cực thấp

⇒ Chỉ cho kính ra khi E_1, E_2 tích cực
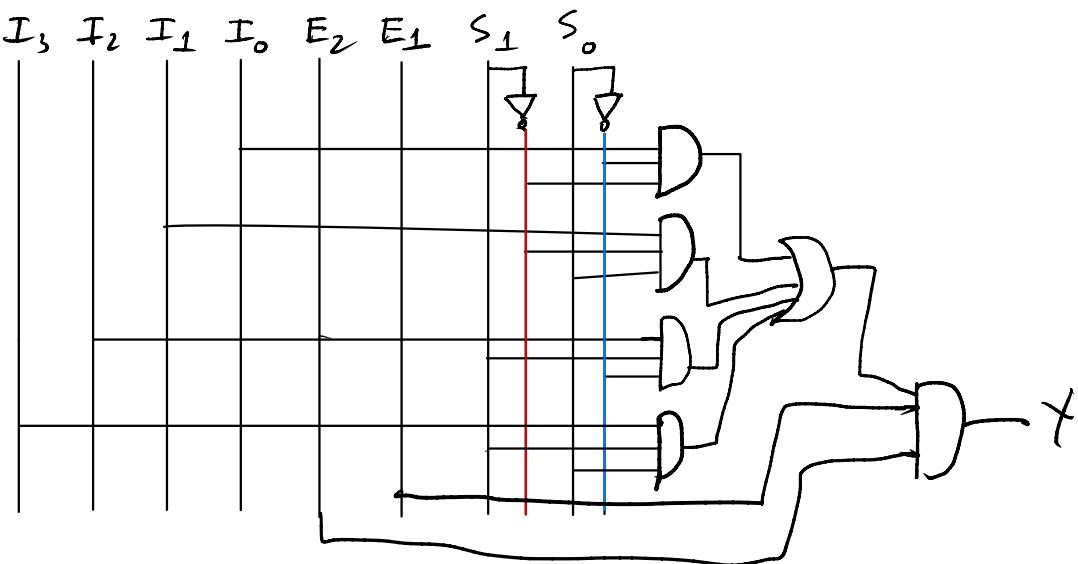
$$Y = \bar{E}_2 E_1 \left(F_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0 \right)$$



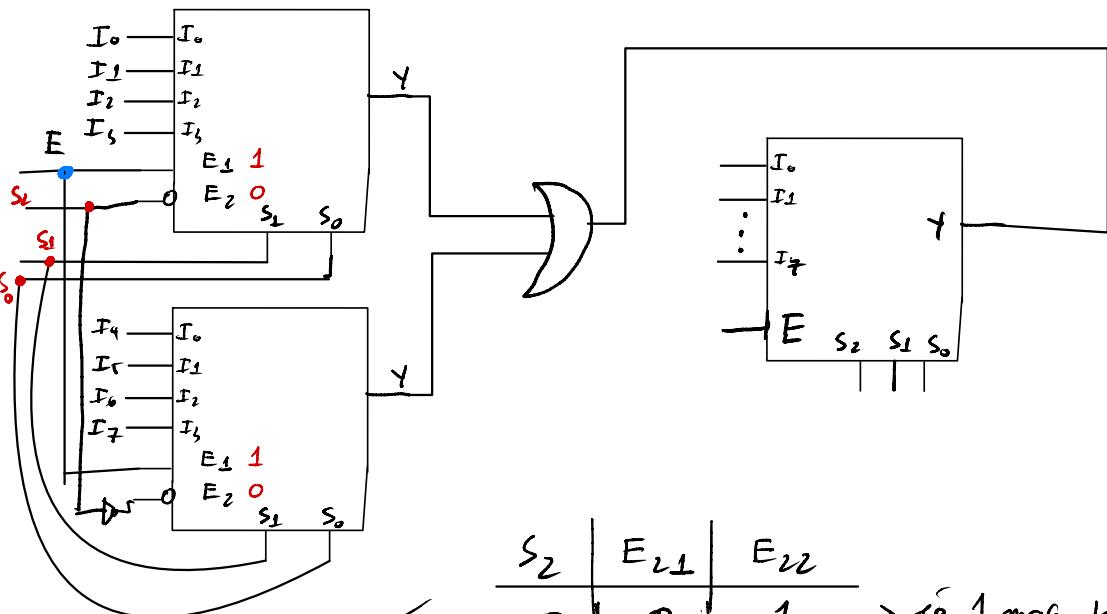$4 \rightarrow 1 + 4 \rightarrow 1 \rightarrow 8 \rightarrow 1 \rightarrow E_2$ tích up thấp



S_2	E_{21}	E_{22}
0	0	1
1	1	0

áp 1 маш ko hét

áp 1 маш bro hét

$$E_{22} = \bar{S}_2$$

$$E_{21} = S_2$$

