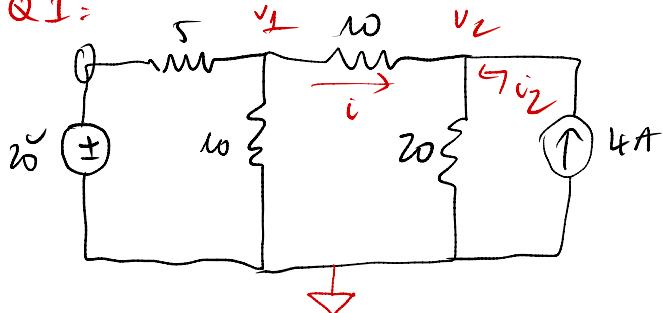


Time : 90 minutes

Note A 4

Content : All

Q1:




$$\frac{V_1 - 20}{5} + \frac{V_1 - V_2}{10} + \frac{V_1}{20} = 0 \Rightarrow \begin{cases} V_1 = 20 \text{ V} \\ V_2 = 40 \text{ V} \end{cases}$$
$$\frac{V_2 - V_1}{10} + \frac{V_2}{20} - 4 = 0$$

b) $\underline{I} = \frac{V_1 - V_2}{10} = 2A$


c) $P_{uA} = -V_I = (40)(-4) = -160 \text{ W}$

Q, :

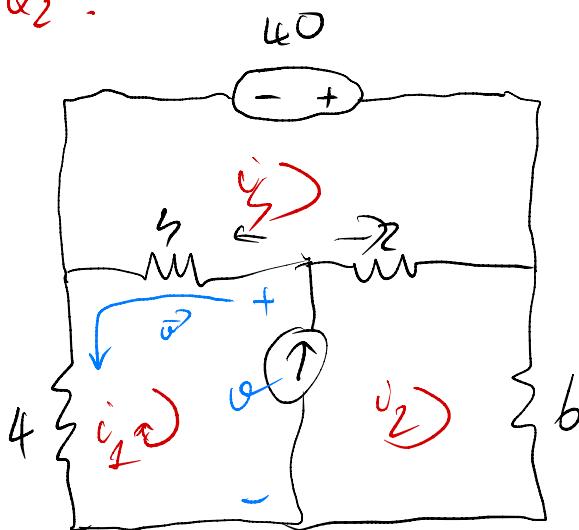

- a) mesh
 - b) Please
 - c) $\vartheta = ?$

$$i_2 - i_1 = 16^A$$

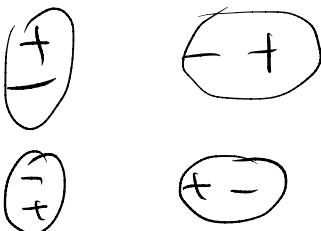

$$a) \text{ Loop 3: } 2(c_3 - c_2) + 3(c_3 - c_2) = 40 \quad (1)$$

$$\text{loop (1)(2): } 4v_4 + 3(v_1 - v_3) + 2(v_2 - v_3) + 6 = 0 \quad (2)$$


$$(1)(2)(4) \Rightarrow \left\{ \begin{array}{l} i_1 = -5,6 \text{ A} \\ i_2 = 10,4 \text{ A} \\ i_3 = 8,8 \text{ A} \end{array} \right.$$

$$b) P_{i_{40}v} = -IV = (-8.8)(40) = -352 \text{ W}$$




$$c) \quad \vartheta = 3(\vartheta_3 - \vartheta_1) - 4\vartheta_1 =$$

$$\text{or } \vartheta = 2(c_2 - c_3) + 6c_2 =$$

Q5:

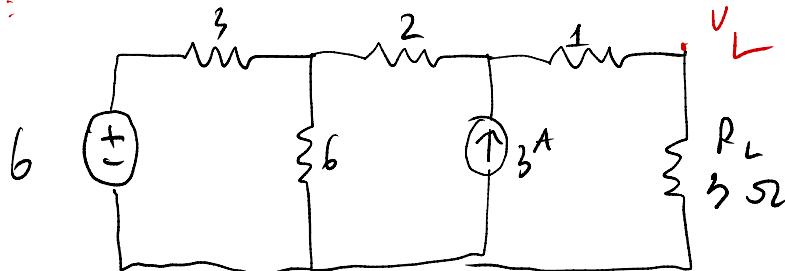

$$I = \frac{6}{3} = 3^A,$$

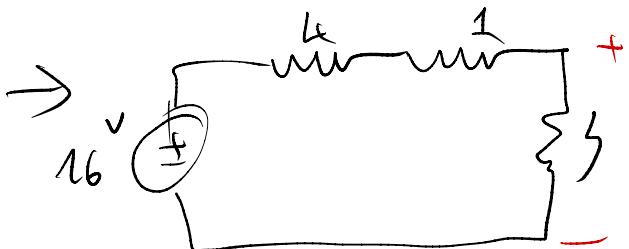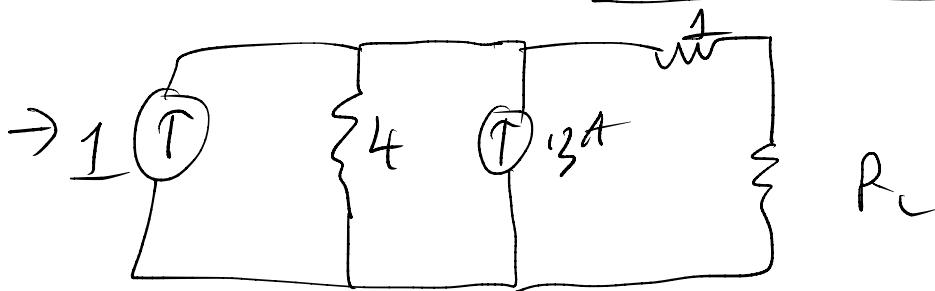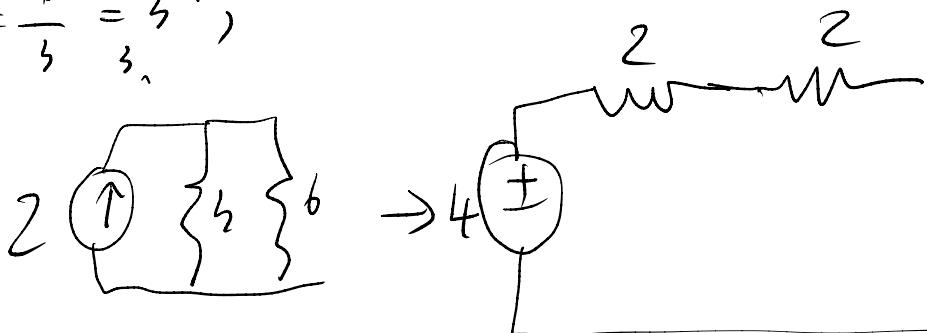


$$V_L = 16 \frac{3}{4+1+3} = 6^V$$

$$P_{3A} = -3^A \times 8 = -24^W$$

$$\vartheta = 2(1+3) = 8^V$$


Q 4 :

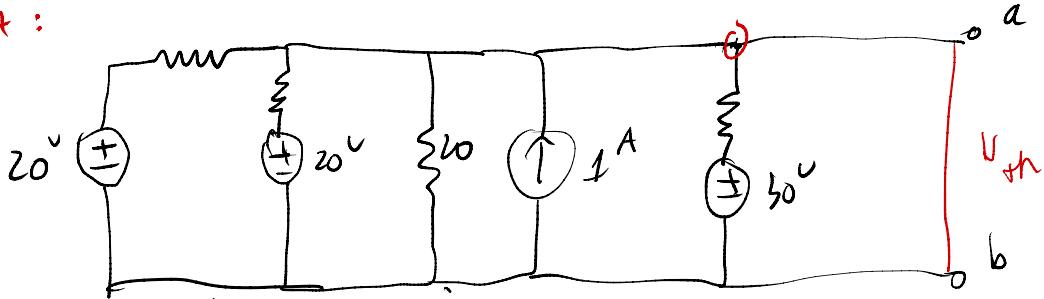

a) V_{th} b) $P_{max} R_L$?


$$\frac{V_{th} - 20}{20} + \frac{V_{th} - 60}{10} + \frac{V_{th}}{10} - 1 + \frac{V_{th} - 40}{10} = 0$$
$$\Rightarrow V_{th} = 22V$$

b)

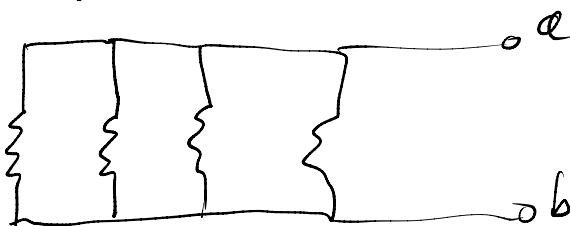

$$R_{th} = R_{ab} = 4\Omega$$


c)

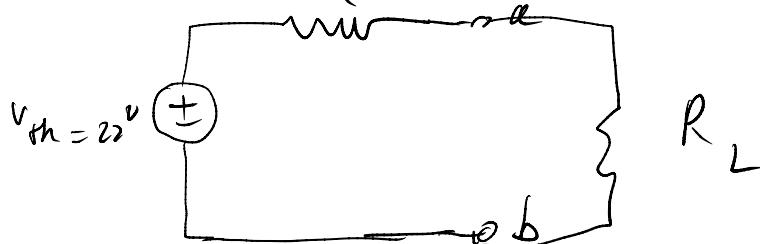

$$\text{When } R_L = R_{th} = 4\Omega$$

$$P_{R_{max}} = \frac{V_{th}^2}{4R_L} = 30.25W$$

Question 5:

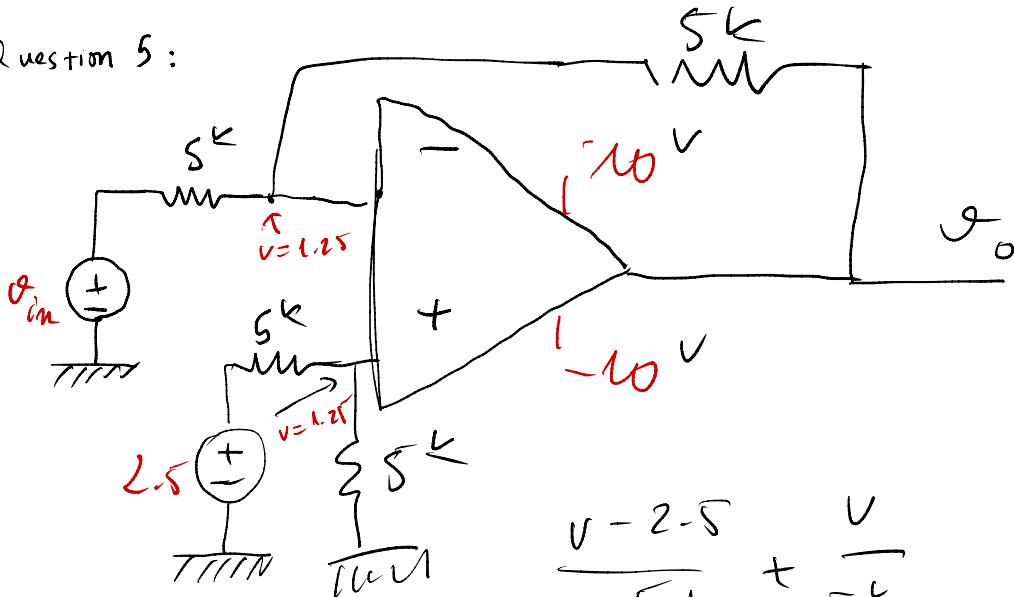

$$\frac{v - 2.5}{5k} + \frac{v}{5k} = 10$$

$$\Rightarrow v = 1.25V$$

$$v_o = \frac{5k \times 10}{5k \times 10} + 2.5 - \frac{5k}{5k} v_A$$

$$(2) v_o = 2.5 - v_A$$

$$(3) 2.5 - v_A = 10 \Rightarrow v_A = -7.5$$

$$2.5 - v_A = -10 \Rightarrow v_A = 12.5V$$

Difference Amplifier Circuit

$$-19i_3 + i_a(4+6) + i_2(2.5+7.5) + i_3(2+8) + 0.8i_0 \\ + 0.8(-7.5i_b) - 6i_b$$

$$= 10i_a + 4i_b + 10i_c = 19i_3 \quad (1)$$

$$i_a = 2i_c$$

$$0.4i_a = i_b - i_a$$

$$\Leftrightarrow 0.8i_c = i_b - i_a$$

$$\Leftrightarrow -i_a + i_b - 0.8i_c = 0 \quad (2)$$

$$0.5 = i_c - i_a \quad (3)$$

$$\Rightarrow \begin{cases} i_1 = 2 \\ i_2 = 4 \\ i_3 = 2.5 \end{cases}$$

$$a) v_o = -\left(\frac{250}{5} \times 0.1 + \frac{250}{25} \times 0.25\right) = -7.5 \text{ V}$$

b) If $v_b = 0.25 \text{ V}$, how large be v_a before saturation:


$$v_o = -\left(\frac{250}{5} v_a + \frac{250}{25} \times 0.25\right) = -10 \quad \left. \begin{array}{l} \\ 15 \end{array} \right\}$$

$$\rightarrow v_a = 0.15 \text{ V} \quad \Rightarrow 0.15 \leq v_a \leq 0.15 \text{ V}$$

$$v_a = -0.35$$

$$\frac{v_b - 1.5}{25 \text{ k}} + \frac{v_b - (-10)}{100 \text{ k}} = -0.8 \text{ V}$$
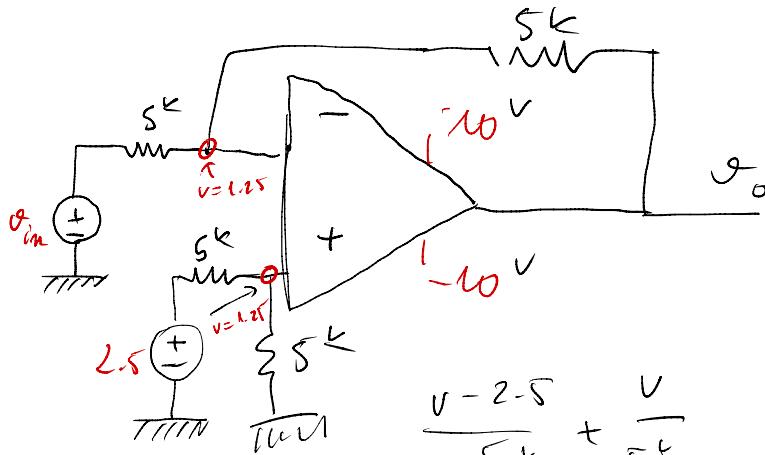
$$v_o = 10 \rightarrow v_b = 3.2 \text{ V}$$



$$\frac{v - 2.5}{5\text{ k}} + \frac{v}{5\text{ k}} = 0 \Rightarrow v = 1.25\text{ V}$$

$$\frac{v_b - 2.5}{5\text{ k}} + \frac{v_b}{5\text{ k}} = 0 \Rightarrow v_b = 1.25\text{ V}$$

$$\text{Node I: } \frac{1.25 - v_a}{5\text{ k}} + \frac{1.25 - 10}{5\text{ k}} = 0$$

$$\Rightarrow v_a = -7.5\text{ V}$$

$$v_o = 10 \rightarrow v_o = 12.5\text{ V}$$