

Techniques of Circuit Analysis

(Chapter 4)


Link to download materials:

[Blackboard of IU](#)

Outline


- *The node-voltage method*
- *The mesh-current method*
- *Source transformation*
- *Thevenin & Norton equivalents*
- *Maximum power transfer*
- *Superposition*

Terminology

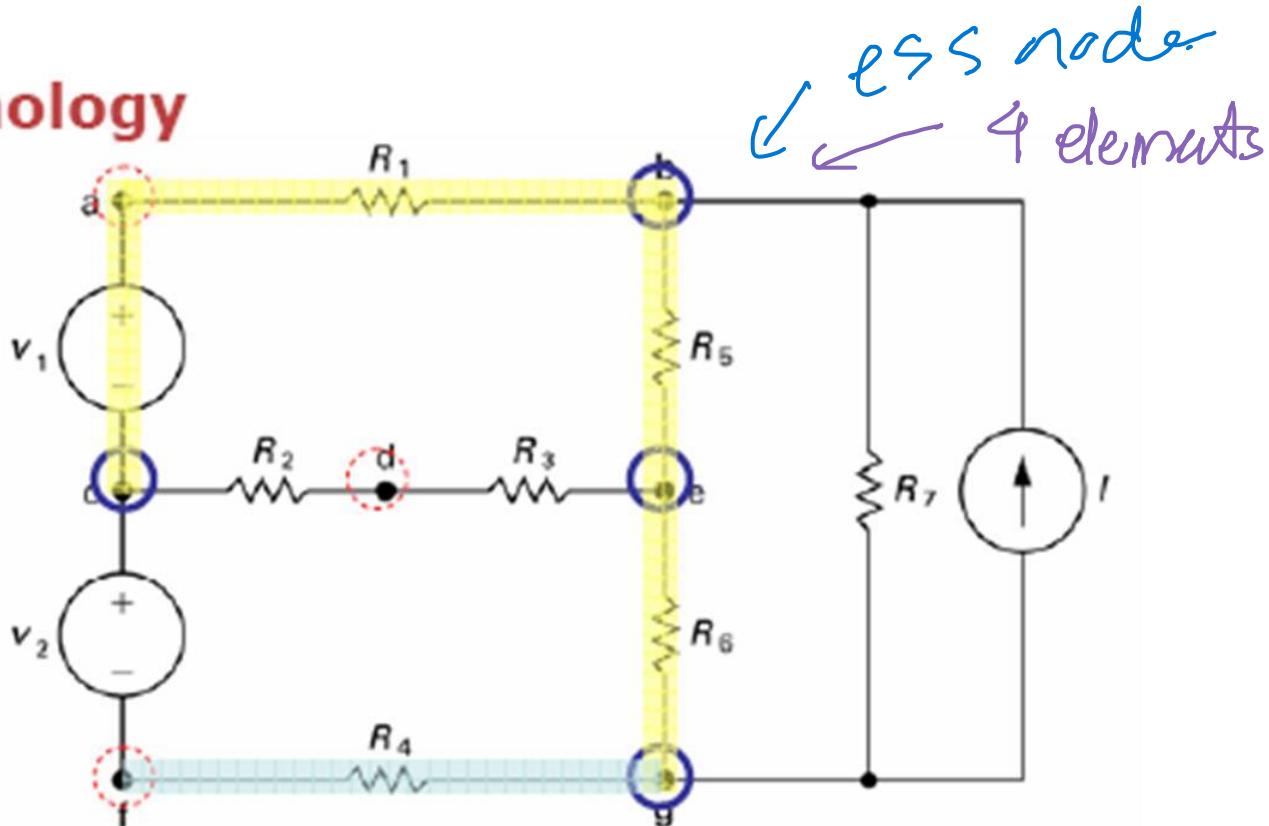

Node	A point where two or more circuit elements join	a, f
Essential Node	A node where three or more circuit elements join	b, e, g
Path	A trace of adjoining basic elements with no elements included more than once	$v_1-R_1-R_5-R_6$
Branch	A path that connects two nodes	R_4


Terminology

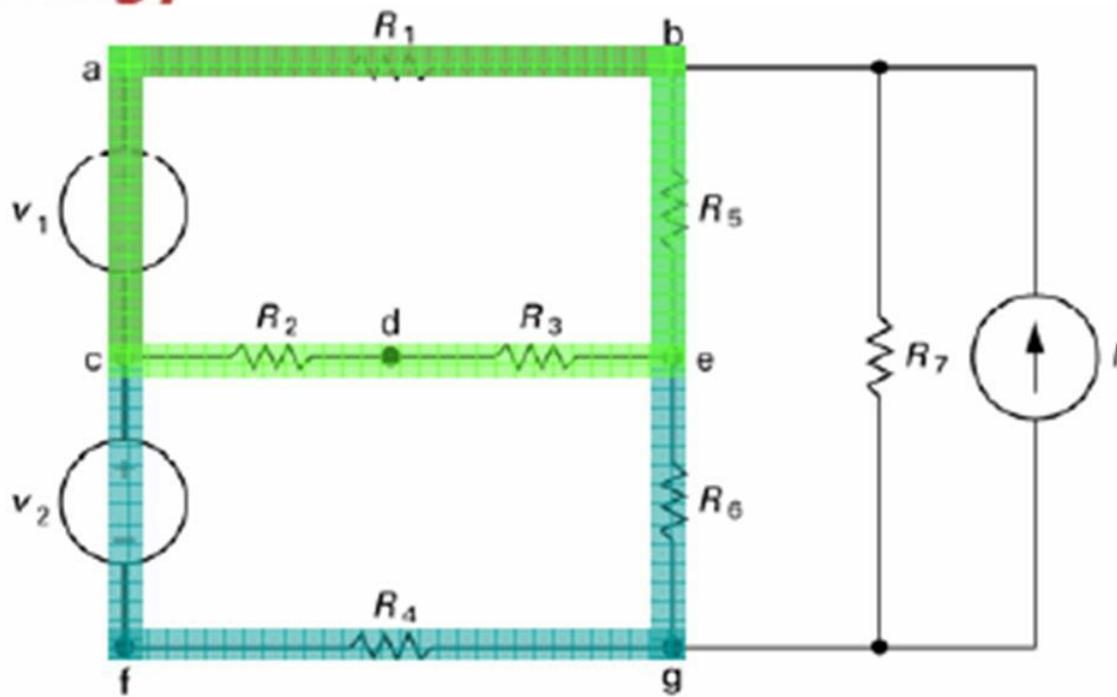

Essential branch	A path which connects two <u>essential nodes</u> without passing through an <u>essential node</u>	$v_1 - R_1$
Loop	A path whose last node is the same as the <u>starting node</u>	$v_1 - R_1 - R_5 - R_6 - R_4 - v_2$
Mesh	A loop that does not enclose any other loop	$v_1 - R_1 - R_5 - R_3 - R_2$


↙ Loop nhỏ nhất / Lớp đơn

Planar and Non-planar circuit

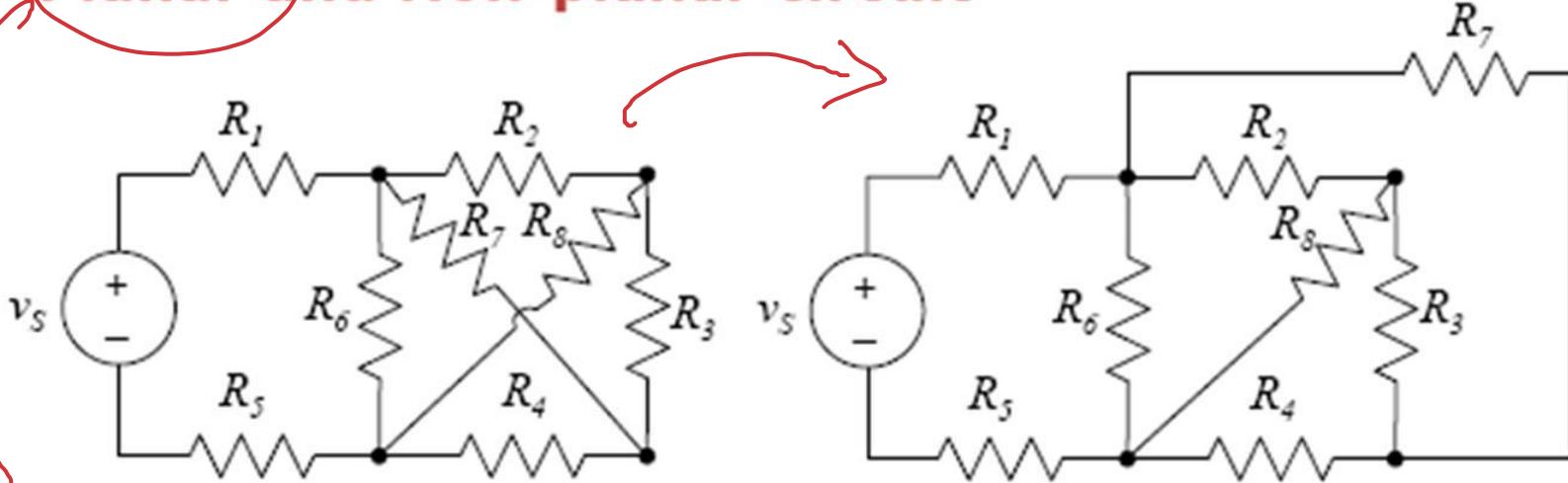

Planar Circuits

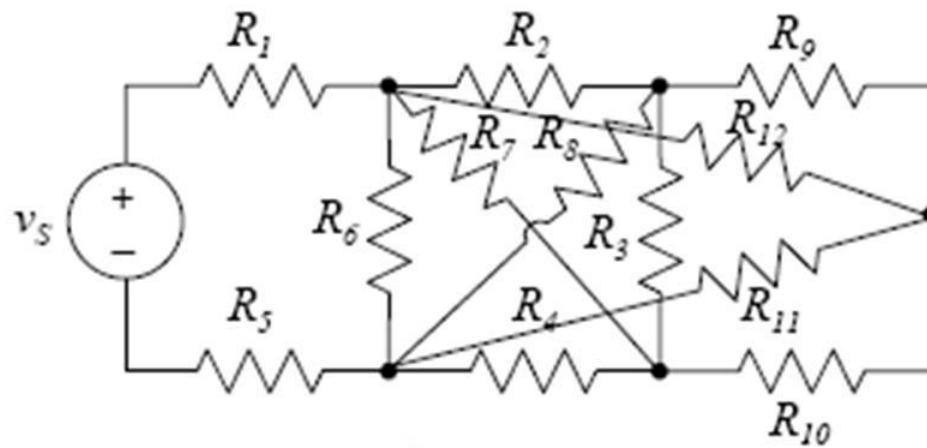
Planar circuit is a circuit that can be drawn on a plane with no crossing branches



Non-Planar Circuits

Introduction to node-voltage method

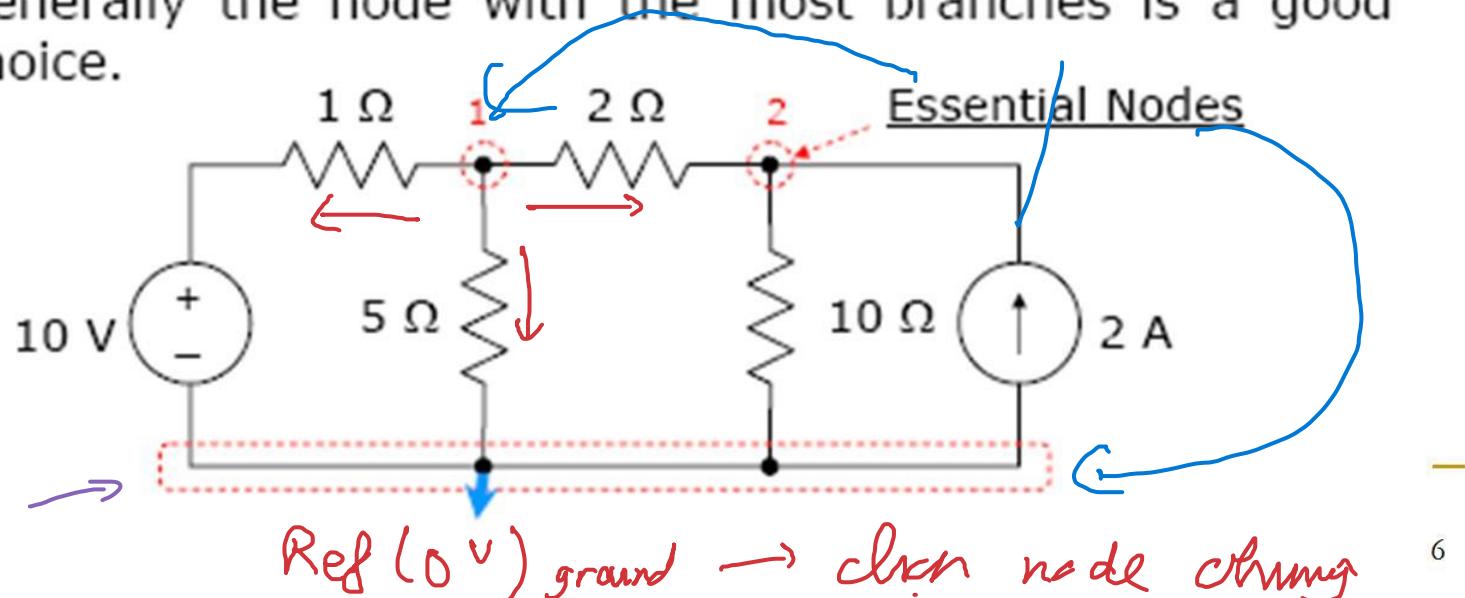- Can be applied to both planar and non-planar circuits.
- 1st redraw the circuit so that no branches cross over.
- 2nd mark clearly all essential nodes in the circuit.
 - In a circuit with n_e essential nodes, $\frac{n_e - 1}{2}$ node voltage can be written.
- 3rd select one of the essential nodes to be the reference node. (0V)
 - Generally the node with the most branches is a good choice.




$$V_2 : \frac{V_2 - V_1}{2} + \frac{V_2}{10} - 2 = 0 \quad (2)$$

$$V_1 : \frac{V_1 - 10}{1} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0 \quad (1)$$

Introduction to node-voltage method

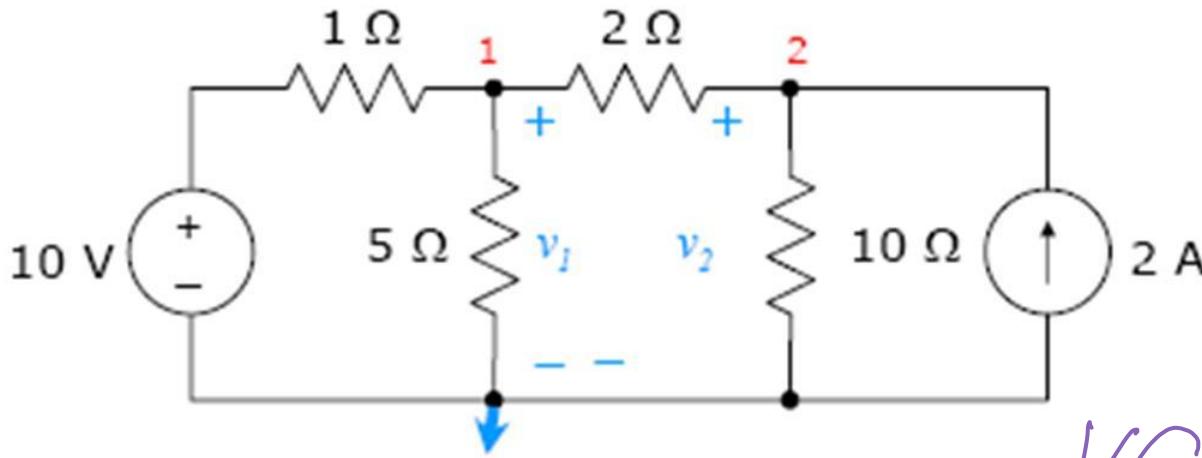- 4th define the node voltages. 
- Voltage rise from the reference node to a non-reference node.








- 5th generate the node-voltage equations.
 - Write the current leaving each branch connected to a non-reference node as a function of the node voltages.
 - Apply KCL at the nodes by summing the currents.

$$\sum i = 0$$

Introduction to node-voltage method

- At node 1

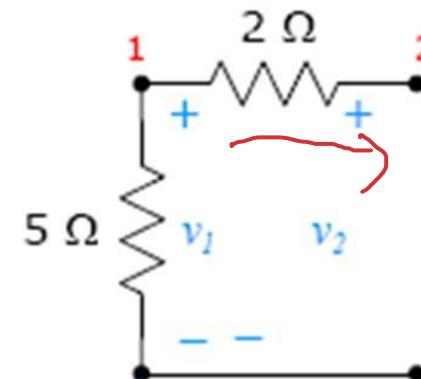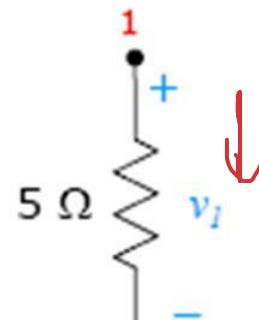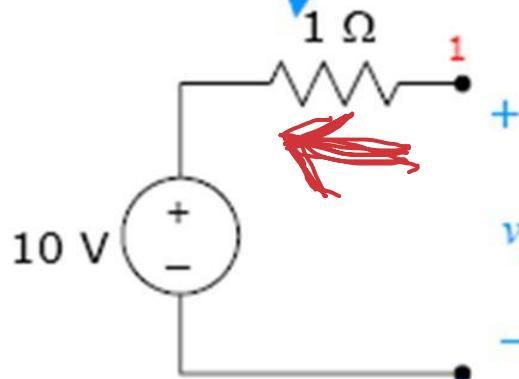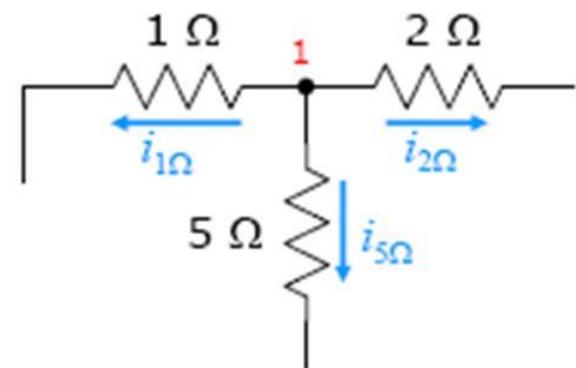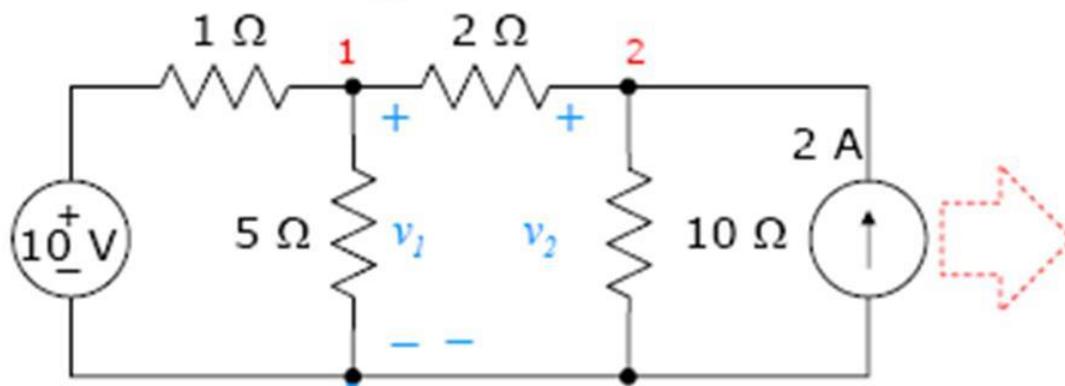

KCL





$$i_{1\Omega} = \frac{v_1 - 10}{1}$$

$$i_{5\Omega} = \frac{v_1}{5}$$

$$i_{2\Omega} = \frac{v_1 - v_2}{2}$$

Introduction to node-voltage method

- At node 2

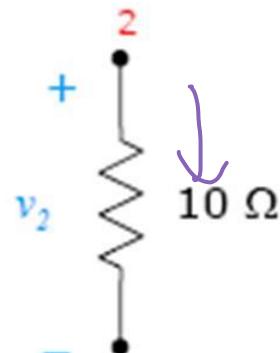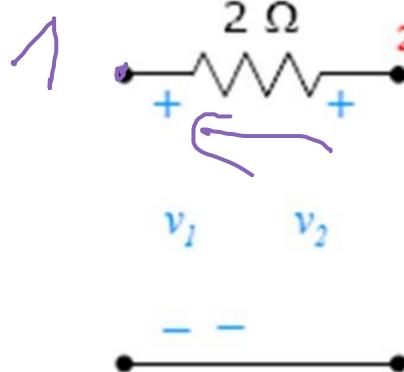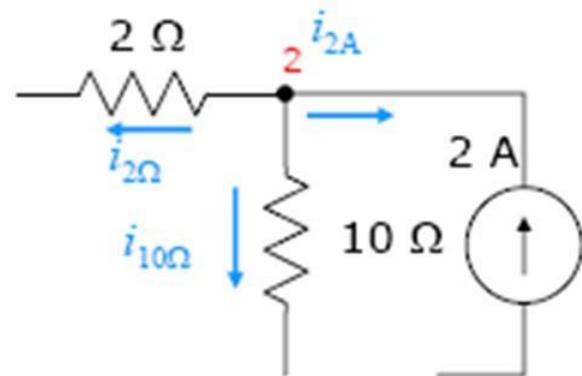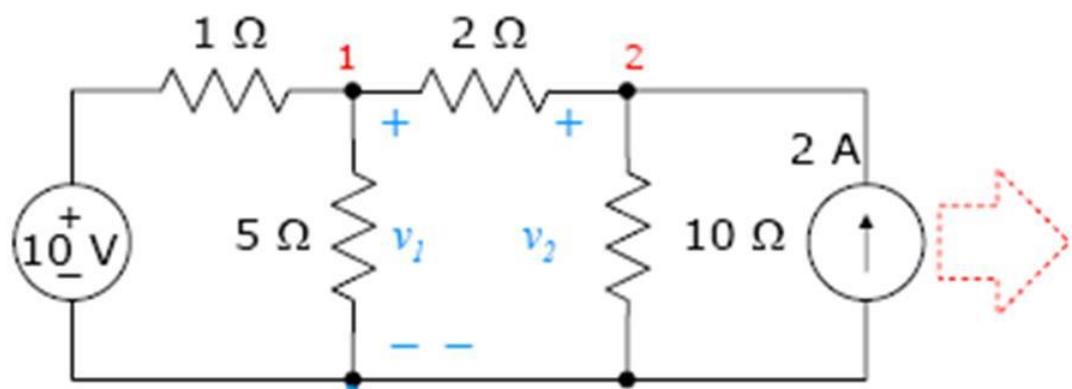

$$i_{2\Omega} = \frac{v_2 - v_1}{2}$$

$$i_{10\Omega} = \frac{v_2}{10}$$

$$i_{2A} = -2$$



$$10(v_1 - 10) + 2v_1 + 5(v_1 - v_2) = 0$$

$$12v_1 - 5v_2 = 100$$

Introduction to node-voltage method

KCL
 $i_{1\Omega} + i_{5\Omega} + i_{2\Omega} = 0$

KCL
 $i_{2\Omega} + i_{10\Omega} + i_{2A} = 0$

$$\frac{v_1 - 10}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0 \quad (1)$$

$$\frac{v_2 - v_1}{2} + \frac{v_2}{10} - 2 = 0 \quad (2)$$

Rearranging the equations

$$5(v_2 - v_1) + v_2 - 20 = 0$$

$$\begin{cases} 17v_1 - 5v_2 = 100 \\ -5v_1 + 6v_2 = 20 \end{cases}$$

$$v_1 = 9\frac{1}{11}V \quad \underline{v_2 = 10\frac{10}{11}V}$$

Or Using Matrices

$$\begin{bmatrix} 17 & -5 \\ -5 & 6 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 20 \end{bmatrix}$$

$$AV = I \quad V = A^{-1}I$$

$$i_{1\Omega} = \frac{10V - v_1}{1}$$


$$P_{10\Omega} = -v_1 i$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \frac{1}{(17 \times 6 - 25)} \begin{bmatrix} 6 & 5 \\ 5 & 17 \end{bmatrix} \begin{bmatrix} 100 \\ 20 \end{bmatrix} = \frac{1}{77} \begin{bmatrix} 700 \\ 840 \end{bmatrix}$$

$$= -10 \cdot i_{1\Omega}$$

Assessing Objective 1

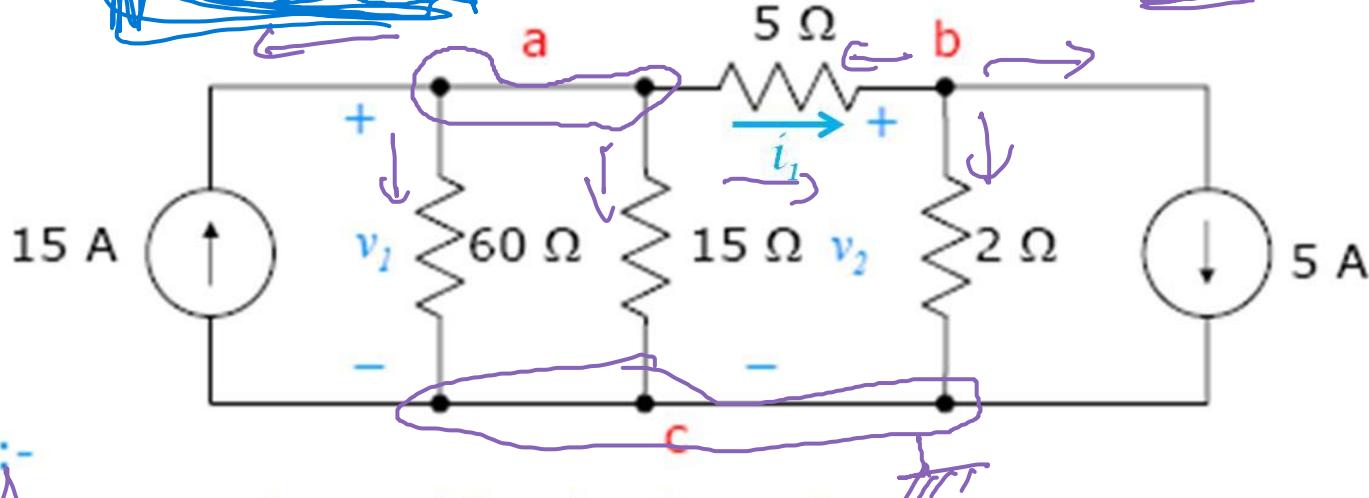Use the node voltage method to find v_1 , v_2 , and i_1 .



$$a) -15 + \frac{v_1}{60} + \frac{v_1}{15} + \frac{v_1 - v_2}{5} = 0$$

$$b) \frac{v_2 - v_1}{5} + \frac{v_2}{2} + 5 = 0$$

$$\begin{cases} v_1 = 60 \text{ V} \\ v_2 = 10 \text{ V} \\ i_1 = \frac{v_1 - v_2}{5} = 10 \text{ A} \end{cases}$$

Problem 1

4 essential nodes, 3 equations

Use the node-voltage method to find the branch currents i_1-i_6 .

Ans.:

$$1) \frac{v_1 - 110}{2} + \frac{v_1 - v_2}{8} + \frac{v_1 - v_3}{16} = 0$$

KCL

$$2) \frac{v_2 - v_1}{8} + \frac{v_2}{3} + \frac{v_2 - v_3}{24} = 0$$

$$3) \frac{v_3 + 110}{2} + \frac{v_3 - v_2}{24} + \frac{v_3 - v_1}{16} = 0$$

$$\begin{bmatrix} 11 & -2 & -1 \\ -3 & 12 & -1 \\ -3 & -2 & 29 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 880 \\ 0 \\ -2640 \end{bmatrix}$$

$$v_1 = 74.64 \text{ V}$$

$$v_2 = 11.79 \text{ V}$$

$$v_3 = -82.5 \text{ V}$$

$$i_1 = 17.68 \text{ A}$$

$$i_2 = 3.93 \text{ A}$$


$$i_3 = 13.75 \text{ A}$$

$$i_4 = 7.86 \text{ A}$$

$$i_5 = 3.93 \text{ A}$$

$$i_6 = 9.82 \text{ A}$$

$$i_1 = \frac{110 - v_1}{2}$$

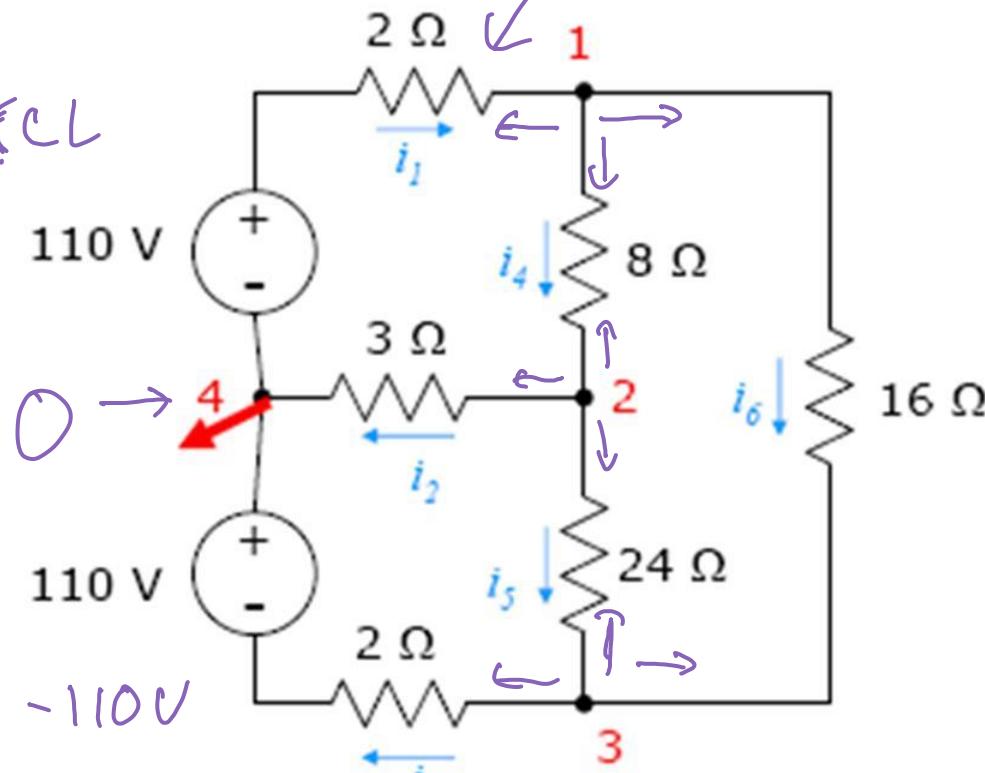

$$\frac{v_3 - (-110)}{2}$$




Problem 2

4 essential nodes, 3 equations

Use the node-voltage method to find the branch currents.

Ans.:

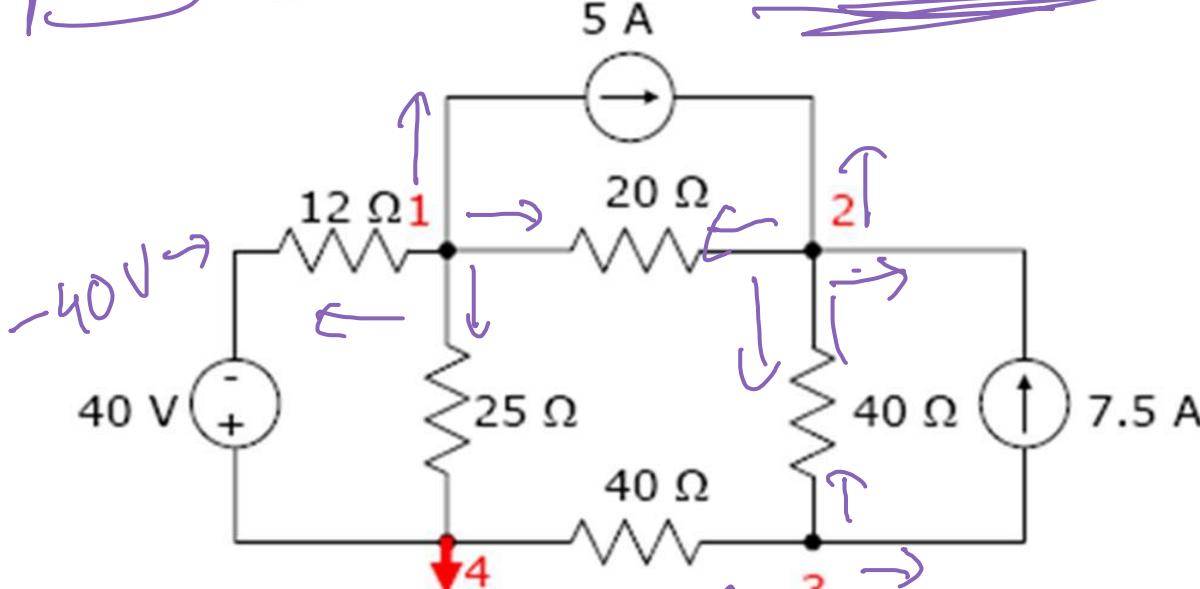

$$① \frac{v_1 + 40}{12} + \frac{v_1}{25} + 5 + \frac{v_1 - v_2}{20} = 0$$


$$② \frac{v_2 - v_1}{20} + \frac{v_2 - v_3}{40} - 7.5 - 5 = 0$$

$$③ \frac{v_3 - v_2}{40} + \frac{v_3}{40} + 7.5 = 0$$

$$\left. \begin{aligned} v_1 &= -10 \text{ V} \\ v_2 &= 132 \text{ V} \\ v_3 &= -84 \text{ V} \end{aligned} \right\}$$

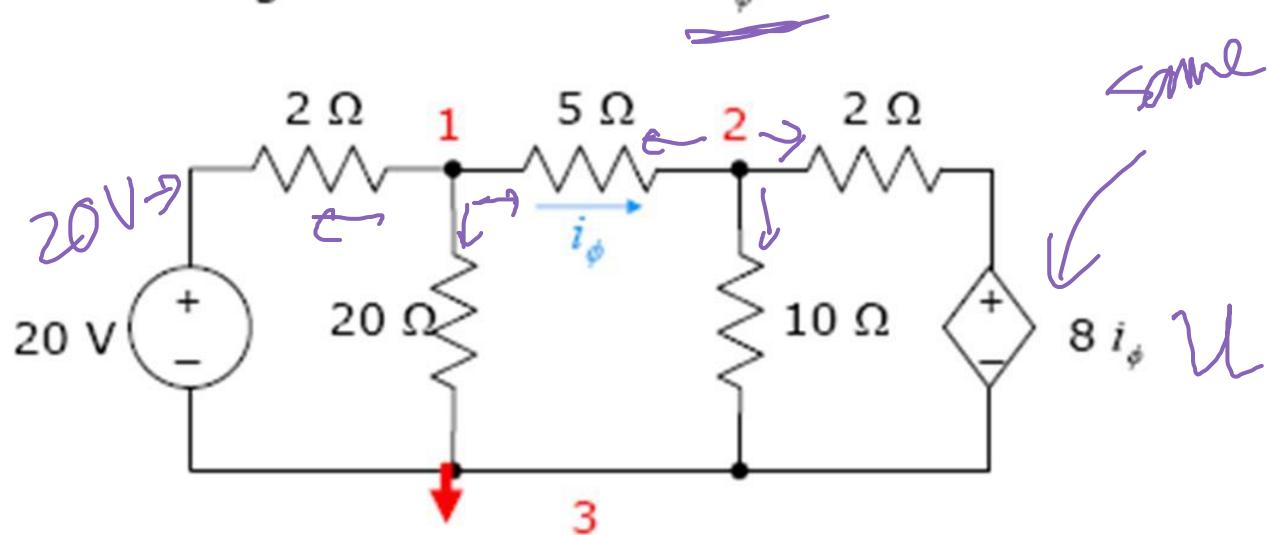Example 1

Use the node-voltage method to find i_ϕ .



Ans.: -


$$\begin{aligned} \textcircled{1} \quad & \frac{v_1 - 20}{2} + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0 \\ \textcircled{2} \quad & \frac{v_2 - v_1}{5} + \frac{v_2}{10} + \frac{v_2 - 8i_\phi}{2} = 0 \end{aligned} \quad \Rightarrow \quad \begin{cases} v_1 = 16 \text{ V} \\ v_2 = 10 \text{ V} \\ i_\phi = 1.2 \text{ A} \end{cases}$$
$$i_\phi = \frac{v_1 - v_2}{5}$$

3 essential nodes, 2 equations, we must express the controlling current in terms of the node voltages

Reduce number of equations

Special Cases

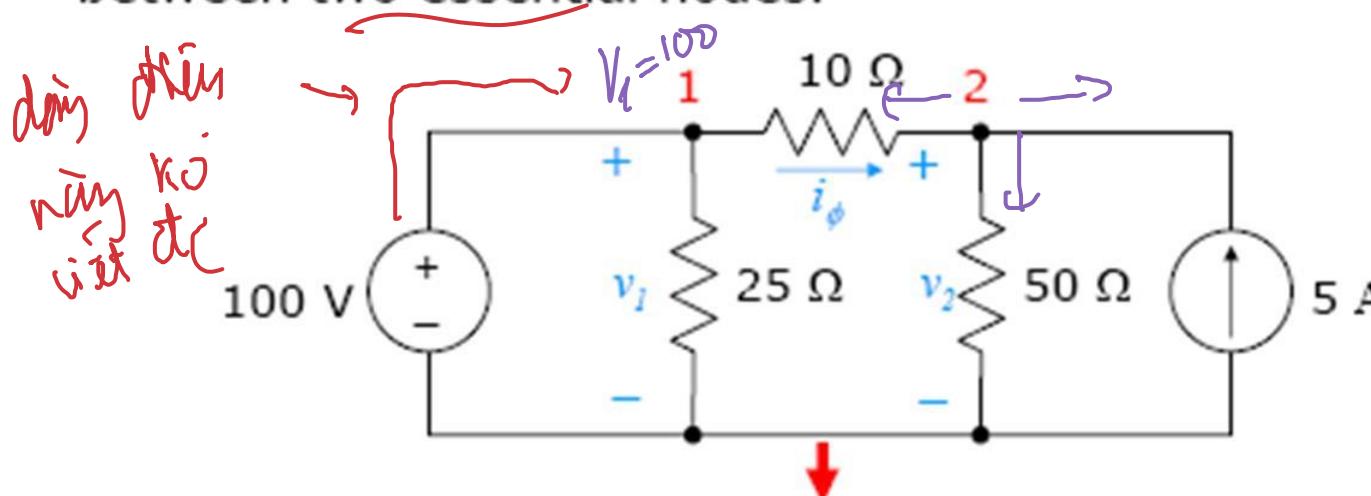- When a voltage source is the only element connected between two essential nodes.



$$\frac{v_2 - v_1}{10} + \frac{v_2}{50} - 5 = 0$$

$$v_1 = 100 V$$

$$v_2 = 125 V$$

Reduce 1 equation due to known node voltage

Problem 3


Use the node-voltage method to find v_o .

Ans.: -

a) $v_a = 40 \text{ V}$

b) $\frac{v_b - 40}{5} + \frac{v_b}{50} + \frac{v_b - v_c}{10} = 0$ *Ans y*

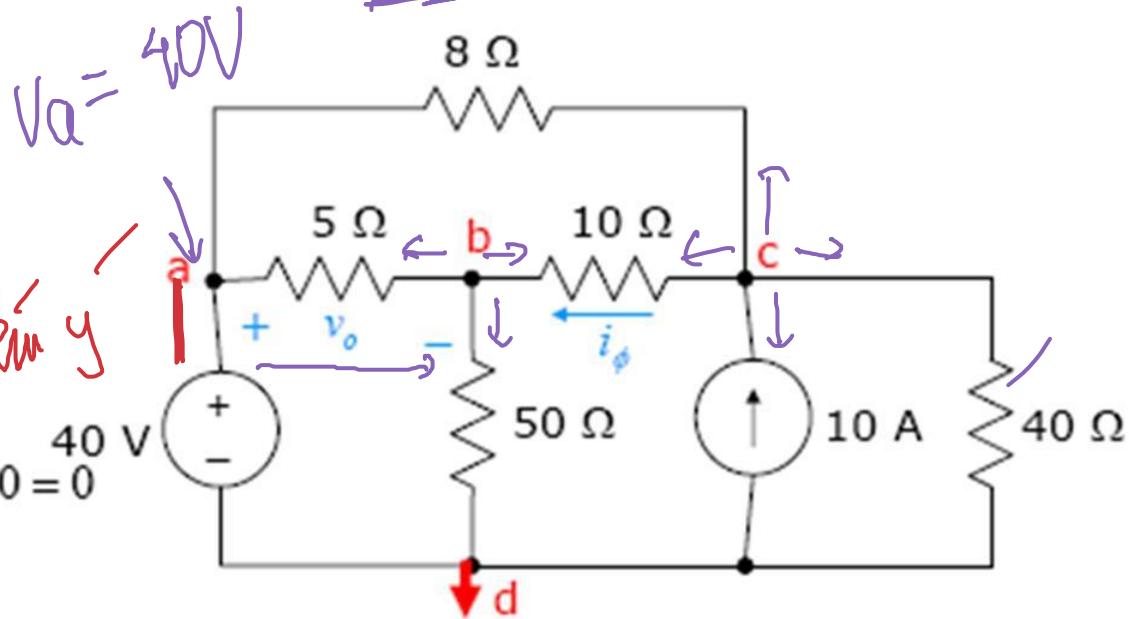c) $\frac{v_c - 40}{8} + \frac{v_c}{40} + \frac{v_c - v_b}{10} - 10 = 0$ $\frac{40}{8} = 5 \text{ V}$



$v_a = 40 \text{ V}$

$v_b = 50 \text{ V}$

$v_c = 80 \text{ V}$


~~$I_{D_s} = \frac{v_a - v_b}{5}$~~

Or $I_{D_s} > 0$ *Ans be true*

Problem 4

Use the node-voltage method to find i_1 , i_2 & i_3 .

Ans.: -

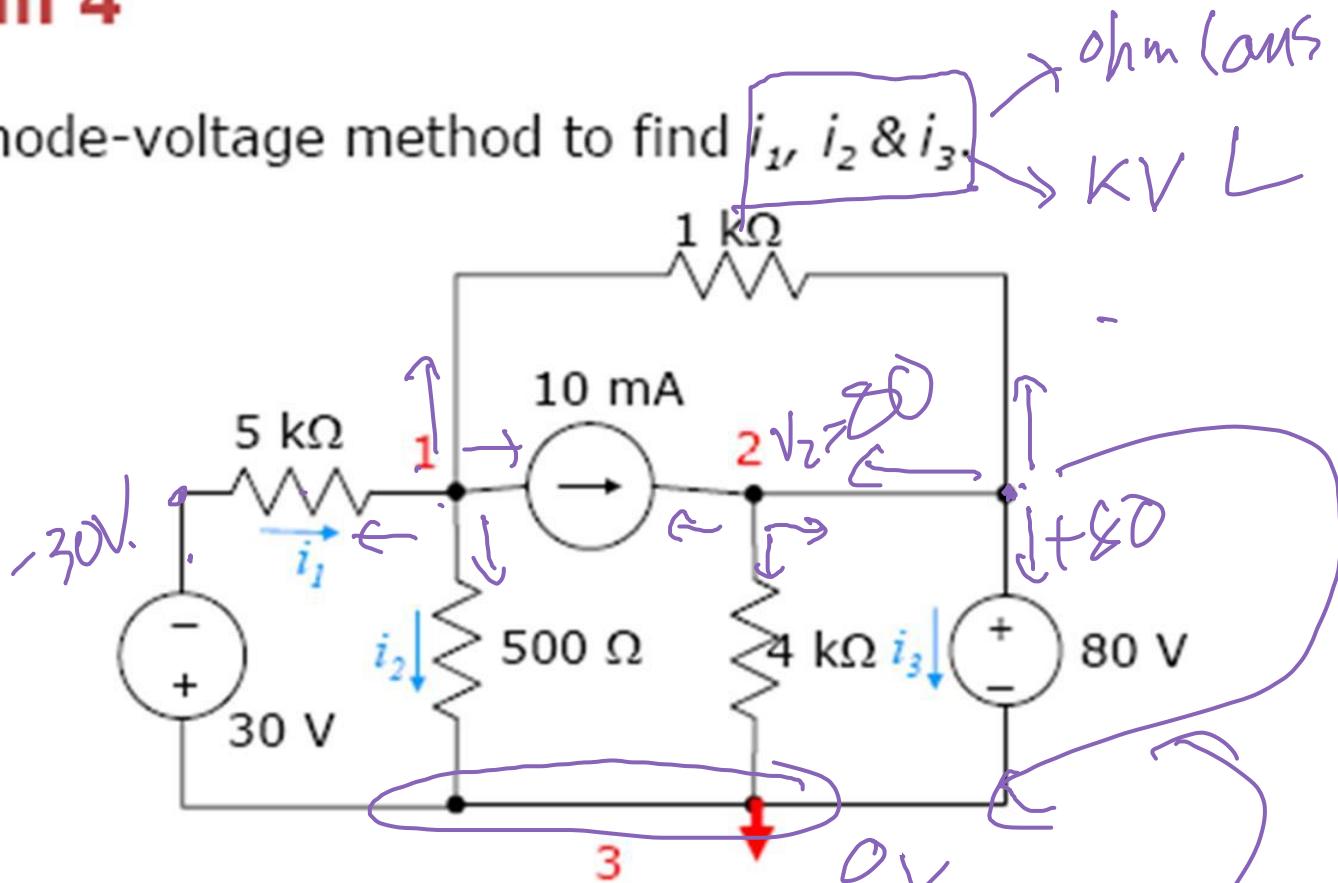

$$1) \frac{v_1 + 30}{5000} + \frac{v_1}{500} + \frac{v_1 - 80}{1000} + 10 \times 10^{-3} = 0$$

$$v_1 = 20 \text{ V}$$

$$V_2 = 80 \text{ V}$$

Write the equation @ node 2 by yourselves!


$$i_1 = \frac{-30 - v_1}{5000}$$

$$-10 \times 10^{-3} + \frac{V_2}{4000} + \dots$$

$$i_2 = \frac{V_1}{500}$$

Special Cases

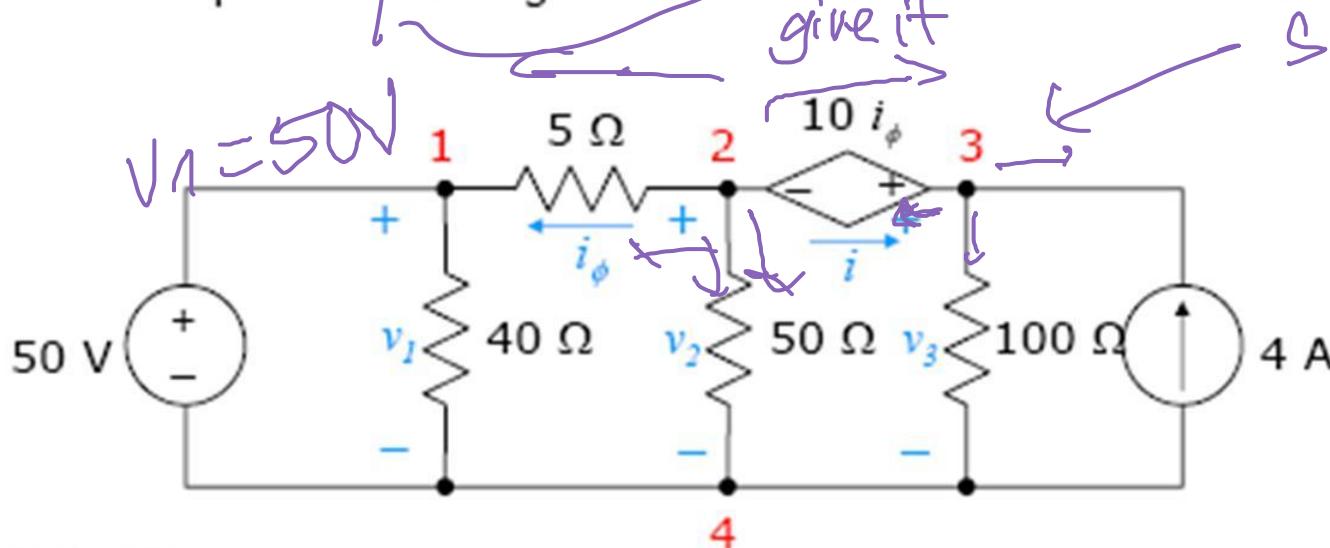- When a dependent voltage source is connected between nodes.



So in Super node
 \downarrow
 look b
 V₁ gain
 thanks
 1 node

First technique

$$1) \quad v_1 = 50 \text{ V}$$

$$2) \quad + \frac{v_2 - v_1}{5} + \frac{v_2}{50} + i = 0$$

$$- 3) \quad \frac{v_3}{100} - i - 4 = 0$$

Take sum

give it


? + try to eliminate

@ Super node

Special Cases

coi là 1 trout

Second technique (Super Node)

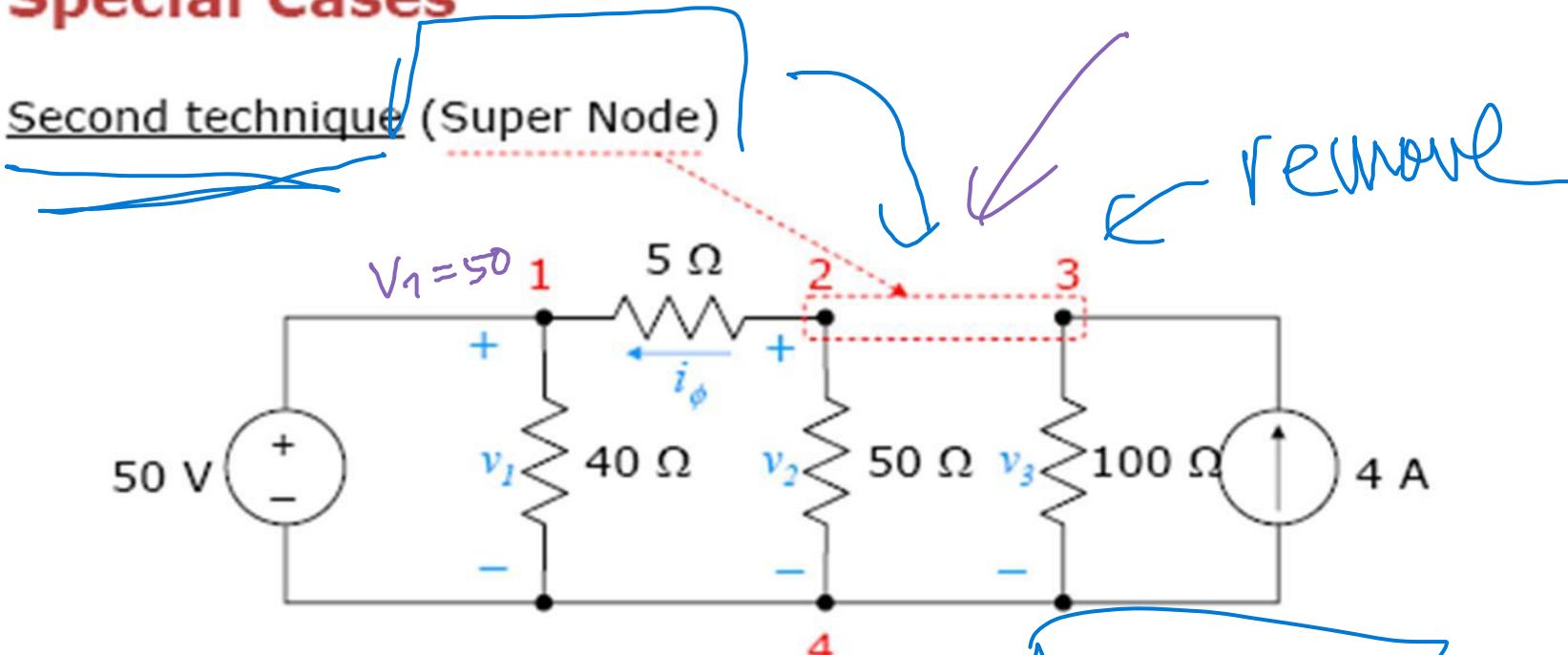

→ @ Super Node $\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0$

equation

Need more equations

$$v_3 = v_2 + 10i_\phi \quad \& \quad i_\phi = \frac{v_2 - v_1}{5} = \frac{v_2 - 50}{5}$$

$$v_1 = 50 \text{ V}$$

$$v_2 = 60 \text{ V}$$

$$v_3 = 80 \text{ V}$$

$10i_\phi$

$$V_1 = 50 \text{ V}$$

Assessing Objective 2

Use the node-voltage method to find v_o .


$$V_o = 0 \quad \text{KCL at node 1}$$

Ans.: -

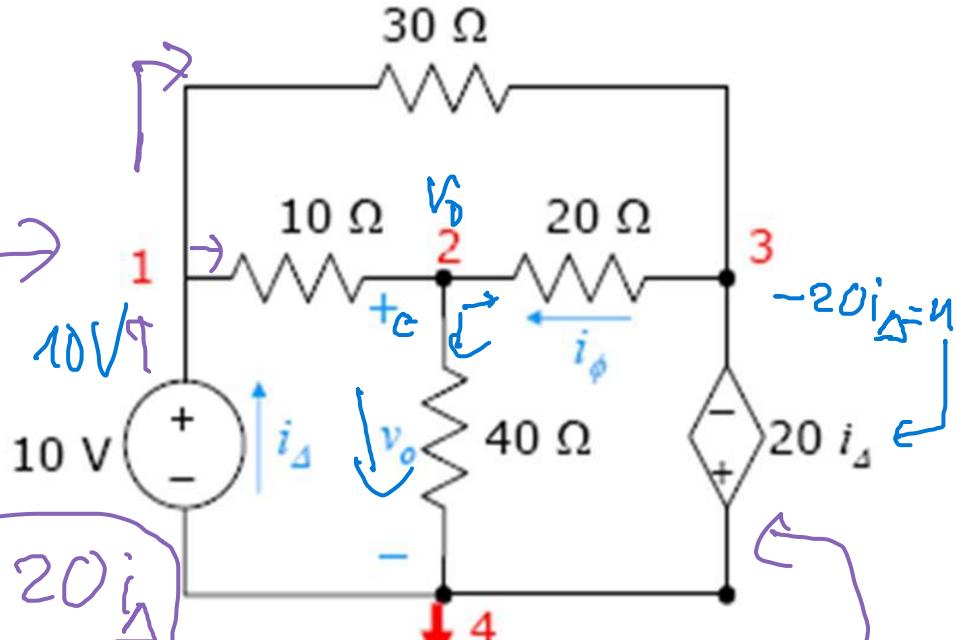2)

$$\frac{v_o - 10}{10} + \frac{v_o}{40} + \frac{v_o + 20i_\Delta}{20} = 0$$

$$i_\Delta = i_1 + i_2 = \frac{10 - v_o}{10} + \frac{10 + 20i_\Delta}{30}$$



$$0 - V_3 = 20i_\Delta$$

$$v_o = 24 \text{ V}$$

$$i_\Delta = -3.2 \text{ A}$$

Assessing Objective 3

v_1 at node 2

Use the node-voltage method to find i_ϕ .


Ans.: -

$$2) \quad \frac{v_1 - 60}{2} + \frac{v_1}{24} + \frac{v_1 - 6i_\phi - 60}{3} = 0$$

$$b) \quad i_\phi = \frac{6i_\phi + 60 - v_1}{3} \quad \approx \frac{v_3 - v_2}{3}$$

$$v_1 = 48 \text{ V}$$

$$i_\phi = -4 \text{ A}$$

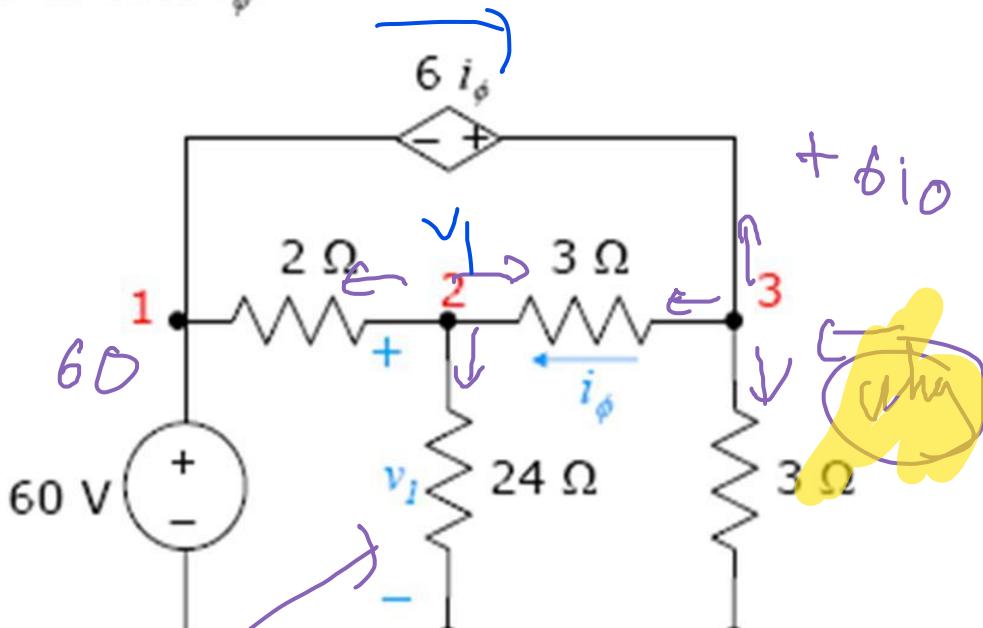


$$\frac{v_3 - v_2}{3} + \frac{v_3 - v_4}{3} + \frac{v_1 - 60}{2} + \frac{v_1 - 6i_\phi - 60}{3} = 0$$

Problem 5

Use the node-voltage method to find v_3 and i_ϕ .

Ans.: -

Equivalent

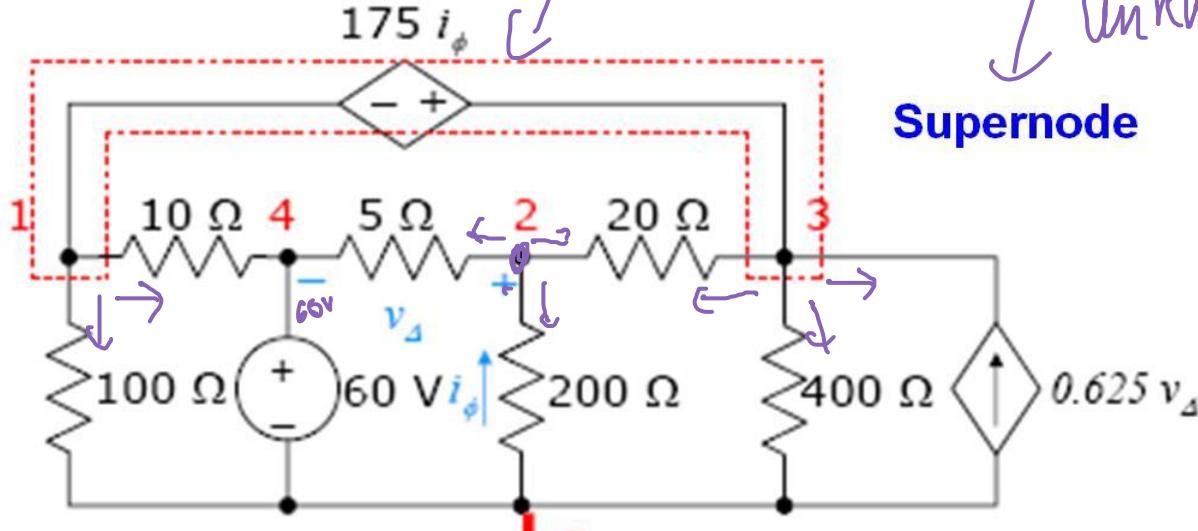

$$1,3) \frac{v_1 - 60}{10} + \frac{v_1}{100} - 0.625v_\Delta + \frac{v_3}{400} + \frac{v_3 - v_2}{20} = 0$$

$$2) \frac{v_2 - 60}{5} + \frac{v_2}{200} + \frac{v_2 - v_3}{20} = 0$$

$$i_\phi = \frac{-v_2}{200}$$

$$v_\Delta = v_2 - 60$$

$$v_3 = v_1 + 175i_\phi$$

$v_3 - v_1 = 175i_\phi$

connect with 2 nodes

Unknown

$$\begin{cases} v_1 = -60.75 \text{ V} \\ v_2 = 30 \text{ V} \\ v_3 = -87 \text{ V} \\ i_\phi = -0.15 \text{ A} \\ v_\Delta = -30 \text{ V} \end{cases}$$

Hết nha ✓


Introduction to Mesh-Current Method

- Applicable only to planar circuits.
- Describe a circuit in terms of $b_e - (n_e - 1)$ equations.

$b_e = 7$ Numbers of Essential branches

$n_e = 4$ Numbers of Essential nodes

$$b_e - (n_e - 1) = 7 - (4 - 1) = 4$$

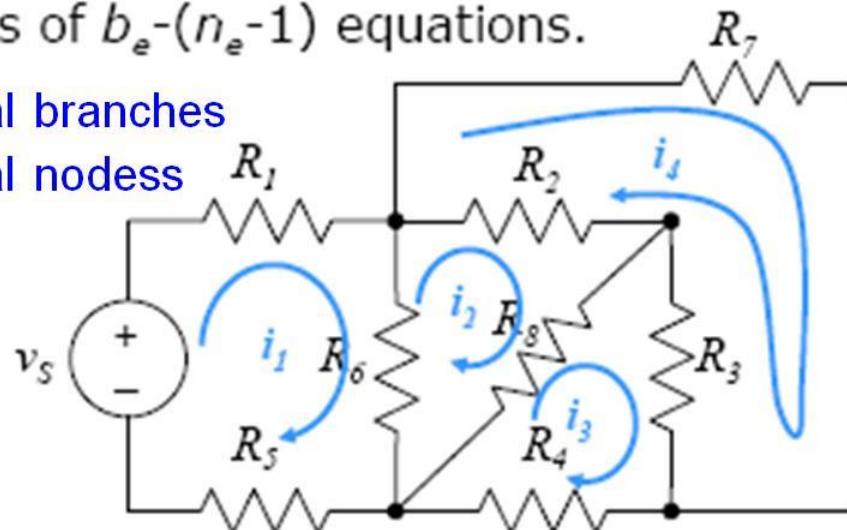


- A **mesh current** is the current that exists only in the perimeter of a mesh.

A mesh is a loop that does not enclose any other loops

Introduction to Mesh-Current Method

$$-v_1 + i_a R_1 + (i_a - i_b) R_3 = 0$$


$$(i_b - i_a) R_3 + i_b R_2 + v_2 = 0$$

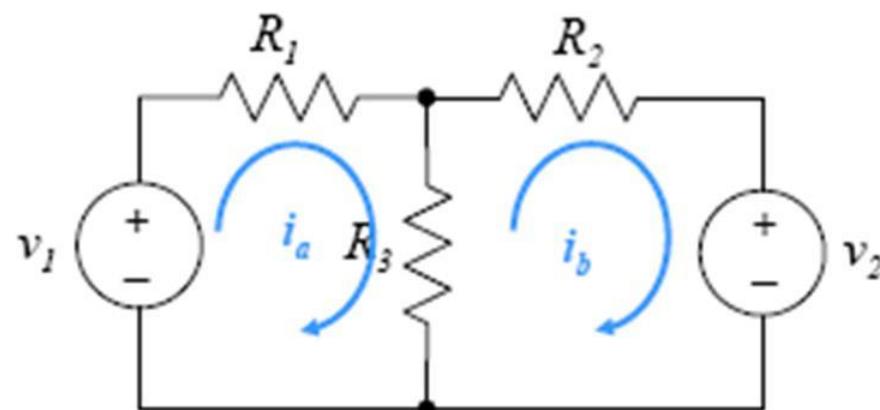

$$i_1 = i_a$$

$$i_2 = i_b$$

$$i_1 = i_2 + i_3$$

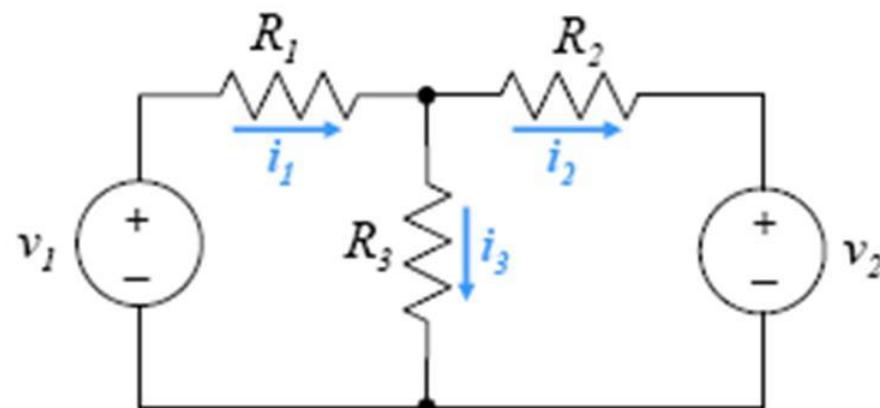

Example 2



Find v_o ?

Ans.:-

$$-40 + i_a 2 + (i_a - i_b)8 = 0$$

$$(i_b - i_a)8 + i_b 6 + (i_b - i_c)6 = 0$$

$$(i_c - i_b)6 + i_c 4 + 20 = 0$$

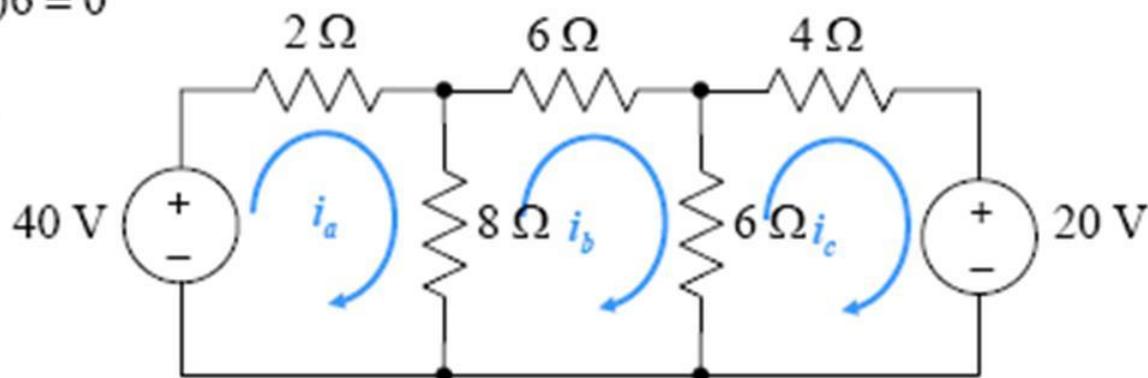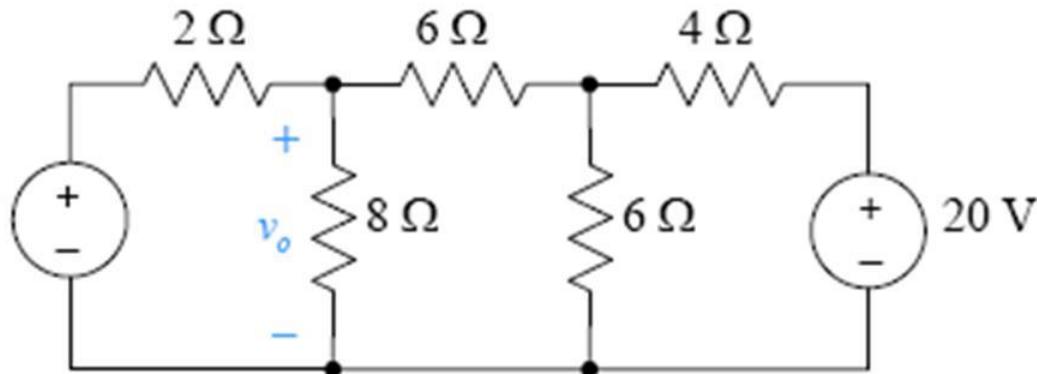

$$\begin{bmatrix} 10 & -8 & 0 \\ -8 & 20 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ -20 \end{bmatrix}$$

↗ $i_a = 5.6 \text{ A}$
 $i_b = 2.0 \text{ A}$
 $i_c = -0.8 \text{ A}$

Assessing Objective 4


- Power delivered by the 80 V source and power dissipated in the 8 Ω resistor.

Ans.: -

$$-80 + (i_a - i_c)5 + (i_a - i_b)26 = 0$$

$$(i_b - i_a)26 + (i_b - i_c)90 + i_b 8 = 0$$
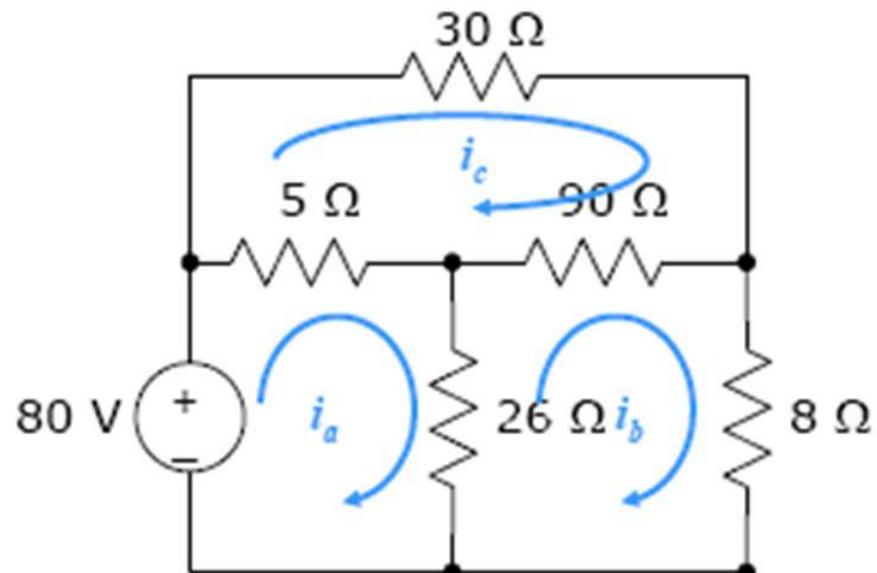
$$(i_c - i_a)5 + i_c 30 + (i_c - i_b)90 = 0$$



$$\begin{bmatrix} 31 & -26 & -5 \\ -26 & 124 & -90 \\ -5 & -90 & 125 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 80 \\ 0 \\ 0 \end{bmatrix}$$



$$\begin{aligned} i_a &= 5.0 \text{ A} \\ i_b &= 2.5 \text{ A} \\ i_c &= 2.0 \text{ A} \end{aligned}$$



$$\begin{aligned} P_{80V} &= 400 \text{ W} \\ P_{8\Omega} &= 50 \text{ W} \end{aligned}$$

Mesh-current method and dependent sources

Find i_ϕ ?

Ans.:-


$$-50 + (i_a - i_c)5 + (i_a - i_b)20 = 0$$

$$(i_b - i_a)20 + (i_b - i_c)4 + 15i_\phi = 0$$

$$(i_c - i_a)5 + i_c + (i_c - i_b)4 = 0$$

$$i_\phi = i_a - i_b$$
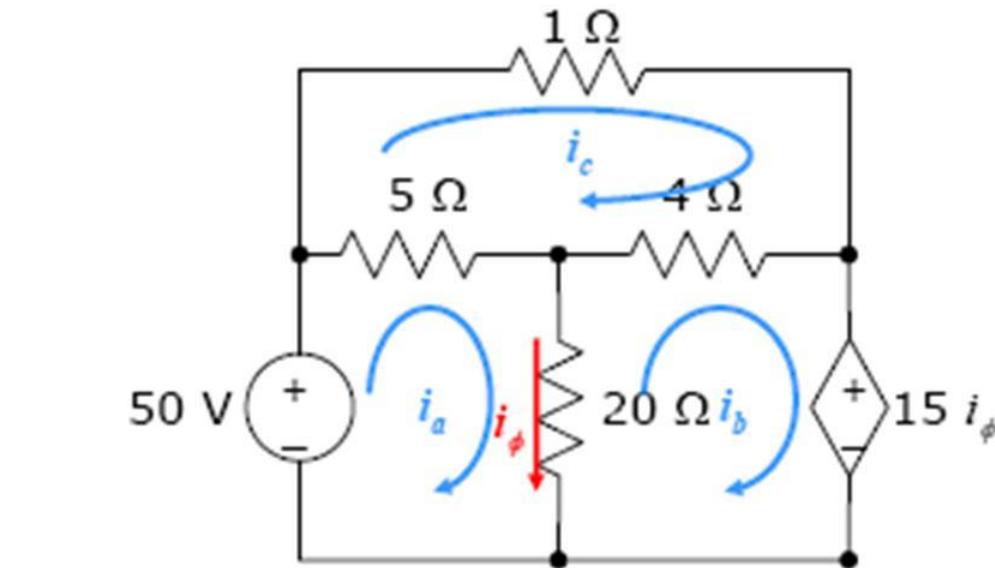
$$\begin{bmatrix} 25 & -20 & -5 \\ -5 & 9 & -4 \\ -5 & -4 & 10 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$



$$i_a = 29.6 \text{ A}$$

$$i_b = 28.0 \text{ A}$$

$$i_c = 26.0 \text{ A}$$

$$i_\phi = 1.6 \text{ A}$$

Assessing Objective 5

Find i_ϕ ?

Ans.: -

$$-25 + (i_a - i_c)2 + (i_a - i_b)5 + 10 = 0$$

$$-10 + (i_b - i_a)5 + (i_b - i_c)3 + i_b = 0$$

$$(i_c - i_a)2 + 3v_\phi + i_c 14 + (i_c - i_b)3 = 0$$

$$v_\phi = (i_b - i_c)3 \rightarrow \text{any direct output}$$

$$\begin{bmatrix} 7 & -5 & -2 \\ -5 & 9 & -3 \\ -2 & 6 & 10 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 15 \\ 10 \\ 0 \end{bmatrix}$$




$$i_a = 4 \text{ A}$$

$$i_b = 3 \text{ A}$$

$$i_c = -1 \text{ A}$$



$$i_\phi = 1 \text{ A}$$

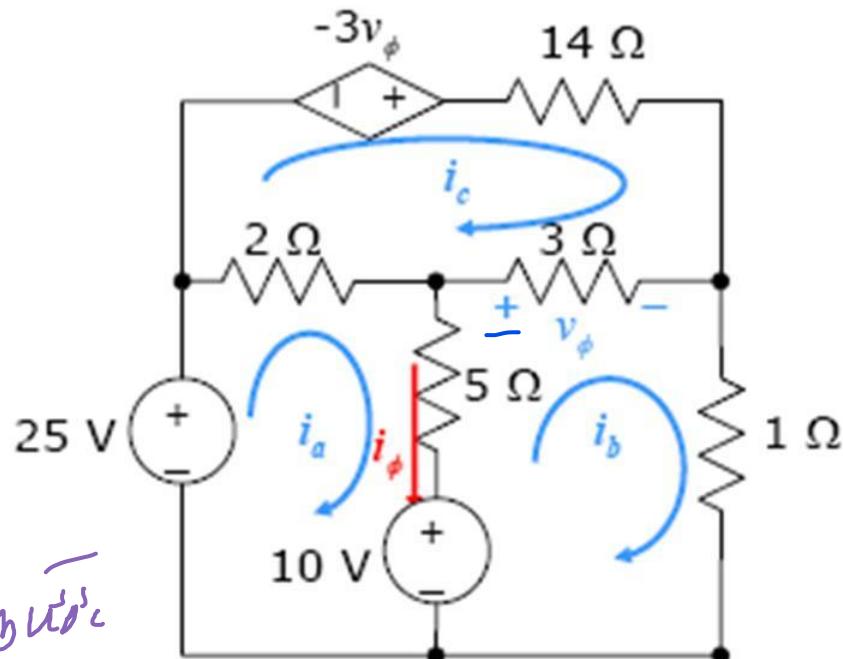

Special Cases

- When an independent source is connected between two essential nodes.

a) $-100 + (i_a - i_b)3 + v + i_a 6 = 0$

b) $(i_b - i_a)3 + i_b 10 + (i_b - i_c)2 = 0$

c) $-v + (i_c - i_b)2 + 50 + i_c 4 = 0$

$$i_c - i_a = 5$$


a) + c) (Cancelling v)

$$-100 + (i_a - i_b)3 + i_a 6 + (i_c - i_b)2 + 50 + i_c 4 = 0$$

$$\begin{aligned} 9i_a - 5i_b + 6i_c &= 50 \\ -3i_a + 15i_b - 2i_c &= 0 \\ -i_a + 0i_b + i_c &= 5 \end{aligned}$$

$$\Rightarrow \begin{bmatrix} 9 & -5 & 6 \\ -3 & 15 & -2 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}$$

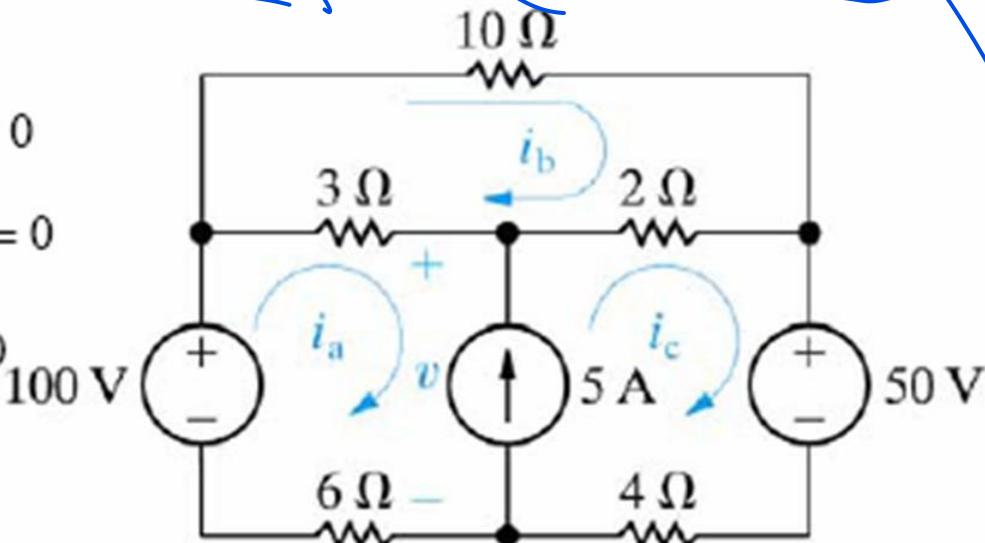
$$\begin{aligned} i_a &= 1.75 \text{ A} \\ i_b &= 1.25 \text{ A} \\ i_c &= 6.75 \text{ A} \end{aligned}$$



Special Cases

- Supermesh

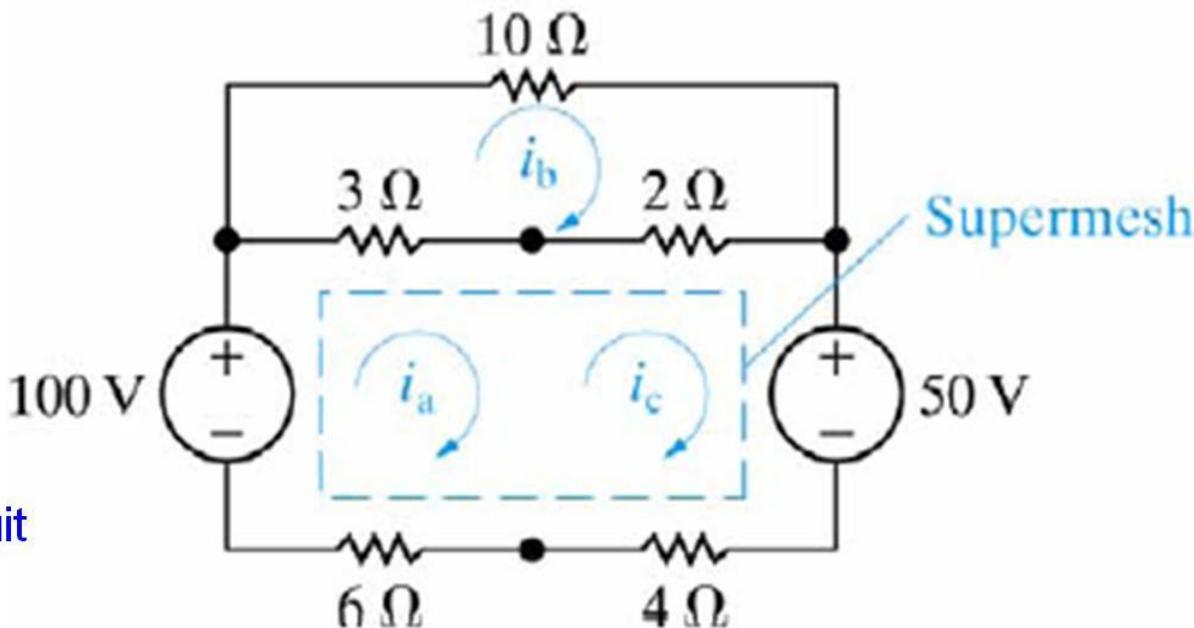Remove the current source from the circuit




$$-100 + (i_a - i_b)3 + i_a 6 + (i_c - i_b)2 + 50 + i_c 4 = 0$$

Assessing Objective 6

- Find the power dissipated in the $2\ \Omega$ resistor.

Ans.:-

No ~~S/R~~ resistor

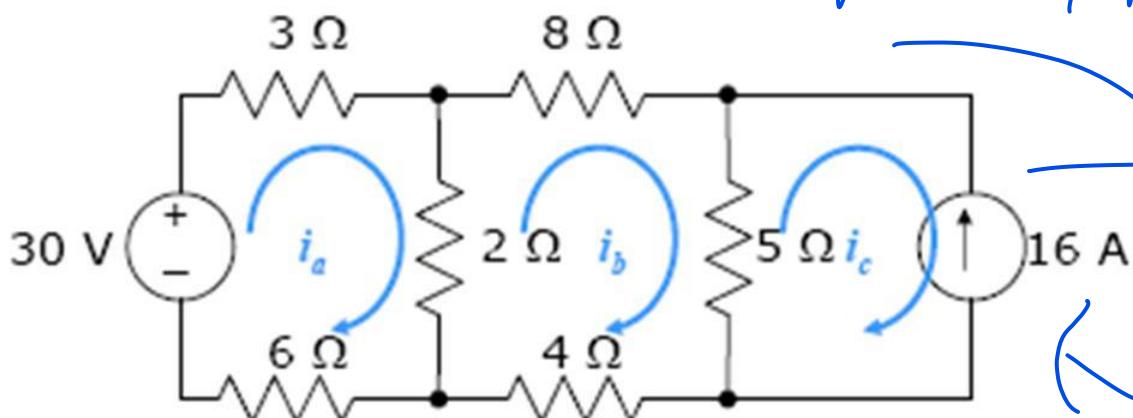

$$-30 + i_a 3 + (i_a - i_b) 2 + i_a 6 = 0$$

$$(i_b - i_a) 2 + i_b 8 + (i_b - i_c) 5 + i_b 4 = 0$$

$$\boxed{i_c = -16 \text{ A}}$$

$$\Rightarrow i_a = 2 \text{ A}$$

$$i_b = -4 \text{ A}$$

$$P_{2\Omega} = 6^2 2 = 72 \text{ W}$$

Assessing Objective 7

- Find the current i_a .

Ans.: -

$$-75 + (i_a - i_b)2 + (i_a - i_c)5 = 0$$


$$\begin{cases} i_b = -10 \text{ A} \\ v_\phi = (i_a - i_c)5 \end{cases}$$

$$i_c = \frac{2v_\phi}{5}$$

$$i_a = 15 \text{ A}$$

$$i_c = 10 \text{ A}$$

$$v_\phi = 25 \text{ V}$$

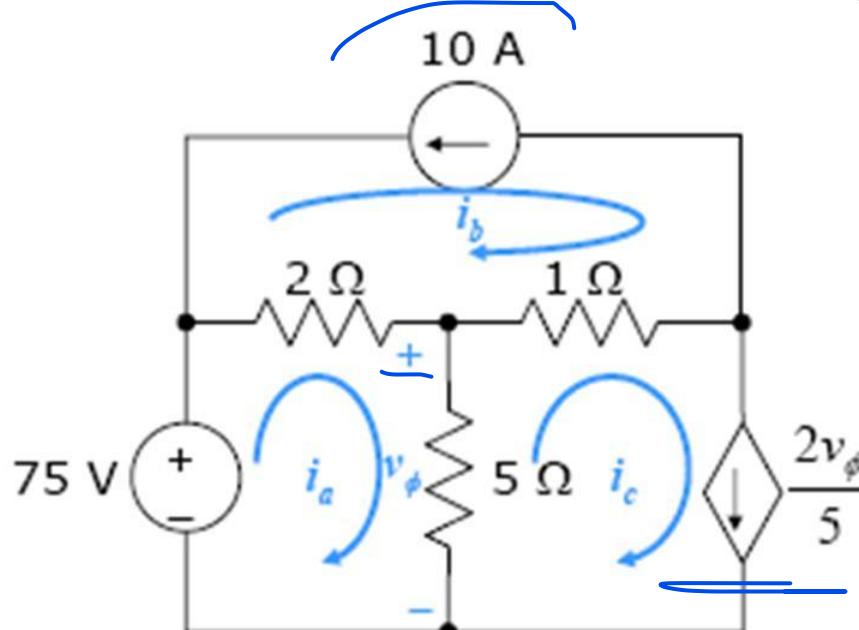


Compute i_c in terms of i_a and substitute into above equation

Assessing Objective 8


- Find the power dissipated in the $1\ \Omega$ resistor.

Ans.: -

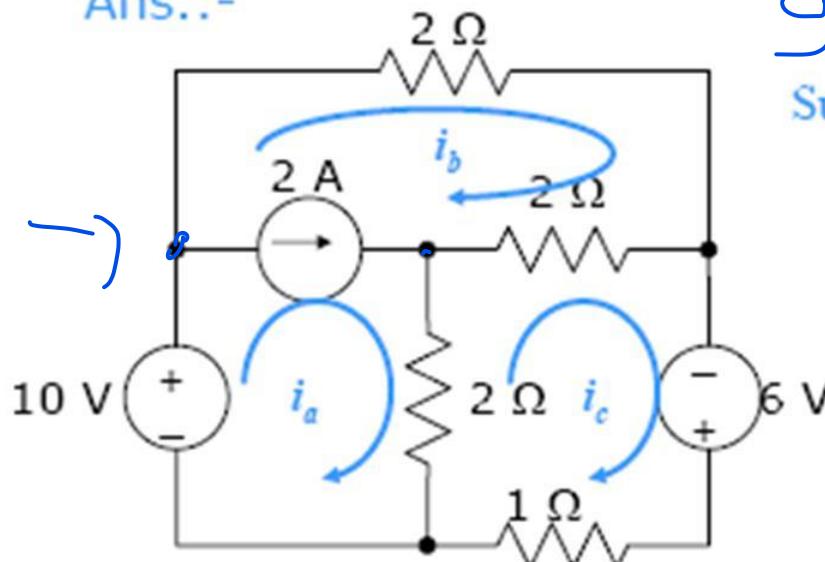

Solve between 2 es notes

Supermesh

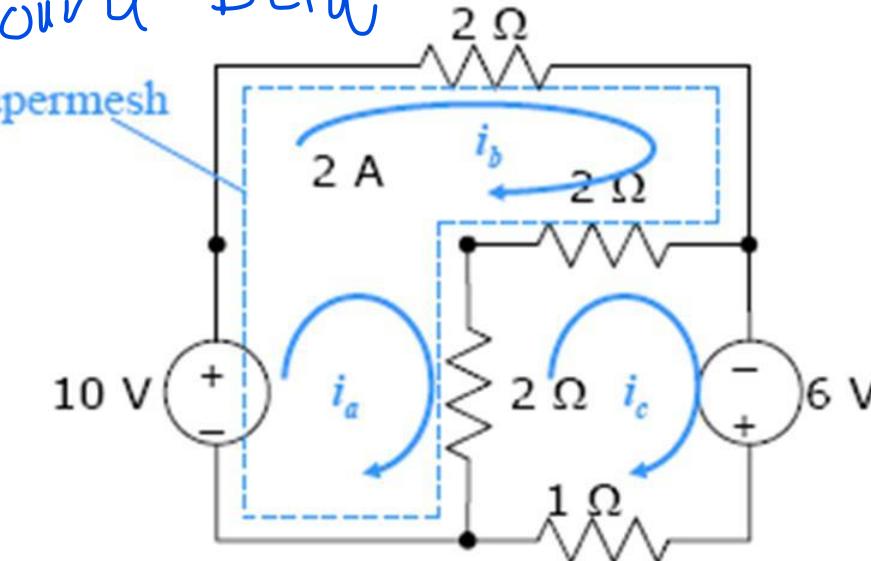

$$-10 + i_b 2 + (i_b - i_c)2 + (i_a - i_c)2 = 0$$

$$(i_c - i_a)2 + (i_c - i_b)2 - 6 + i_c = 0$$

$$i_a - i_b = 2$$

$$i_a = 7 \text{ A}$$


$$i_b = 5 \text{ A}$$

$$i_c = 6 \text{ A}$$

$$P_{2\Omega} = 6^2 1 = 36 \text{ W}$$

Node voltage method vs. Mesh current method




Which method is more efficient?

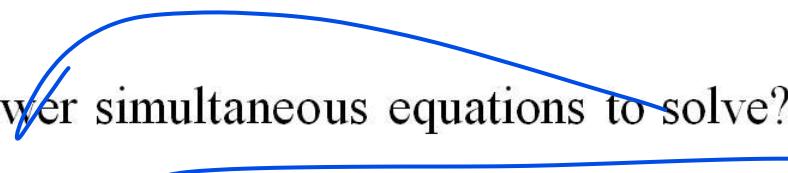- ❖ Does one of the methods result in fewer simultaneous equations to solve?

- ❖ Does the circuit contain supernodes?
If so, use the **node-voltage method**.
- ❖ Does the circuit contain supermeshes?
If so, use the **mesh-current method**.

Example 3

Find the power dissipated in the 300Ω resistor?

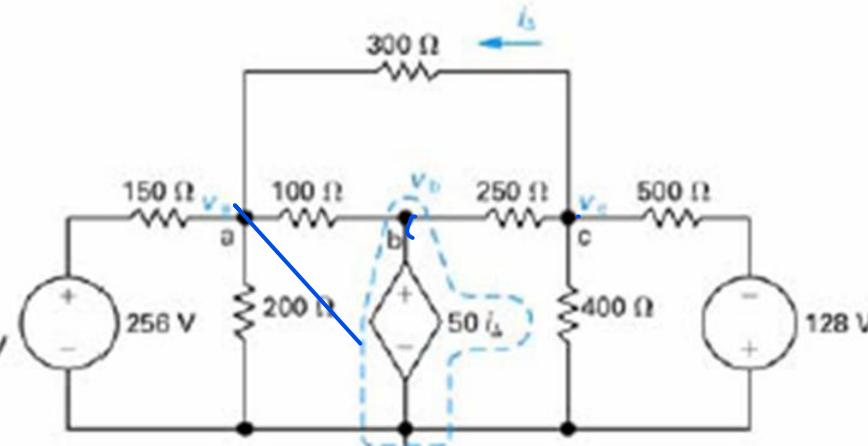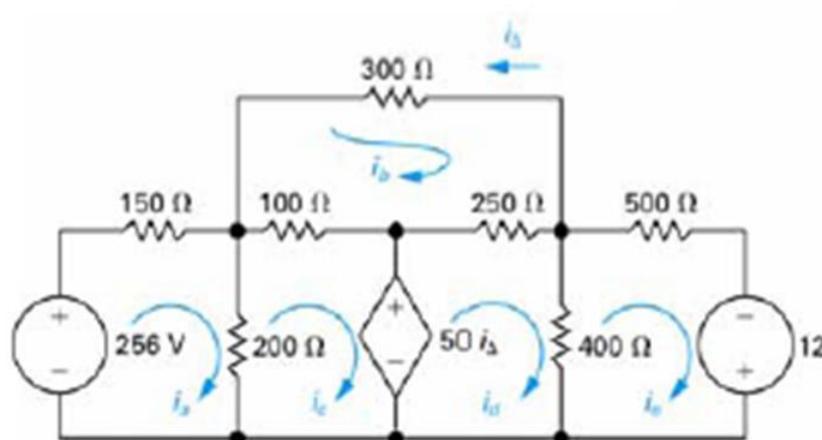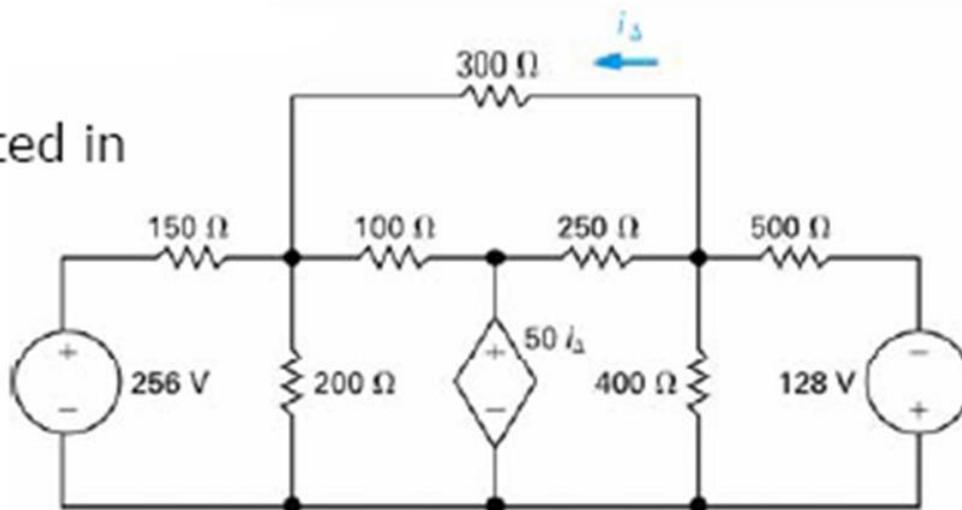
Ans.: -



Mesh current equations = 5

Node voltage equations = 3

Example (Cont.)

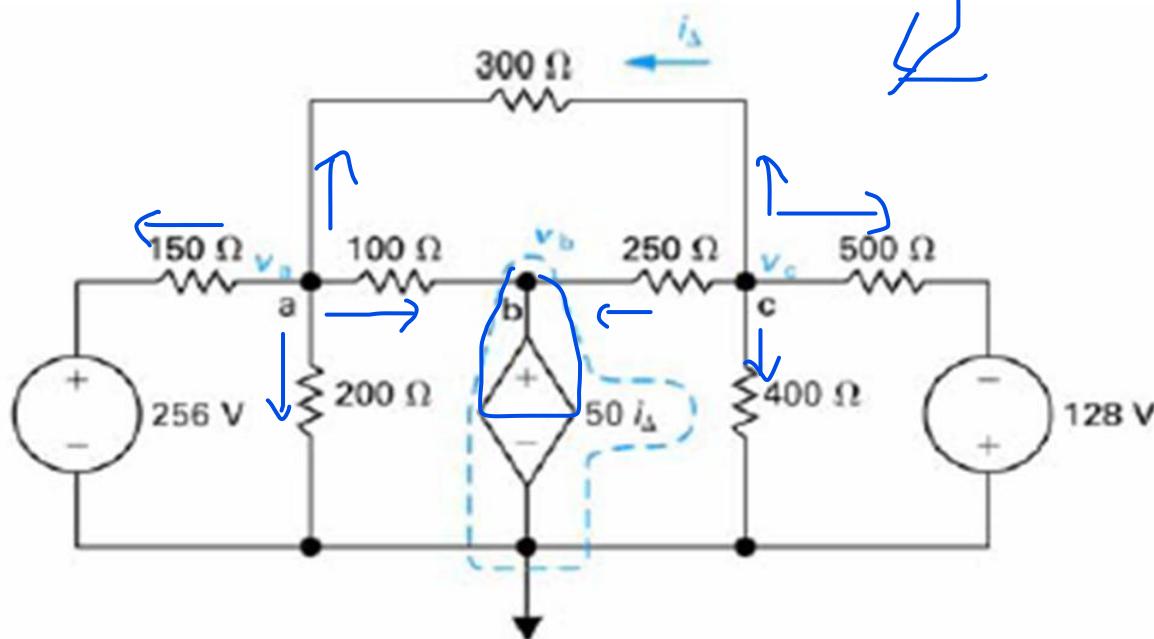

a) $\frac{v_a - 256}{150} + \frac{v_a}{200} + \frac{v_a - v_c}{300} + \frac{v_a - v_b}{100} = 0$




c) $\frac{v_c + 128}{500} + \frac{v_c}{400} + \frac{v_c - v_b}{250} + \frac{v_c - v_a}{300} = 0$

$v_b = 50i_\Delta$

Example 4

Find v_o ?


Ans.: -

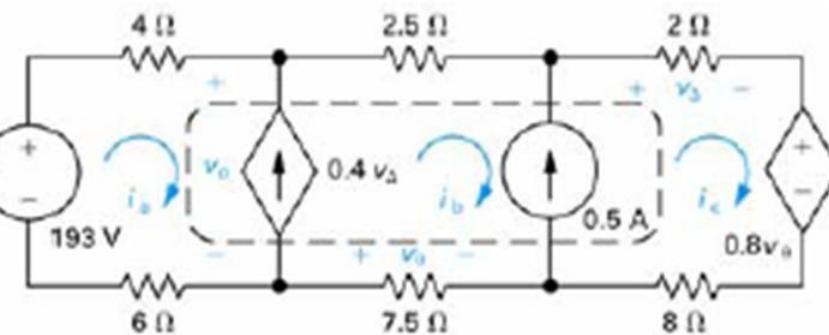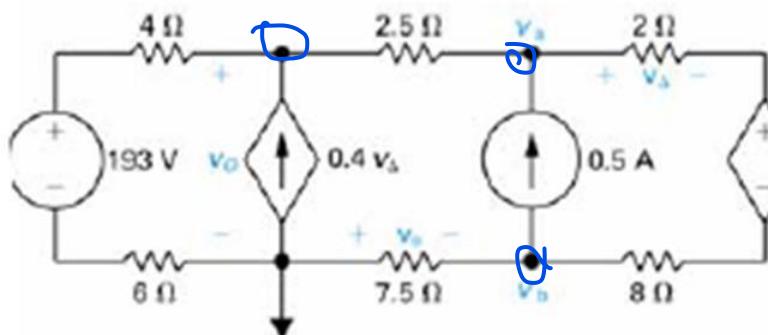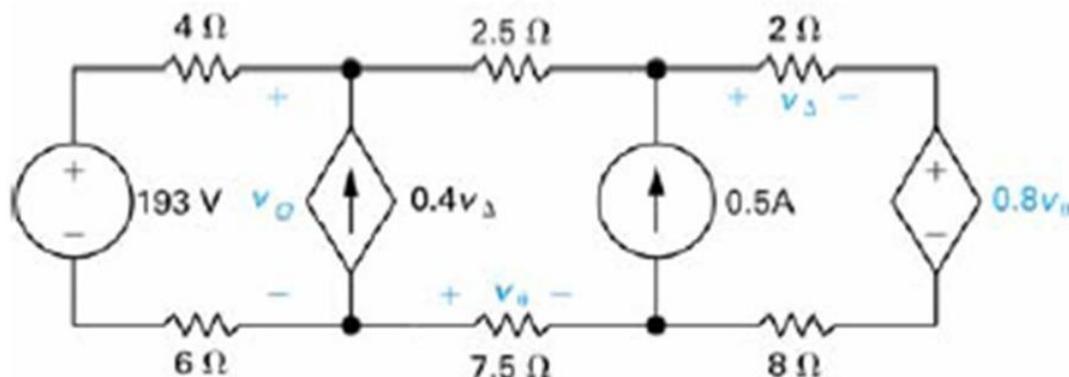

Node voltage equations = 3

Mesh current equations = 1

Example (Cont.)

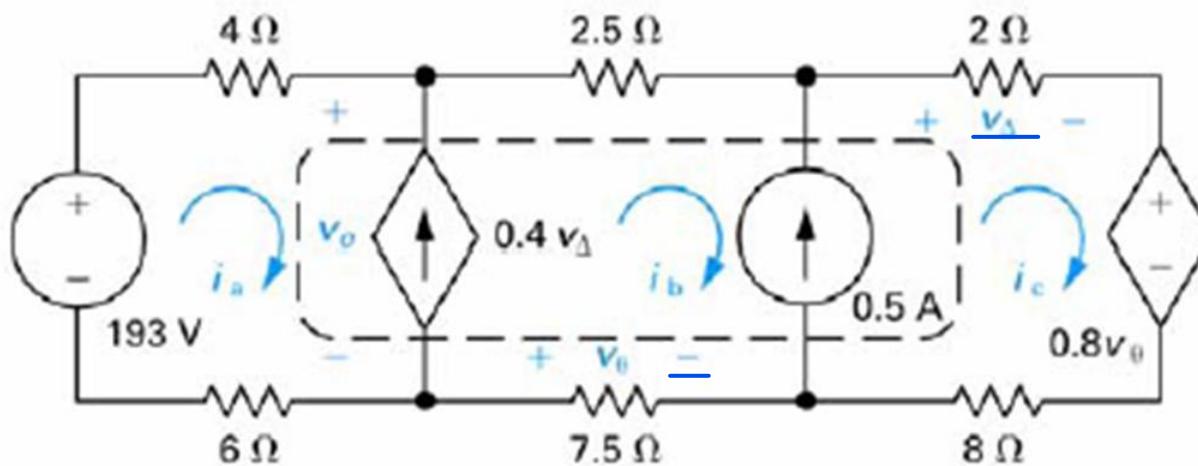

$$-193 + i_a 4 + i_b 2.5 + i_c 2 + 0.8v_\theta + i_c 8 + i_b 7.5 + i_a 6 = 0$$

$$\left. \begin{array}{l} i_b - i_a = 0.4v_\Delta \\ i_c - i_b = 0.5 \end{array} \right\}$$

$$\left. \begin{array}{l} v_\Delta = i_c 2 \\ v_\theta = -i_b 7.5 \end{array} \right\}$$

Ωm

$i_a = 2 \text{ A}$

Ans