

$$v_s(t) = 10 \angle 0^\circ$$


$$v_s(t) = 100 \angle -90^\circ$$

$$N = 50000 \text{ rad/s}$$


$$\bar{Z}_c = \frac{-j20}{g}$$

$$\bar{V} = 31.62 \angle -71.57^\circ$$
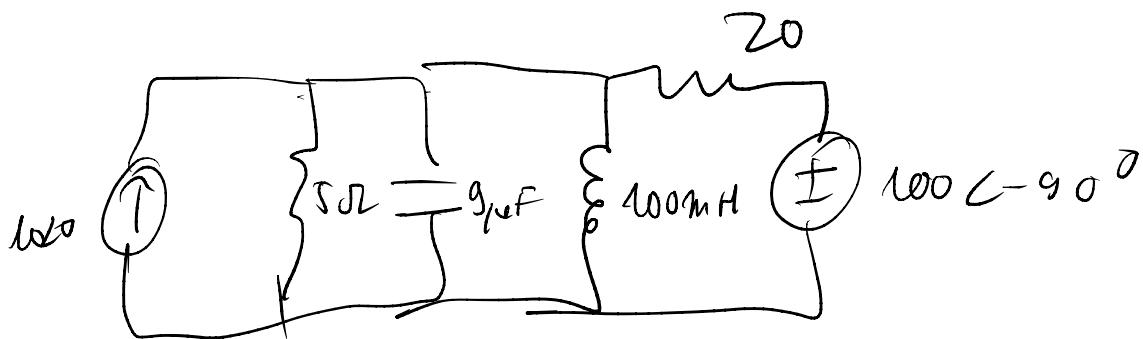
$$v(t) = 31.62 \cos(5000t - 71.57^\circ) \text{ V.}$$



$$N = 50000 \text{ rad/s}$$

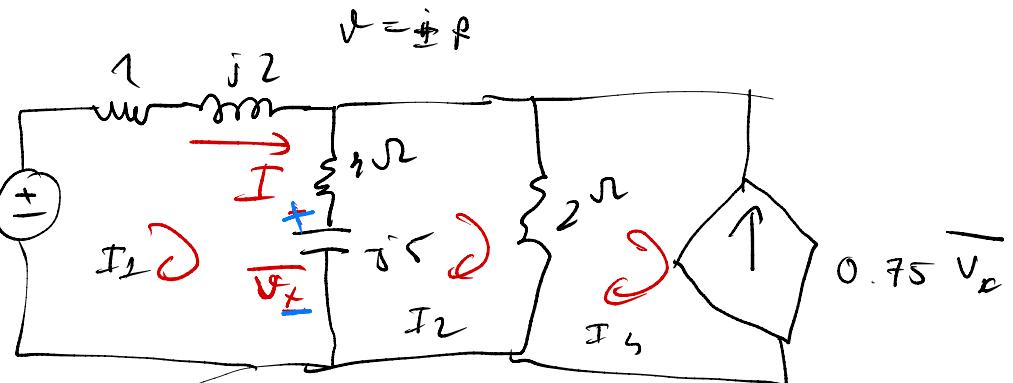

$$I_3 = 0.75 \bar{V}_x, \bar{V}_x = (-j5)(I_1 - I_2)$$

$$= - (0.75(-j5)(I_1 - I_2))$$

$$\text{Loop 1: } -33.8 \angle 0 + I_1(1 + j2) + (3 - j5)(I_1 - j)$$

$$= I_1(1 + j2 + 3 - j5) + I_2(j5 - 3) = 33.8 \angle 0$$


$$= I_1(4 - j3) + I_2(j5 - 3) = 33.8 \angle 0$$

$$\text{Loop 2: } (3 - j5)(I_2 - I_1) + 2(I_2 - V_x) = 0$$

=

$$\bar{I} = I_1 = 23.07 \angle 3.95^\circ$$

Question 3:

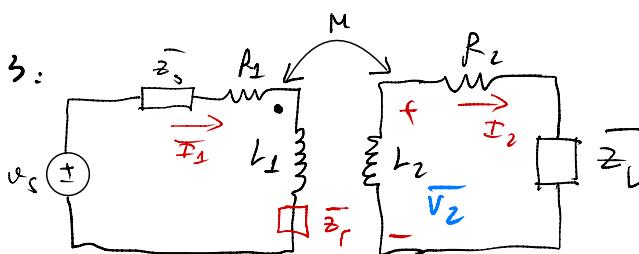

Z_L = 360 Ω in series with 0.25 H

$$\bar{z}_s = 18 \text{ m} \text{, } v_g = 245 \cdot 2 \cos(800t) \text{ (V)}$$

$$R_f = 100 \Omega, L_f = 0.5 \text{ H} \quad \text{and} \quad L_2 = 0.125 \text{ H}$$

$$R_2 = 40 \Omega, \quad k = 0.5$$

a) Find \bar{z} reflected 1

$$\text{b) } \overline{I_1} = ? \quad , \quad \overline{I_2} = ?$$

$$\bar{z}_L = 360 + j 800 \times 0.25$$

$$\bar{z}_{11} = \bar{z}_S + R_1 + jwL_1 =$$

$$\bar{Z}_{\text{eff}} = R_2 + j\omega L_2 + \bar{Z}_L = 400 + j 300 \text{ } (\Omega)$$

$$a) \quad \bar{z}_1 = \frac{(wM)^2}{1 \bar{z}_{22} \mid^2} \quad \bar{z}_{22}^* = 10.24 - j7.68 \text{ (52)}$$


$$b) \quad \overline{f_1} = \frac{\overline{v_8}}{\overline{z_{11}} + \overline{z_r}} = \frac{245 \cdot 220}{\overline{z_{11}} + \overline{z_r}} = 0,5 \angle -83,13^\circ$$

$$\Rightarrow i_1(+) = 0.5 \cos(800t - 53.13^\circ) \text{ (A)}$$

$$I_2 = \frac{\overline{V_2}}{R_2 + \overline{Z}_L} = \frac{j \omega N \overline{I_1}}{R_2 + \overline{Z}_L} = 0.08 \angle 0^\circ$$


$$\Rightarrow i_2(t) = 0.08 \cos(80\pi t)$$
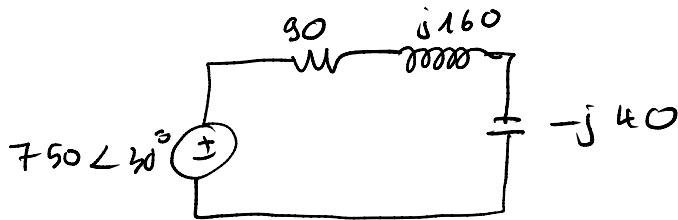
$$v_s = 750 \cos(5000t + 30^\circ) \text{ V}$$



$$Z_{\text{total}} = 90 + j120$$
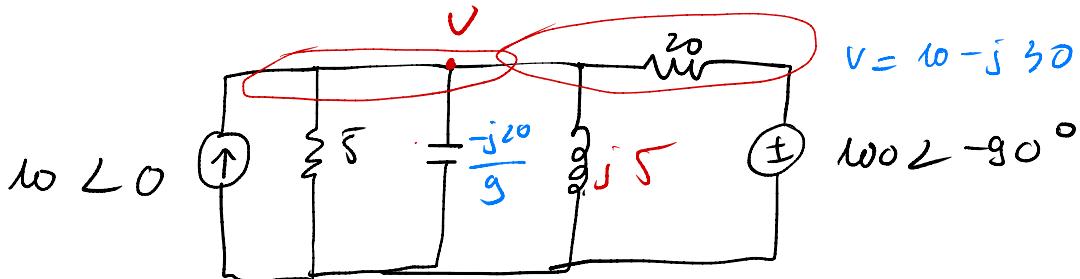
$$\rightarrow I_s = \frac{750 \angle 30^\circ}{90 + j120} = 5 \angle -2.34^\circ$$



$$i_s(t) = 10 \cos \omega t, v_c(t) = 100 \sin \omega t, \omega = 50 \text{ rad/s}$$

$$\text{Node-Voltage: } \frac{\bar{V}}{-j\frac{10}{5}} + \frac{\bar{V}}{5} + \frac{\bar{V}}{j5} + \frac{\bar{V} - 100 \angle -90^\circ}{20} = 10$$

$$\Rightarrow \bar{V} \left(j\frac{9}{20} + \frac{1}{5} - \frac{j}{5} + \frac{1}{20} \right) = 10 - j5$$

$$\Rightarrow \bar{V} \left(0.25 + j0.25 \right) = 10 - j5$$

$$\Rightarrow \bar{V} = 10 - j5 = 31.62 \angle -71.56^\circ$$

$$100 \times 10^{-6} \times 10^3 \times 5000$$

$$Z_L = 100 \text{ mH} = 100 \times 10^{-6} \times 50 \times 10^3 j$$

$$= j5 \quad ? ? ?$$

