

• Complex numbers:

$$j^2 = -1$$

$$n = a + jb$$

↓ Real ↓ Imaginary

$$n = c e^{j\theta} = c \angle \theta^\circ$$

c: amplitude (radius)

θ : phase angle $= \tan^{-1} \frac{b}{a}$

Euler's formula: $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

$$n = 5 e^{j\frac{\pi}{4}} = 5 \angle \frac{\pi}{4} = 5 (\cos \frac{\pi}{4} + j \sin \frac{\pi}{4})$$


$$= \frac{5\sqrt{2}}{2} + \frac{5\sqrt{2}}{2} j$$

$$1 \angle 0^\circ, -1 = 1 \angle \pm 180^\circ, j = 1 \angle 90^\circ$$

\downarrow
 $\cos \theta + j \sin \theta$

$$\cos \frac{\pi}{2} + j \sin \frac{\pi}{2}$$

$$-j = 1 \angle -90^\circ$$

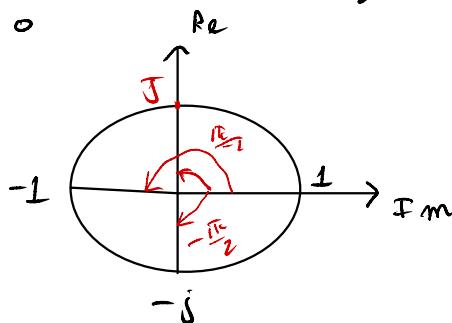

{ Addition \rightarrow Rectangular form
Subtraction


{ Multiplication: $n_1 n_2 = c_1 c_2 \angle (\theta_1 + \theta_2)$
Division: $= \frac{c_1}{c_2} \angle (\theta_1 - \theta_2)$

$$\sqrt{c e^{j\theta}} = \sqrt{c} [e^{j\theta}]^{\frac{1}{2}} = \sqrt{c} e^{j\frac{\theta}{2}} = \sqrt{c} \angle \frac{\theta}{2}$$

Fourier Series:

Sine + Cose
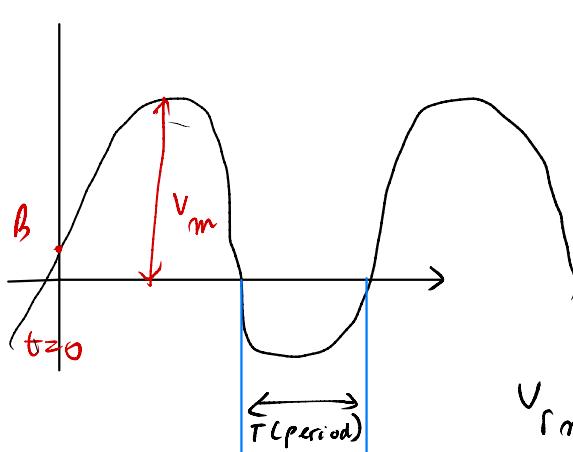
$$v = V_m \cos(\omega t + \phi) \text{ (v)}$$



$$\omega = \frac{2\pi}{T} = 2\pi f$$

Angular fre
Radian fre


phase angle

$$B = V_m \cos \theta \Rightarrow \theta = \cos^{-1} \frac{B}{V_m}$$

V_{rms} (root mean square)

: Điện áp hiệu dụng
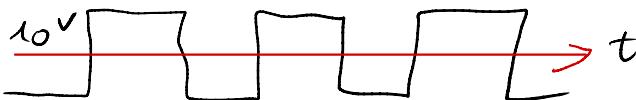
$$= 220 \text{ V in VN} = \frac{V_m}{\sqrt{2}}$$



Phase Lead or Lag :

$\theta_1 - \theta_2 = 0 \rightarrow v_1(+)$ and $v_2(+)$ are in phase

$\theta_1 - \theta_2 \neq 0 \rightarrow$ " out of phase

$\left\{ \begin{array}{l} \theta_1 - \theta_2 > 0, v_1(+) \text{ leads } v_2(+) \text{ by } \theta_1 - \theta_2 \\ \theta_1 - \theta_2 < 0, " \text{ lags } " \text{ by } \theta_1 - \theta_2 \end{array} \right.$

$$\begin{aligned} \sin \omega t &= \cos(\omega t - 90^\circ) \\ -\sin \omega t &= \cos(\omega t + 90^\circ) \end{aligned}$$

$$Ex_1: i = I_m \cos(\omega t + \phi) \quad 20A \cos(10^3 \pi)$$

$$f = \frac{1}{T} = 10^3 \rightarrow \omega = 2\pi f \quad \text{cycles/period}$$

$$v = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10 - 90^\circ) \\ = 12 \cos(\omega t - 100^\circ)$$

phasor:

$$\text{Euler's: } e^{\pm j\theta} = \cos \theta \pm j \sin \theta \quad \begin{matrix} \text{Real} \\ \text{Imaginary} \end{matrix}$$

$$v(t) = V_m \cos(\omega t + \theta) \quad \text{Time Domain}$$

$$= \text{Re} \left\{ V_m e^{j(\omega t + \theta)} \right\}$$

$$= \text{Re} \left\{ \underbrace{V_m e^{j\theta}}_{\text{Phasor } \bar{V}} e^{j\omega t} \right\}$$

$$\text{Phasor } \bar{V} = V_m e^{j\theta} = V_m \angle \theta$$


$$\bar{V} = P \{ v(t) \} = V_m e^{j\theta} = V_m \angle \theta \quad (\text{phasor domain})$$

$$i = 6 \cos(100t + 45^\circ)$$

$$I = 6 \angle 45^\circ$$

$$\left| \begin{array}{l} \bar{V} = 10 \angle 30^\circ \\ v(t) = 10 \cos(200t + 30^\circ) \end{array} \right.$$

For time domain solving
(Complicated)

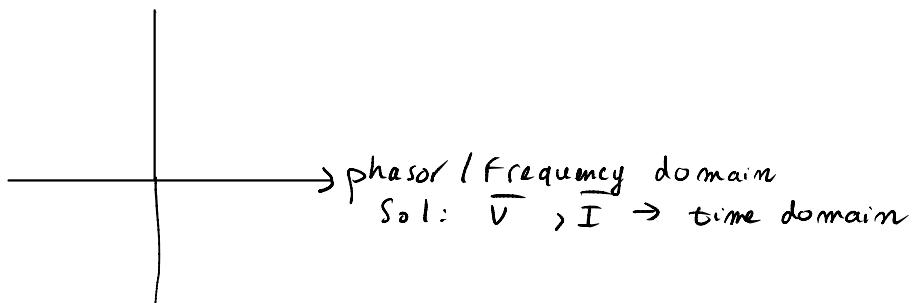

$$\begin{aligned}\bar{V} &= \int_0^t 8 e^{-j 20^\circ} dt = 8 e^{-j 20^\circ} \cdot 1 e^{j \frac{90}{2}} \\ &= 8 e^{j 70^\circ} \\ &= 8 \angle 70^\circ \\ &\quad \angle 45^\circ\end{aligned}$$

$$\begin{aligned}\text{Time Domain} \\ i = I_m \cos(\omega t + \theta_i) \quad A \quad \rightarrow \quad \text{Phasor Domain} \\ \bar{I} = I_m \angle \theta_i\end{aligned}$$


$$\begin{aligned}\theta = R_i = R I_m \cos(\omega t + \theta_i) \quad \rightarrow \quad \bar{V} = R I_m \angle \theta_i \\ \Rightarrow \bar{V} = R \bar{I}, \frac{\bar{V}}{\bar{I}} = R \angle 0^\circ \\ \rightarrow \angle \bar{V} - \angle \bar{I} = 0^\circ\end{aligned}$$

For Inductor (L)

$$\begin{aligned}\theta_L &= L \frac{di}{dt} = L \omega I_m \sin(\omega t + \theta_i) \\ &= -L \omega I_m \cos(\omega t + \theta_i - 90^\circ) \\ &= \operatorname{Re} \left\{ -L \omega I_m e^{j(\omega t + \theta_i - 90^\circ)} \right\} \\ \rightarrow \theta_L &= \operatorname{Re} \left\{ -L \omega I_m e^{j\theta_i} e^{-j90^\circ} e^{j\omega t} \right\} \\ &= \operatorname{Re} \left\{ j \omega L e^{j\theta_i} e^{j\omega t} \right\}\end{aligned}$$

Inductor:


phasor Domain
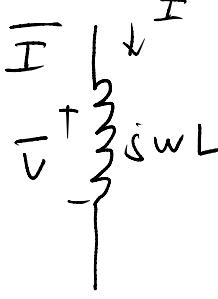
$$\text{Ref} \left\{ j\omega L e^{j\theta_i} e^{j\omega t} \right\} \rightarrow \bar{V} = j\omega L \bar{I}$$

$$\rightarrow \frac{\bar{V}}{\bar{I}} = j\omega L = \omega L \angle 90^\circ$$
$$v \pm \frac{1}{C} \angle \bar{V} - \angle \bar{I} = 90^\circ \text{ leads}$$


$$i = \frac{dv}{dt} \rightarrow \bar{V} = \frac{1}{j\omega C} \bar{I}$$

$$\frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C} = \frac{j}{\omega C} = \cancel{j} \frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$
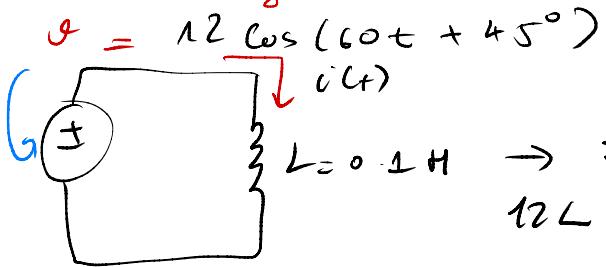
$$\angle \bar{V} - \angle \bar{I} = -90^\circ \text{ lag}$$



0.1 H

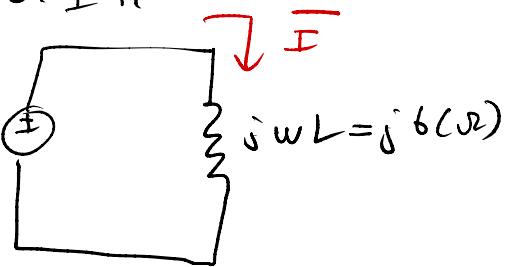

$$\bar{V} = 12 \angle 45^\circ$$

$$\bar{I} = \frac{\bar{V}}{j6} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ} = 2 \angle -45^\circ$$

$$i(t) = 2 \cos(60t - 45^\circ)$$

Solution

$$j6 = 1 \angle 90^\circ \cdot 6 = 6 \angle 0 + 90^\circ$$

Impedance

$$\underline{\underline{Z}} = \underline{\underline{5 \Omega}} + \underline{\underline{j 6 \Omega}}$$

$$\underline{\underline{Z}} = 5 + j 6 (\Omega)$$

\downarrow
Res \downarrow
Reactance

$$\underline{\underline{Y}} = \frac{1}{\underline{\underline{Z}}} = G + j B$$

\uparrow
admittance

Conductance

Subceptance

$$\underline{\underline{V}} = \underline{\underline{Z}} \underline{\underline{I}}$$

$\left. \begin{array}{l} \downarrow \\ \downarrow \\ \downarrow \end{array} \right\} j w L, w L > 0 \Rightarrow \text{inductive}$

$$\frac{1}{\underline{\underline{Y}}} = \frac{1}{j w C} = \frac{-j}{w C} \angle 0 \Rightarrow \text{capacitive}$$

top day

$$V_s = 10 \cos 4t$$

$$\frac{1}{jwC} = \frac{1}{jwC} - \frac{1}{j4.0 \cdot 1} = \frac{1}{j2.5} \text{ (s2)}$$

$$\frac{j-1}{j\sqrt{2.5}} = \frac{-j}{2.5}$$

4) Find \bar{I} $\bar{Z} = 5 + \frac{1}{j2.5}$

$$I = \frac{V_s}{Z} = \frac{10 \angle 0^\circ}{5 + j0.4 \angle -90^\circ} = 1.789 \angle 26.57^\circ$$

$$\sqrt{5^2 + 2.5^2} = 5.95$$

Ans

$$H = j\omega L$$

$$C = \frac{1}{j\omega C}$$

