

# Inductance, Capacitance and Mutual Inductance

---

Textbook:

**Electric Circuits**

James W. Nilsson & Susan A. Riedel


9th Edition.

## The inductor


Coil


Chia năng lượng dang từ

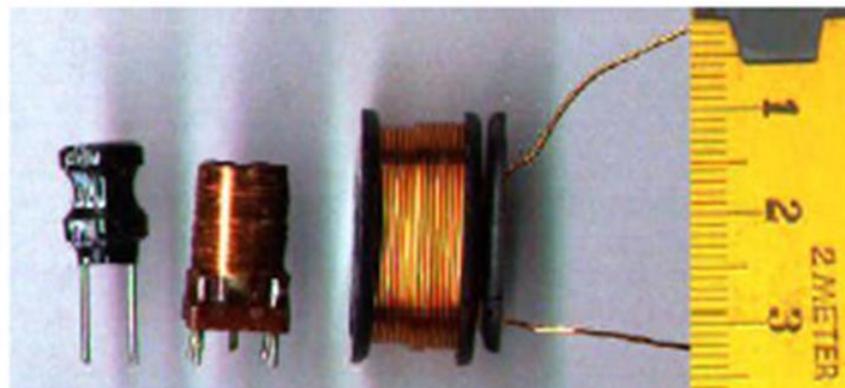- An **inductor** is a passive electrical device that stores energy in a magnetic field, typically by combining the effects of many loops of electric current.



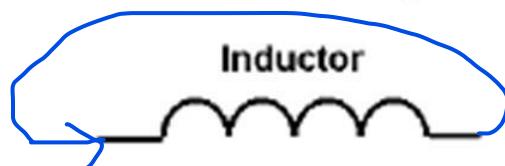
- The inductance is measured in **Henrys** (H) (It is named after the American scientist *Joseph Henry*).




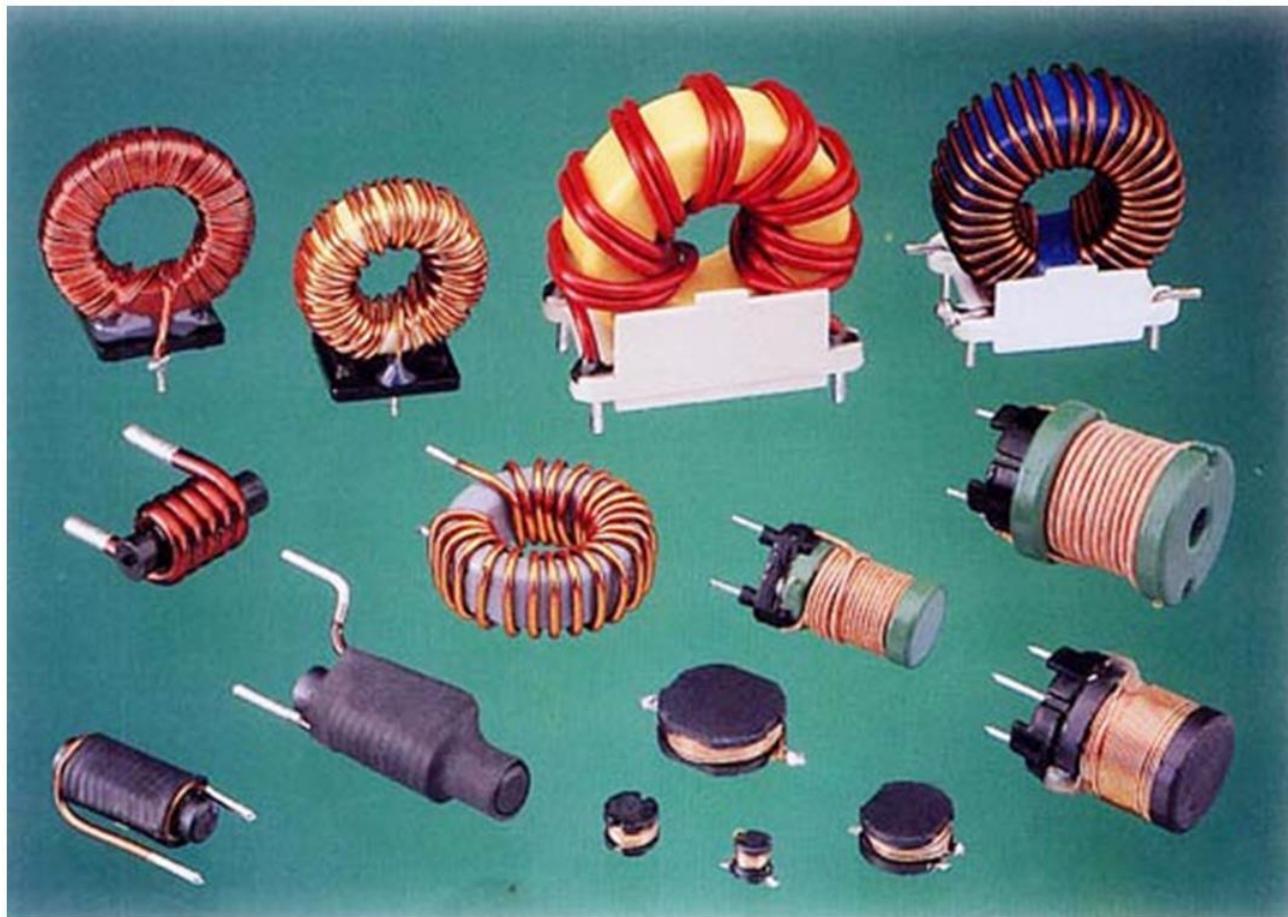


<http://en.wikipedia.org/wiki/Inductor>

Low to High power

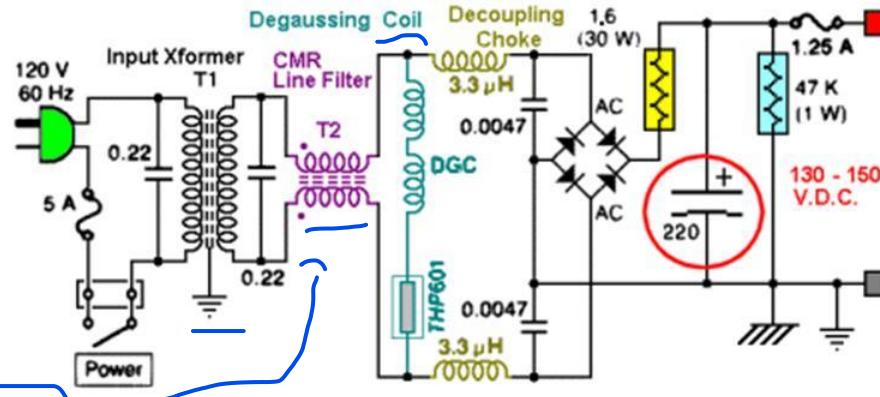


Line Filter

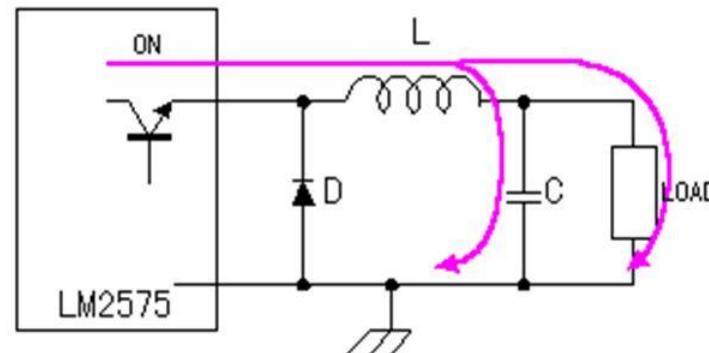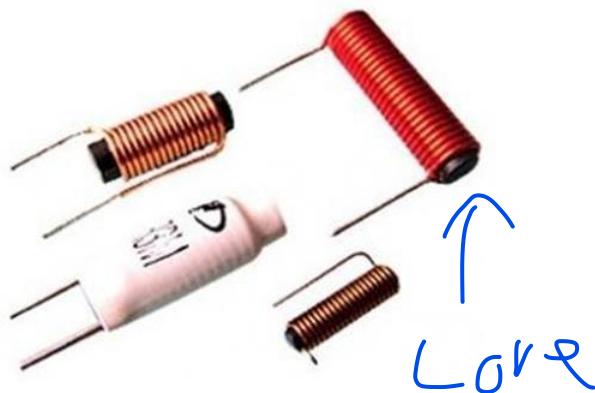


Power supply Filter


air core

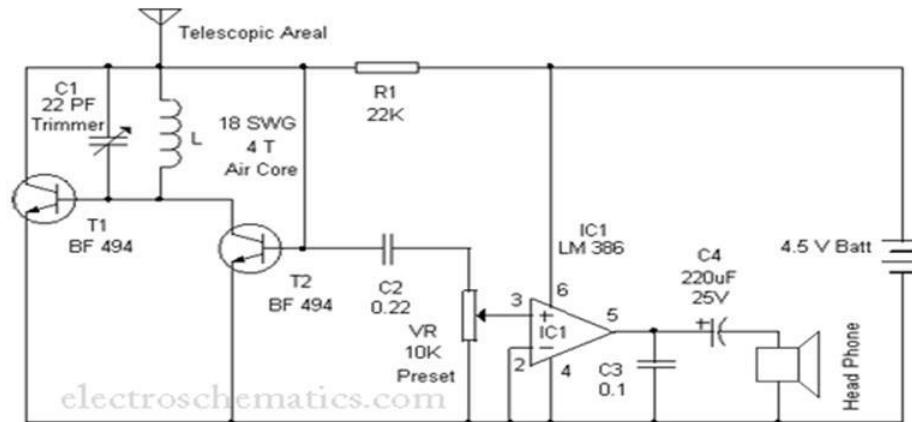


Air core coil in receiving circuit

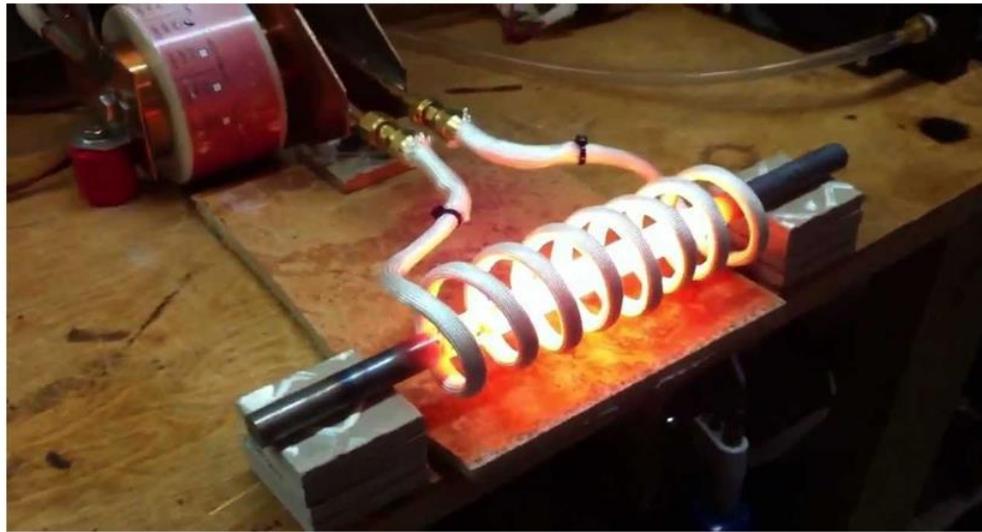

Induction heating

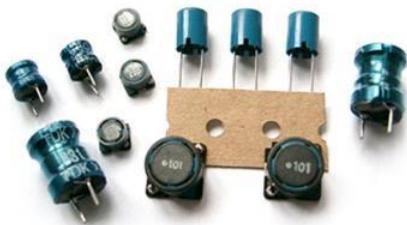

Power Inductor

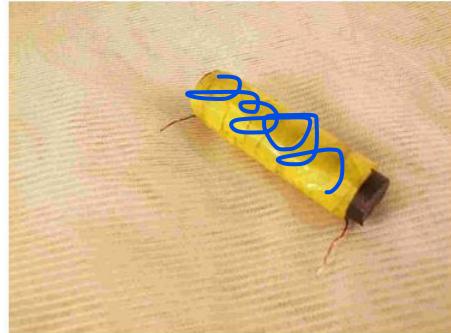

Ferrite Rod Inductor




SMD Wound Chip Inductor



Roller inductor for FM diplexer




DC filter choke Inductor

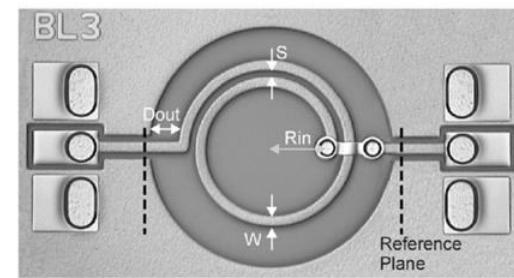



Spiral inductor with  $N=1.5$  turns,  
 $W=20 \mu\text{m}$ ,  $S=10 \mu\text{m}$  and  
 $R_{in}=100 \mu\text{m}$  (area=0.14 mm $^2$ ).  
(called On-chip inductor)

## Physical model of inductor



Compute Inductance

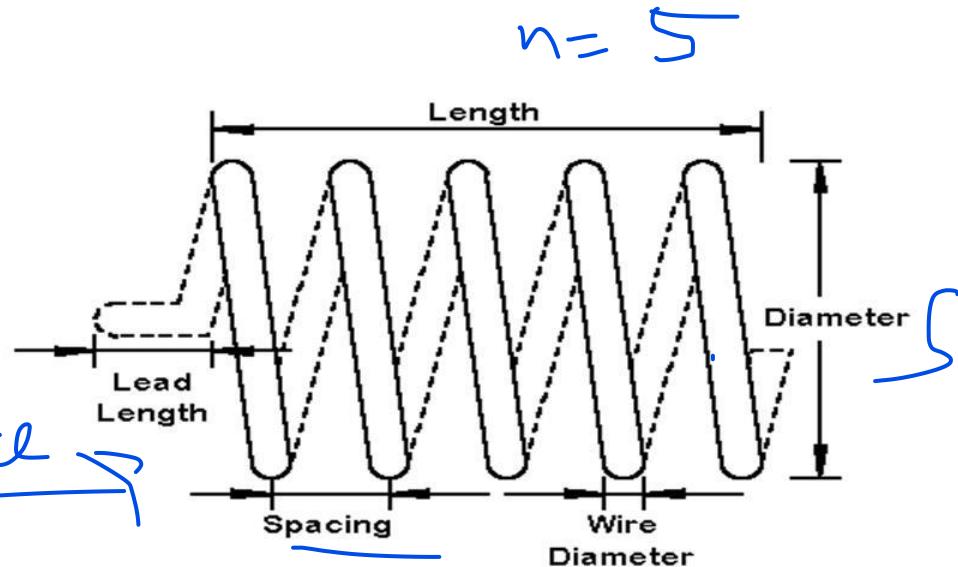

## Symbol

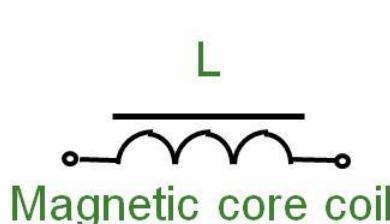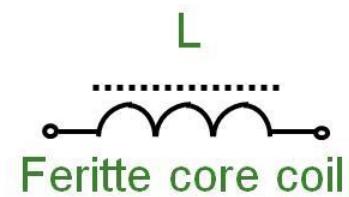

Magnetic core coil

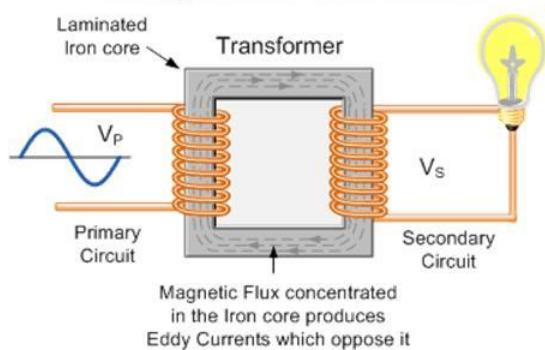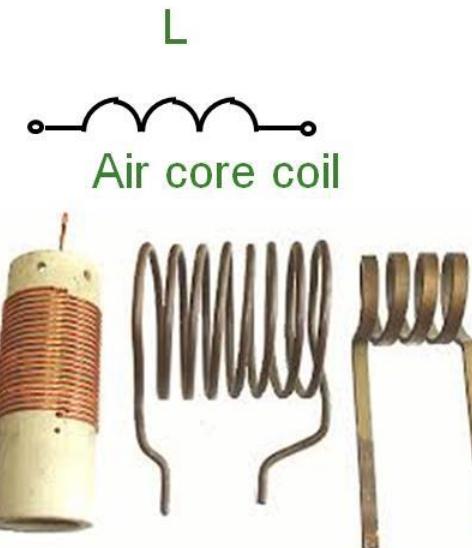

# Inductor characteristics

**Inductance** (or **electric inductance**) is a measure of the amount of **magnetic flux produced for a given electric current**. The SI unit of inductance is the **henry** (H), in honor of Joseph Henry. The symbol  $L$  is used for inductance, possibly in honour of the physicist Heinrich Lenz.

The inductance (called *self-inductance*)

$$L = \frac{\Phi}{i}$$

B.S (Wb)

L is the inductance in H, mH,  $\mu$ H  
i is the current in A,  
 $\Phi$  is the magnetic flux in Wb (webers)

The inductance (when a conductor is coiled-solenoid)

$$L = \mu \cdot N^2 \cdot \frac{S}{l}$$

(H)


S – coil's cross-sectional ( $m^2$ )

N – number of coil; l – length of coil (m)


$\mu$  - permeability of coil's core (H/ m).  $\mu = \mu_r \times \mu_0$ ,

$\mu_0$  - permeability of free space ( $4\pi \times 10^{-7}$  H/m) ;

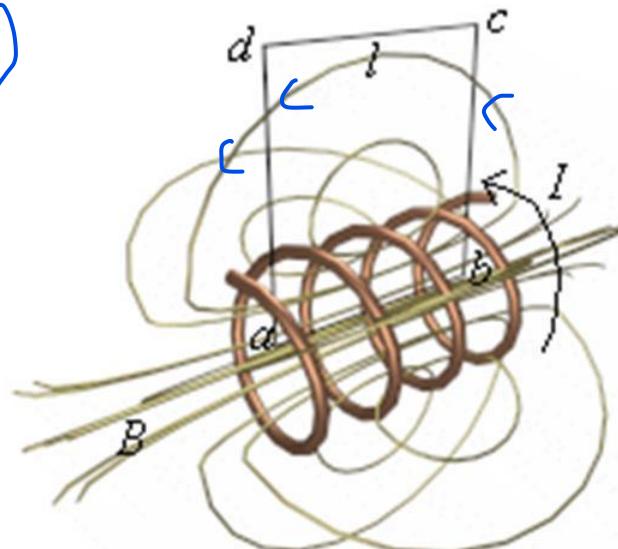
$\mu_r$  - relative permeability of the core (dimensionless)




less inductance

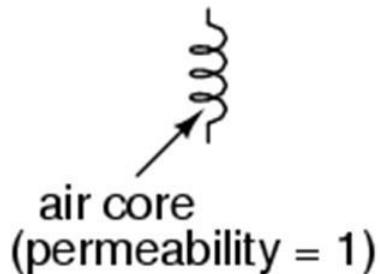

more inductance

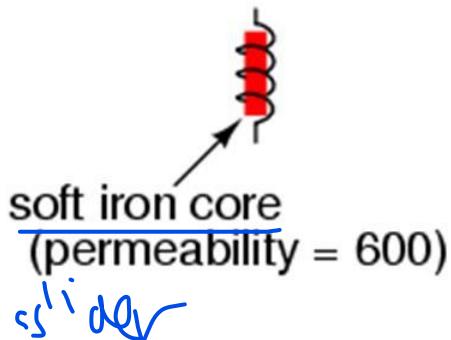

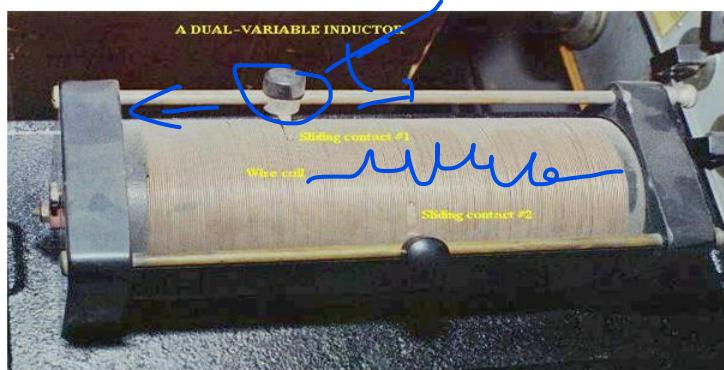A core material with greater magnetic permeability results in greater magnetic field flux for any given amount of field force (amp-turns).





**Variable inductors:** providing a way to vary the number of wire turns in use at any given time, or by varying the core material (a sliding core that can be moved in and out of the coil).



**Fixed-value inductor:** another antique air-core unit built for radios. The connection terminals can be seen at the bottom, as well as the few turns of relatively thick wire


## The inductor

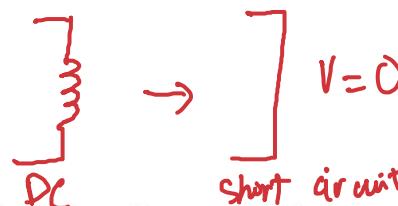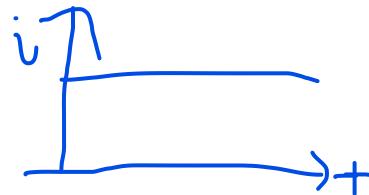

- The voltage drop across the terminals is related to the current by

For DC  $V = L \cdot 0 = 0$

$$V = L \frac{di}{dt}$$

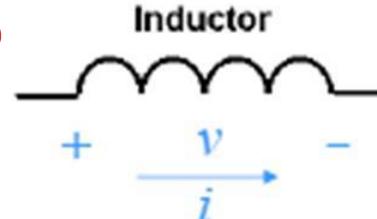

- The voltage across the terminals of an inductor is proportional to the time rate of change of the current in the inductor.
- If the current is constant (DC current) the inductor behaves as a short circuit.

$$i = \text{constant}$$

$$\frac{di}{dt} = 0$$


$$V = 0$$

- Current can not change instantaneously in an inductor (it cannot change by a finite amount in zero time)

$$\frac{di}{dt} \neq \infty$$


$$V \neq \infty$$

not allow

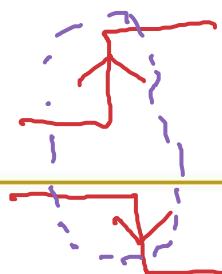
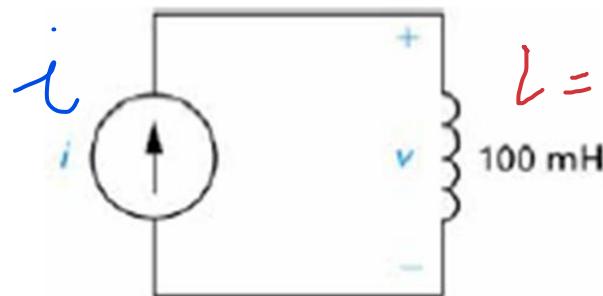
## Example 1

- If  $i = 0$  for  $t \leq 0$   
 $i = 10te^{-5t}$  A for  $t \geq 0$




- Sketch the current waveform.
- At what instant of time is the current maximum.
- Express the voltage across the terminals of the 100 mH inductor as a function of time.
- Sketch the voltage waveform.
- Are the voltage and the current at a maximum at the same time?
- At what instant of time does the voltage change polarity?
- Is there ever an instantaneous change in voltage across the inductor? If so, at what time?

doing this, we do them off the bat it's going to be

## Example (cont.)

a) Sketch the current waveform.

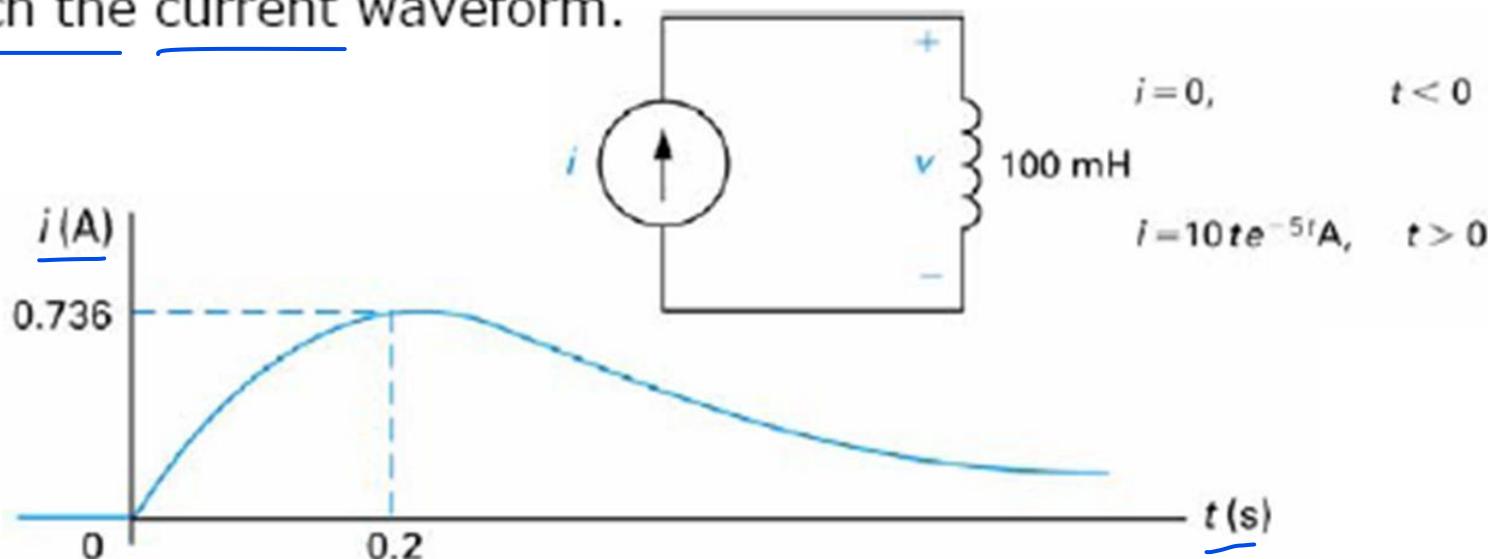

b) At what instant of time is the current maximum.

$$\frac{di}{dt} = 10e^{-5t} + 10(-5)te^{-5t}$$

$$\frac{di}{dt} \Big|_{\max} = 0 \rightarrow 10e^{-5t} + 10(-5)te^{-5t} = 0 \rightarrow 10 - 50t = 0 \rightarrow t = \frac{1}{5} \text{ s}$$

## Example (cont.)


- c) Express the voltage across the terminals of the 100 mH inductor as a function of time.

$$v = L \frac{di}{dt} = L(10 - 50t)e^{-5t} = \underline{100 \times 10^{-3}(10 - 50t)e^{-5t} \text{ V}}$$

$$v = 0 \quad \text{for } t \leq 0$$

$$v = (1 - 5t)e^{-5t} \text{ V} \quad \text{for } t \geq 0$$

- d) Sketch the voltage waveform.

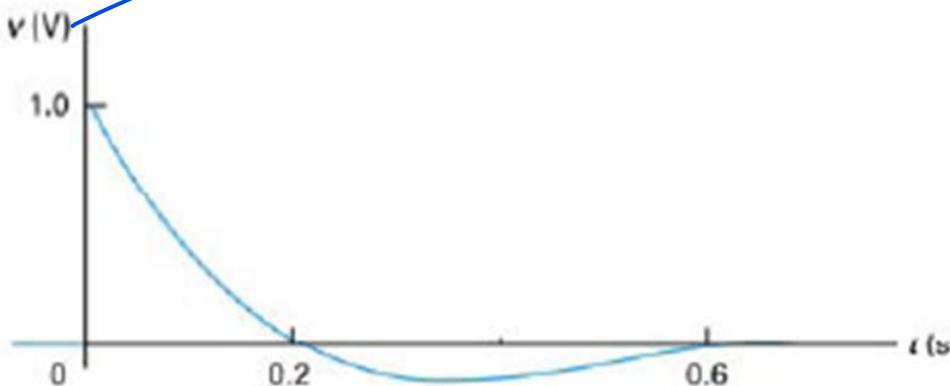

## Example (cont.)

$$V = L \frac{di}{dt}$$

e) Are the voltage and the current at a maximum at the same time.

- No  $v$  is proportional to  $di/dt$  and not  $i$ .  $V \sim \frac{di}{dt}$

f) At what instant of time does the voltage change polarity?

- at  $t=0.2$  s. ( $di/dt$  changes slope)

g) Is there ever an instantaneous change in voltage across the inductor? If so, at what time?

- Yes, at  $t=0$ .

Điing đิง qua w. cảm ko dc

They đิง túc thời

## Current in terms of voltage

- Integrate both sides in terms of  $dt$  of the equation

$$v = L \frac{di}{dt}$$

$$vdt = Ldi$$

$$L \int_{i(t_o)}^{i(t)} di = \int_{t_o}^t vdt$$

$$L[i(t) - i(t_o)] = \int_{t_o}^t vdt$$

$$i(t) = \frac{1}{L} \int_{t_o}^t vdt + i(t_o)$$

given  $v \rightarrow i$  ?


- If  $t_o = 0$ .

$$i(t) = \frac{1}{L} \int_0^t vdt + i(0)$$
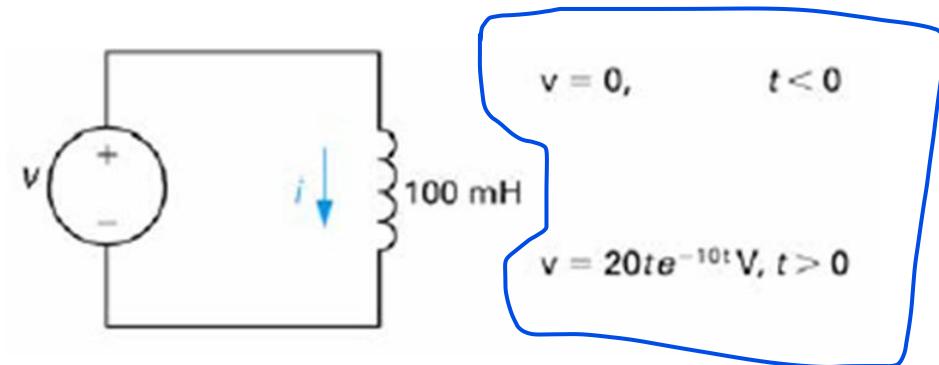
## Example 2


*Don't say  $\rightarrow i(0) = 0$*

- Sketch the voltage as a function of time.
- Find the inductor current as a function of time.
- Sketch the current as a function of time.



Ans:-

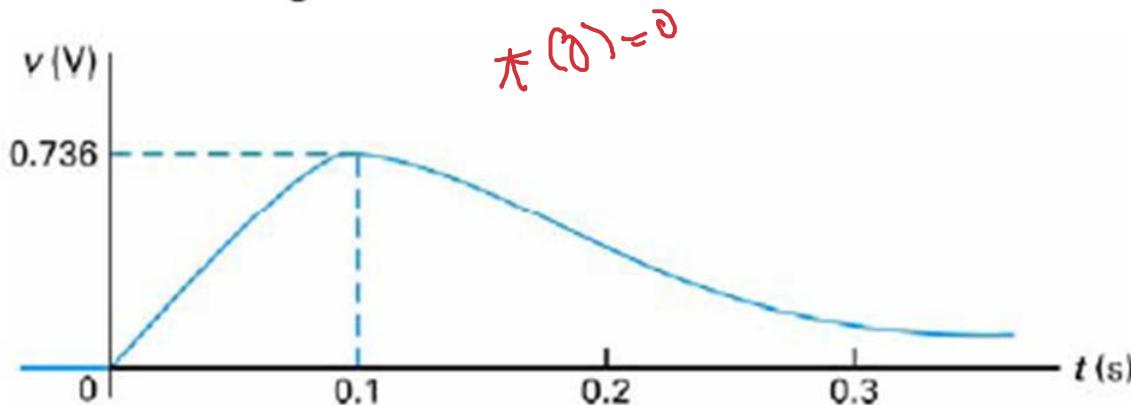- Sketch the voltage as a function of time.



## Example (cont.)


b) Find the Inductor current as a function of time.

$$i(t) = \frac{1}{L} \int_0^t v dt + i(0)$$

$$i(t) = \frac{1}{L} \int_0^t 20te^{-10t} dt + i(0)$$

$$i(t) = \frac{20}{100 \times 10^{-3} \times 100} (1 - e^{-10t} - 10te^{-10t})$$
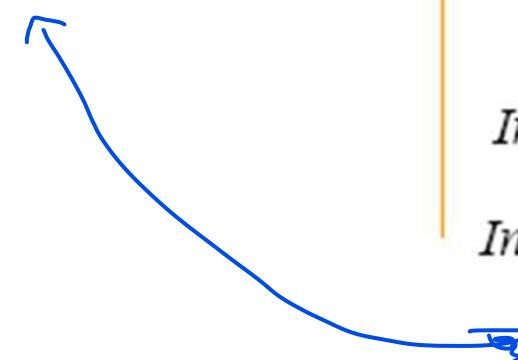
$$i(t) = 2(1 - e^{-10t} - 10te^{-10t}) \text{ A} \quad t > 0$$



$$Int = \int_0^t te^{-10t} dt$$

$$Int = \int_0^t U dV$$

$$U = t \quad dV = e^{-10t} dt$$

$$dU = dt \quad V = \frac{e^{-10t}}{-10}$$

$$Int = UV - \int_0^t V dU$$

$$Int = \frac{te^{-10t}}{-10} \Big|_0^t - \int_0^t \frac{e^{-10t}}{-10} dt$$

$$Int = \frac{te^{-10t}}{-10} - \frac{(e^{-10t} - 1)}{100}$$


$$Int = \frac{1}{100} (1 - e^{-10t} - 10te^{-10t})$$

~~Integration by part~~

## Example (cont.)

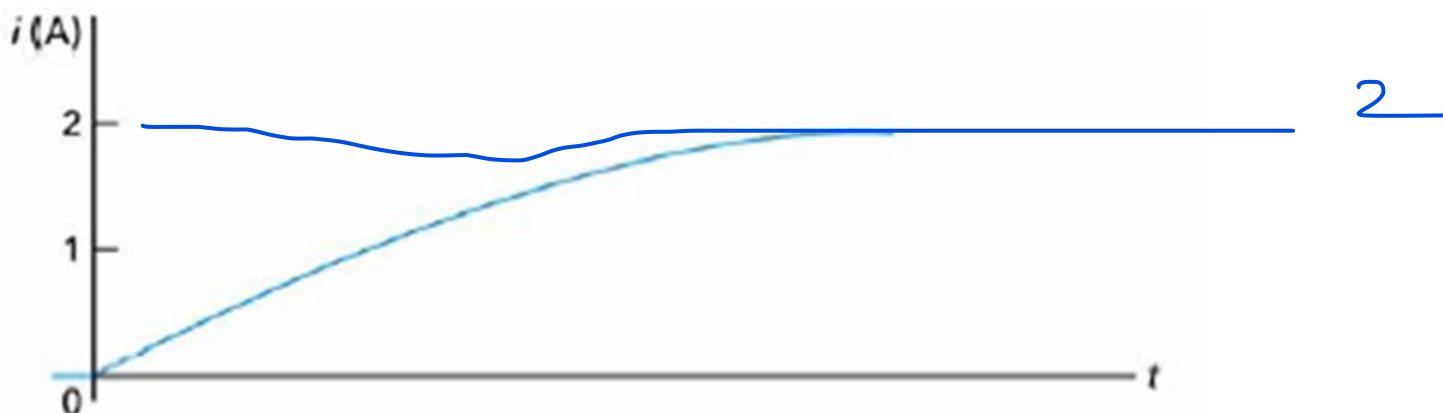c) Sketch the current as a function of time.

$$i(t) = 2(1 - e^{-10t} - 10te^{-10t}) \text{ A} \quad t \geq 0$$



## Power and Energy in the Inductor

$$\text{Power in an inductor}$$
$$P = iv = Li \frac{di}{dt}$$

$$p = iv = v \left[ \frac{1}{L} \int_{t_o}^t v dt + i(t_o) \right]$$

$$p = \frac{dw}{dt} = Li \frac{di}{dt}$$
$$dw = Lidi$$

$$\int_0^w dw = L \int_0^i idi$$

$$w = \frac{1}{2} Li^2$$



Energy in an inductor

### Example 3

- a) For example 6.1 determine, plot  $i$ ,  $v$ ,  $p$ , and  $w$  versus time.
- b) In what time interval is energy being stored on the inductor?
- c) In what time interval is energy being extracted from the inductor?
- d) What is the maximum energy stored in the inductor?
- e) Evaluate the integrals  $\int_0^{0.2} pdt$  and  $\int_{0.2}^{\infty} pdt$  and comment on their significance.
- f) Sketch For Example 6.2, and comment why  $w$  is constant?



## Example (cont.)

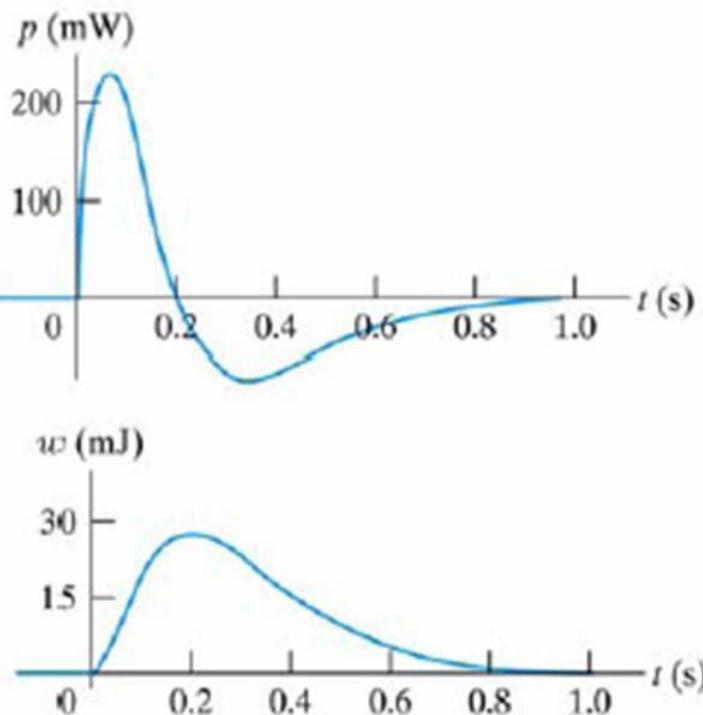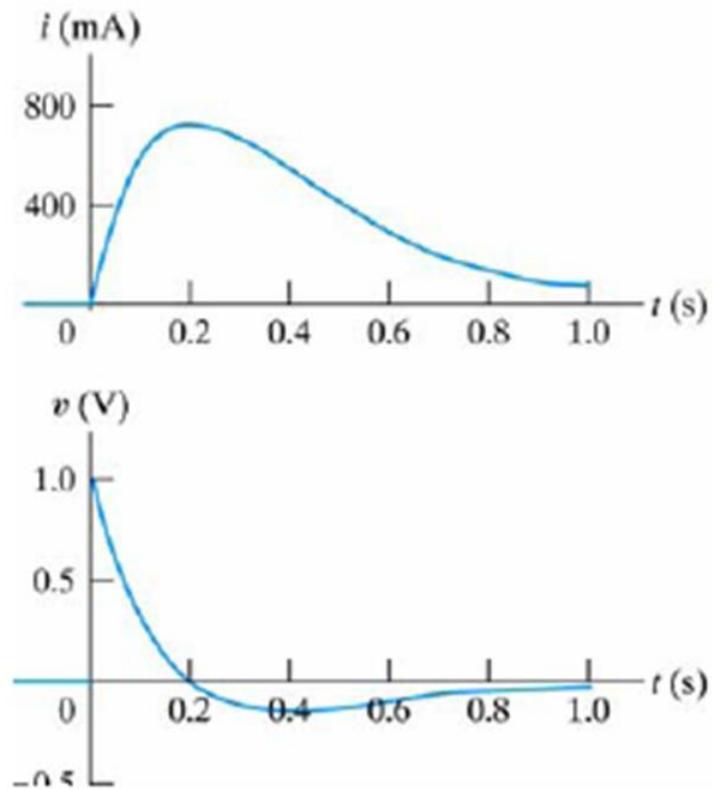- a) For the previous example determine, plot  $i$ ,  $v$ ,  $p$ , and  $w$  versus time.



## Example (cont.)

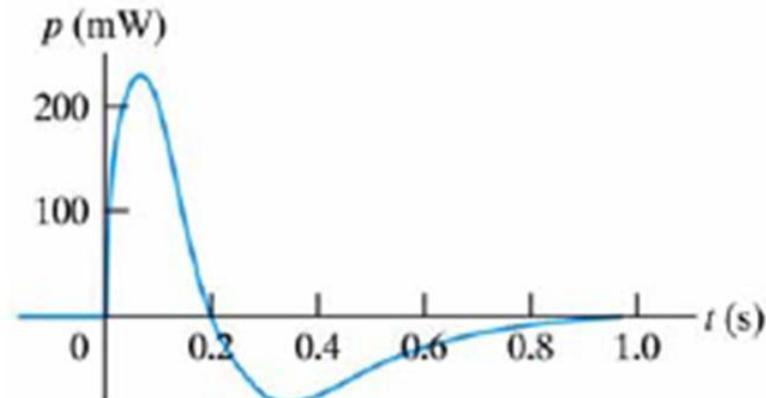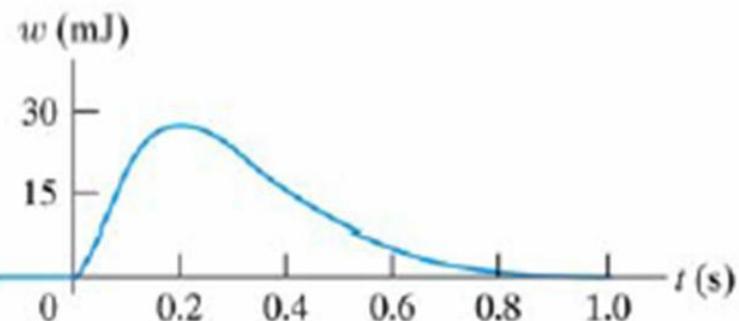- b) In what time interval is energy being stored on the inductor? ans.  $(0 < t < 0.2 \text{ s})$



- c) In what time interval is energy being extracted from the inductor? ans.  $(0.2 < t < \infty)$

- d) What is the maximum energy stored in the inductor?  
ans.  $(w_{max} = 27.07 \text{ mJ})$

## Example (cont.)

- e) Evaluate the integrals  $\int_0^{0.2} pdt$  and  $\int_{0.2}^{\infty} pdt$  and comment on their significance.

$$i = 10te^{-5t} \text{ A} \quad \& \quad v = (1 - 5t)e^{-5t} \text{ V}$$

$$p = vi = 10te^{-5t}(1 - 5t)e^{-5t} = 10t(1 - 5t)e^{-10t} \text{ W}$$

$$\int_0^{0.2} pdt = 27.07 \text{ mJ}$$





Energy Stored

$$\int_{0.2}^{\infty} pdt = -27.07 \text{ mJ}$$

Energy Extracted

## Example (cont.)

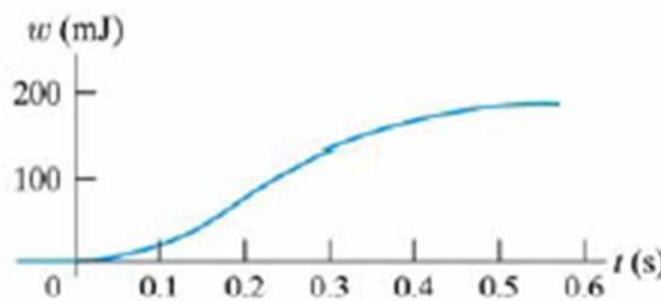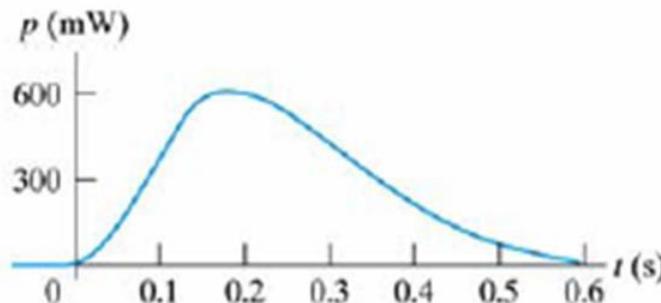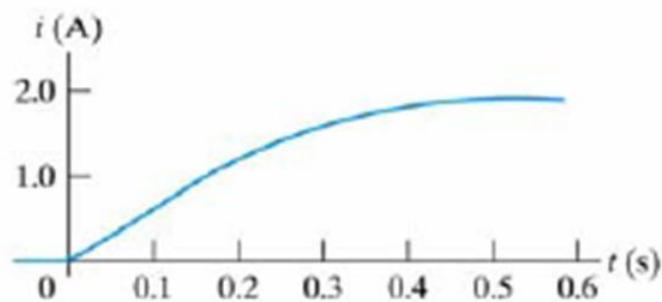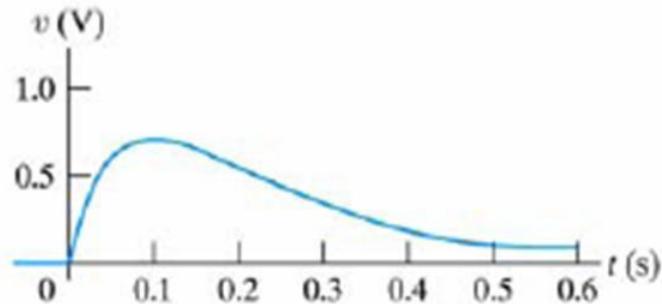f) Sketch For Example 6.2, and comment why  $w$  is constant?



- Since both the source and the inductor is ideal, when the voltage returns to zero, the energy is trapped inside the inductor and there is no means of dissipating energy.

## Impedance:

**Inductive reactance  $X_L$** , the impedance of an inductor to an AC signal, is found by the equation

$$X_L = 2\pi f L$$

$X_L$  = inductive reactance,  $\Omega$ ;  
 $f$  = frequency, Hz; and  
 $L$  = inductance, H.


## Mutual Inductance

**Mutual inductance (in H)** is the property that exists between two conductors carrying current when their magnetic lines of force link together.

The mutual inductance of two coils with fields interacting can be determined by the equation

$$M = k \sqrt{L_1 L_2}$$

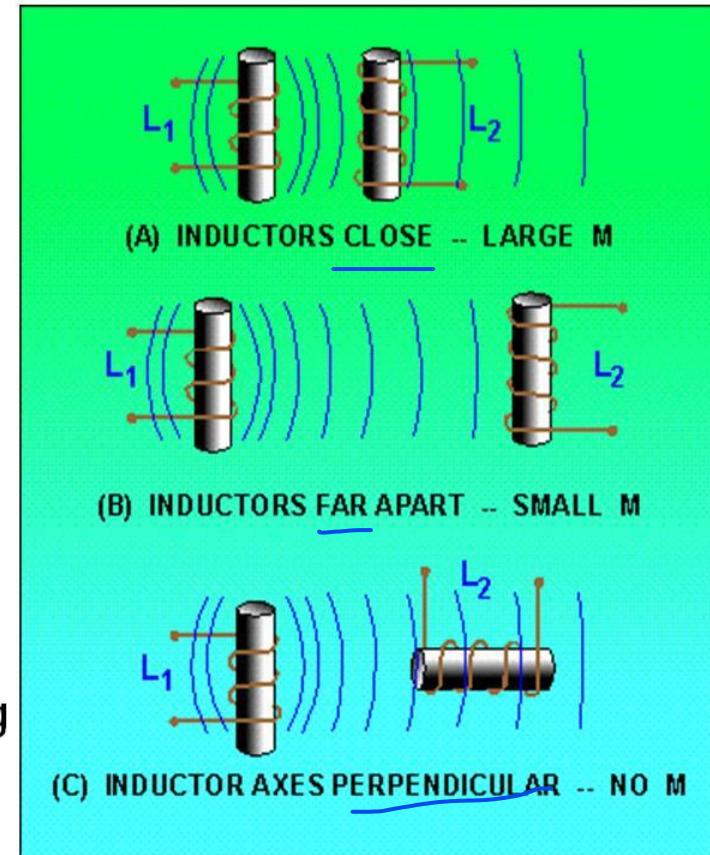
**k**: coefficient of coupling from 0 to 1


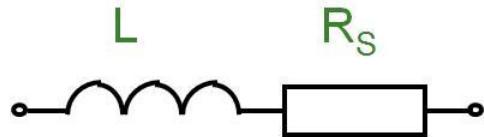
## Quality factor (Q) of Inductor

The **quality factor** of an inductor is the ratio of its inductive reactance to its resistance at a given frequency ( $\omega$ ), and is a measure of its efficiency.

The higher the Q factor of the inductor, the closer it approaches the behavior of an ideal, lossless, inductor.



The Q factor of an inductor can be found through the following formula, where  $R_S$  is its internal electrical resistance

$X_L$  = inductive reactance of the coil ( $\Omega$ )


$$Q = \frac{\omega L}{R_S} = \frac{2\pi f L}{R_S} = \frac{X_L}{R_S}$$

## Working frequency

When working frequency is small enough, the parasitic capacitors between coils of inductor is negligible. But at high frequency, these parasitic capacitors cannot be ignored.

At high frequency, the inductor become a parallel resonant circuit. The resonance of this circuit called self-resonance frequency  $f_0$ .

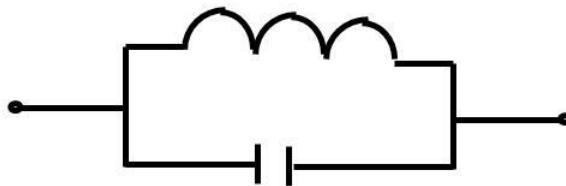At higher frequency,  $f > f_0$ , the coil has more capacitive property. **Thus, the maximum frequency of the coil should less than  $f_0$ .**



$$f_{\max} < f_0 = \frac{1}{2\pi\sqrt{LC}}$$

# Inductor code guide

## TOKEN INDUCTOR COLOR CODE

Result is in  $\mu\text{H}$

4-BAND-CODE

270 $\mu\text{H} \pm 5\%$

COLOR	1st BAND	2nd BAND	MULTIPLIER	TOLERANCE
Black	0	0	1	$\pm 20\%$
Brown	1	1	10	Military $\pm 1\%$
Red	2	2	100	Military $\pm 2\%$
Orange	3	3	1,000	Military $\pm 3\%$
Yellow	4	4	10,000	Military $\pm 4\%$
Green	5	5		
Blue	6	6		
Violet	7	7		
Grey	8	8		
White	9	9		
None				Military $\pm 20\%$
Gold			0.1 / Mil. Dec. Pt.	Both $\pm 5\%$
Silver			0.01	Both $\pm 10\%$


MILITARY-CODE

6.8 $\mu\text{H} \pm 10\%$


Military Identifier (Silver)
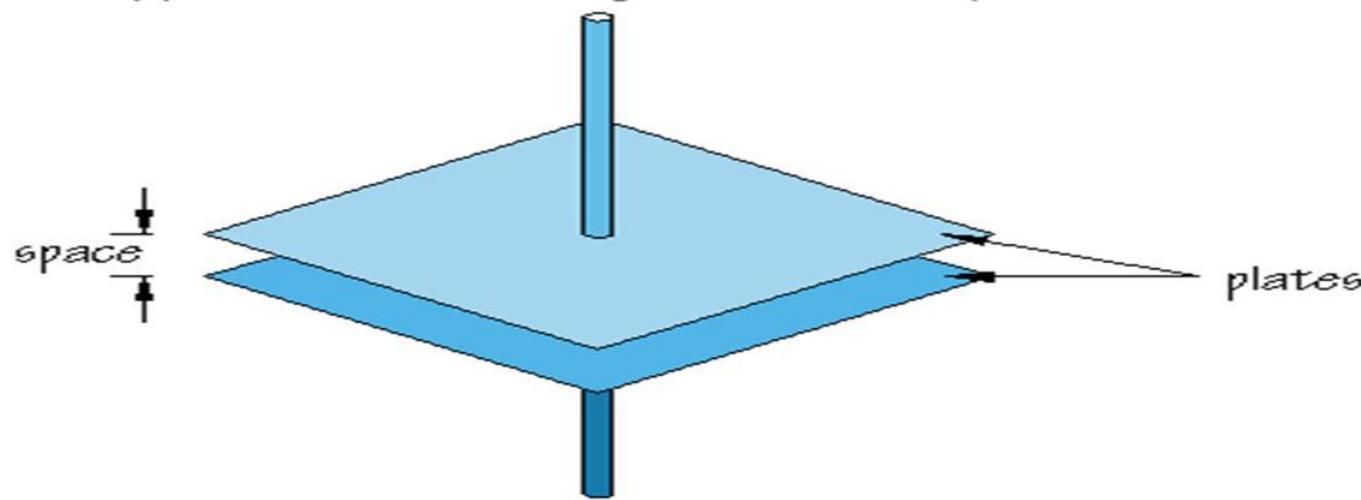
## The capacitor

- A **capacitor** is a device that stores energy in the electric field created between a pair of conductors on which equal but opposite electric charges have been placed



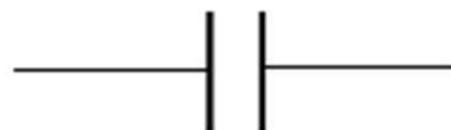
- The capacitance is measured in **Farads** (F) (It is named after the English chemist **Michael Faraday**).



## The capacitor

- The current drop across the terminals is related to the voltage by

$$i = C \frac{dv}{dt}$$

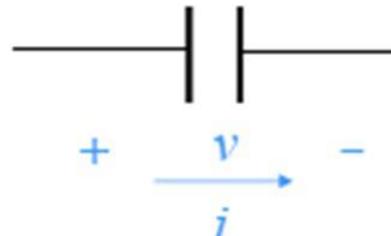

- If the voltage is constant (DC voltage) the capacitor behaves as an open circuit.

$$v = \text{constant}$$

$$\frac{dv}{dt} = 0 \quad i = 0$$

- The voltage cannot change instantaneously across the terminals of a capacitor.

$$\frac{dv}{dt} \neq \infty$$

$$i \neq \infty$$

## The capacitor power and energy

$$idt = Cdv \rightarrow dv = \frac{1}{C} idt \rightarrow v(t) = \frac{1}{C} \int_{t_o}^t idt + v(t_o)$$

$$p = vi = Cv \frac{dv}{dt}$$

Power in a capacitor

$$p = \frac{dw}{dt} = Cv \frac{dv}{dt}$$

$$dw = Cv dv$$

$$\int_o^w dw = \int_o^v Cv dv$$

$$w = \frac{1}{2} Cv^2$$

Energy in a capacitor

## Example 4

The voltage pulse is impressed across the terminals of a  $0.5 \mu\text{F}$  capacitor:

$$v(t) = \begin{cases} 0 & , t \leq 0 \text{ s} \\ 4t & , 0 \leq t \leq 1 \text{ s} \\ 4e^{-(t-1)} & , t \geq 1 \text{ s} \end{cases}$$

- Derive the expressions for the capacitor current, power, and energy.
- Sketch the voltage, current, power, and energy as functions of time.
- Specify the interval of time when energy is being stored in the capacitor.
- Specify the interval of time when energy is being delivered by the capacitor.
- Evaluate the integrals  $\int_0^1 pdt$  and  $\int_1^\infty pdt$

## Example (Cont.)

- a) Derive the expressions for the capacitor current, power, and energy.

$$i = C \frac{dv}{dt}$$





$$i(t) = C \frac{dv}{dt} = \begin{cases} 0 \times 0.5 \times 10^{-6} \\ 4 \times 0.5 \times 10^{-6} \\ -4e^{-(t-1)} \times 0.5 \times 10^{-6} \end{cases} = \boxed{\begin{cases} 0 & , t \leq 0 \text{ s} \\ 2 \mu\text{A} & , 0 \leq t \leq 1 \text{ s} \\ -2e^{-(t-1)} \mu\text{A} & , t \geq 1 \text{ s} \end{cases}}$$

$$p(t) = iv = \boxed{\begin{cases} 0 & , t \leq 0 \text{ s} \\ 8t \mu\text{W} & , 0 \leq t \leq 1 \text{ s} \\ -8e^{-2(t-1)} \mu\text{W} & , t \geq 1 \text{ s} \end{cases}}$$

$$w = \frac{1}{2} Cv^2 = \boxed{\begin{cases} 0 & , t \leq 0 \text{ s} \\ 8Ct^2 & , 0 \leq t \leq 1 \text{ s} \\ 8Ce^{-2(t-1)} & , t \geq 1 \text{ s} \end{cases}}$$

## Example (Cont.)

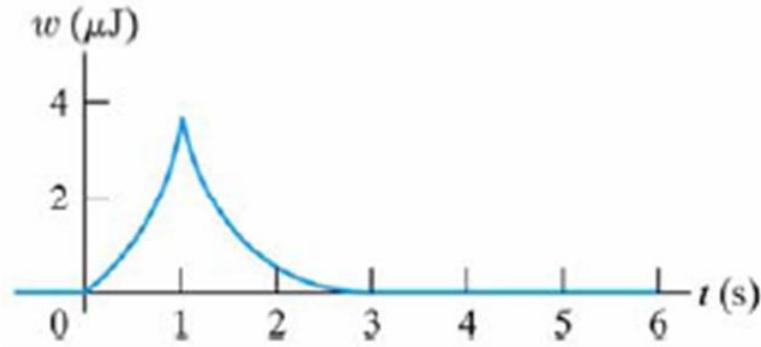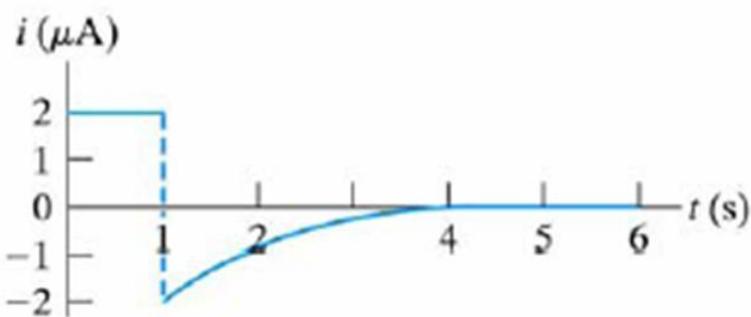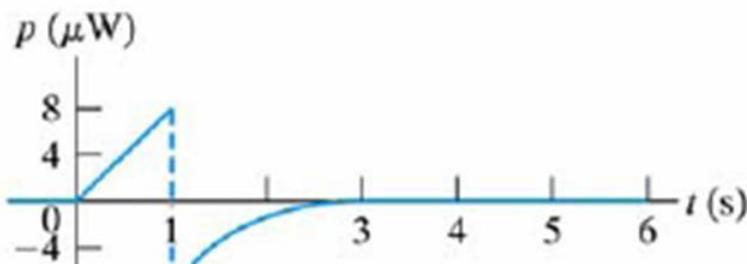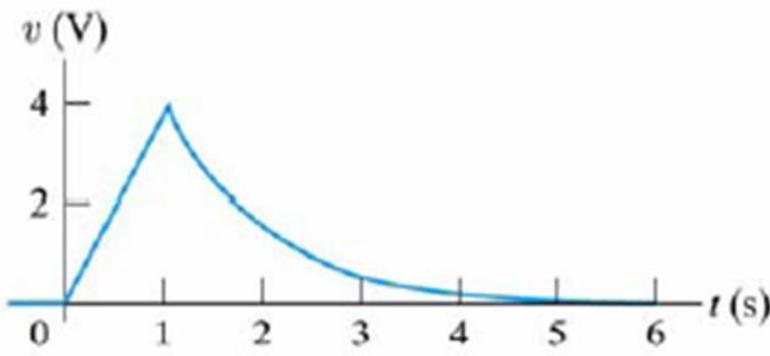- b) Sketch the voltage, current, power, and energy as functions of time.



## Example (Cont.)

- c) Specify the interval of time when energy is being stored in the capacitor.
  - $(0 < t < 1 \text{ s})$
- d) Specify the interval of time when energy is being delivered by the capacitor.
  - $(t > 1 \text{ s})$

- e) Evaluate the integrals  $\int_0^1 pdt$  and  $\int_1^\infty pdt$

$$\int_0^1 pdt = \int_0^1 8tdt = 4 \mu J \quad \text{Energy Stored}$$

$$\int_1^\infty pdt = \int_1^\infty -8e^{-2(t-1)}dt = -4 \mu J \quad \text{Energy Extracted}$$

## Example 5

An uncharged  $0.2 \mu\text{F}$  capacitor is driven by a triangle angular current pulse. The current pulse is described by

$$i(t) = \begin{cases} 0 & , t \leq 0 \text{ s} \\ 5000t \text{ A} & , 0 \leq t \leq 20 \mu\text{s} \\ 0.2 - 5000t \text{ A} & , 20 \leq t \leq 40 \mu\text{s} \\ 0 & , t \geq 40 \mu\text{s} \end{cases}$$

- a) Derive the expressions for the capacitor voltage, power, and energy.
- b) Sketch the current, voltage, power, and energy as functions of time.
- c) Why does a voltage remain on the capacitor after the current returns to zero.

## Example (Cont.)

- a) Derive the expressions for the capacitor voltage, power, and energy.

$t \leq 0 \text{ s}$  (All equal to zero)

$0 \leq t \leq 20 \mu\text{s}$

$$v = \frac{1}{0.2\mu} \int_0^{20\mu} idt + 0 = \frac{1}{0.2\mu} \int_0^{20\mu} 5000tdt = 12.5 \times 10^9 t^2 \text{ V}$$

$$p = vi = 62.5 \times 10^{12} t^3 \text{ W}$$

$$w = \frac{1}{2} Cv^2 = 15.625 \times 10^{12} t^4 \text{ J}$$

$20 \leq t \leq 40 \mu\text{s}$

$$v = (10^6 t - 12.5 \times 10^9 t^2 - 10) \text{ V}$$

$$p = vi = (62.5 \times 10^{12} t^3 - 7.5 \times 10^9 t^2 + 2.5 \times 10^5 t - 2) \text{ W}$$

$$w = \frac{1}{2} Cv^2 = (15.625 \times 10^{12} t^4 - 2.5 \times 10^9 t^3 + 0.125 \times 10^6 t^2 - 2t + 10^{-5}) \text{ J}$$

## Example (Cont.)





$$t \geq 40 \mu\text{s}$$

$$v = 10 \text{ V}$$

$$p = vi = 0$$


$$w = \frac{1}{2} Cv^2 = 10 \mu\text{J}$$

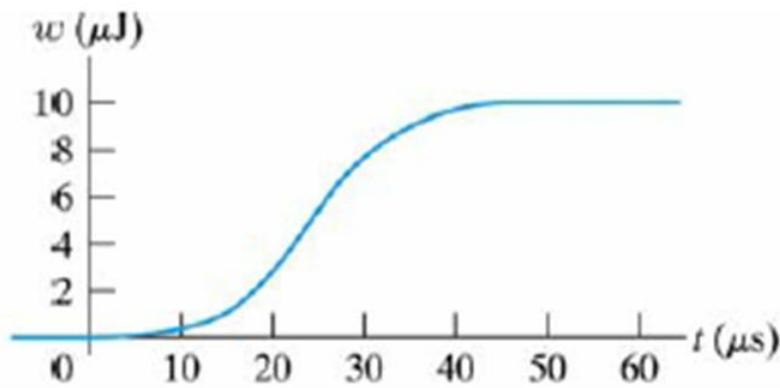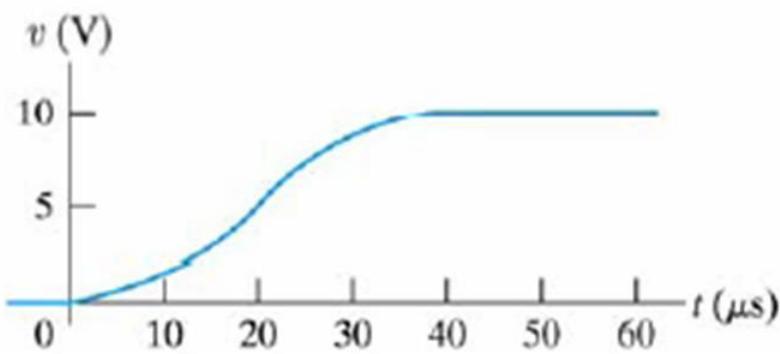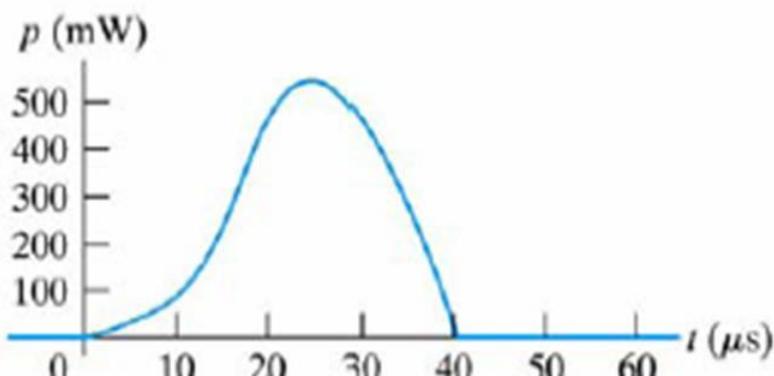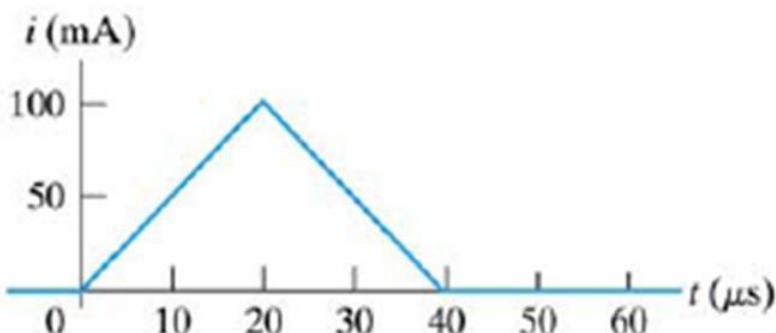- b) Sketch the current, voltage, power, and energy as functions of time.



## Example (Cont.)

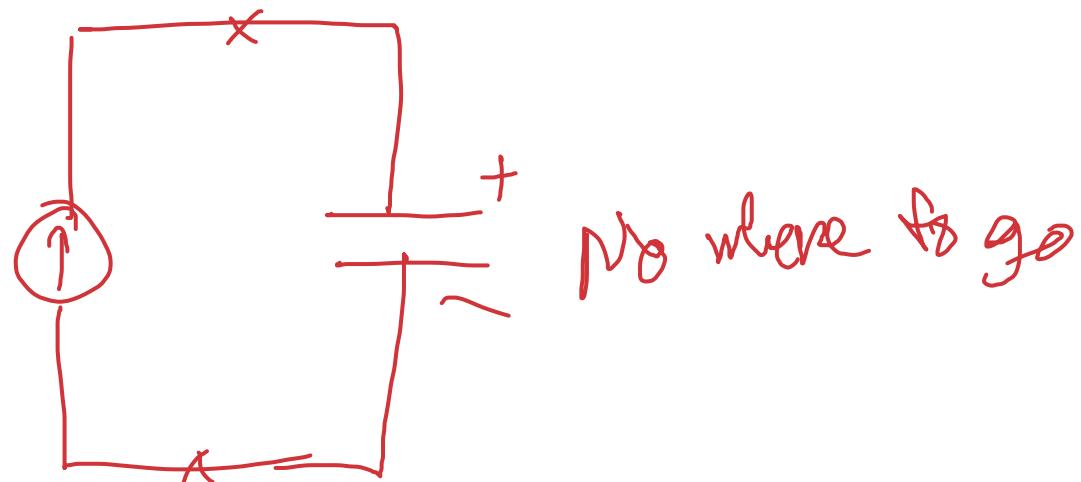- c) Why does a voltage remain on the capacitor after the current returns to zero.
- Since both the source and the capacitor is ideal, when the current returns to zero, the energy is trapped inside the capacitor and there is no means of dissipating energy.



## Various types of capacitors.



tantalum  
capacitor



Polypropylene  
Capacitor



Polyester  
capacitor



High  
Voltage/power  
Capacitors



Multilayer Chip  
Ceramic Capacitor




Motor Running &  
Start Capacitors




Variable  
Capacitor




Tuning/Air  
Variable  
Capacitor

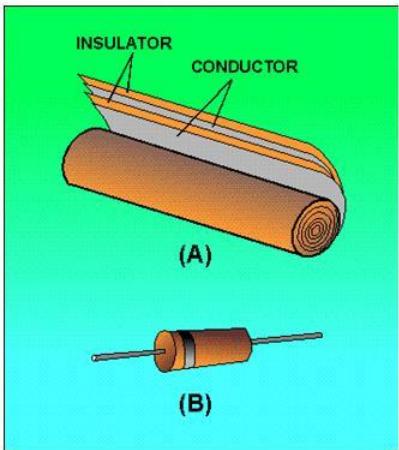

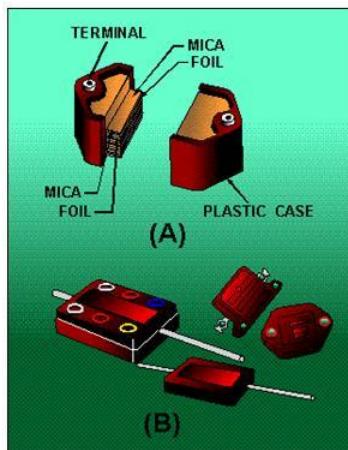
Paper capacitor (300pF - 4 $\mu$ F); max 600Volts



Mica capacitor (50pF -0.02 $\mu$ F)

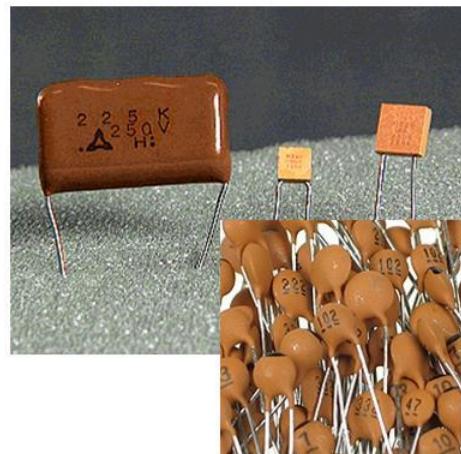

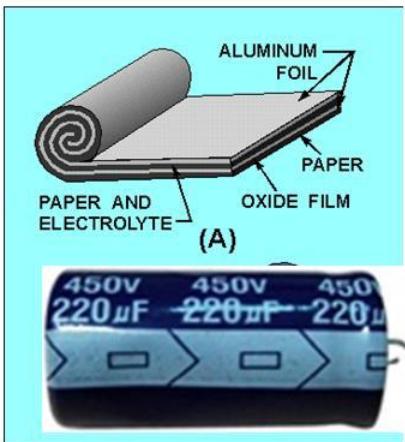
Ceramic Capacitor (1pF - 0.01 $\mu$ F); max 30kVolts



(Aluminum) Electrolytic Capacitor; (4 $\mu$ F ~ several thousand F); max 500Volts



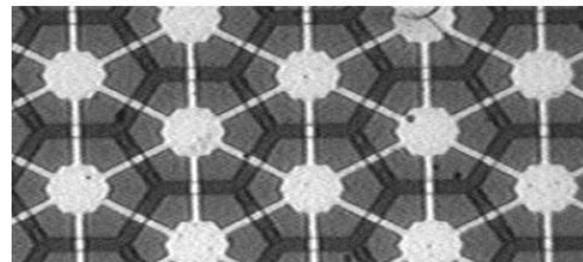Oil capacitor (nF –several hundred  $\mu$ F) several ten Kvolts



Top view of MEMS capacitor built at Stanford. The resonant frequency is 1.64 MHz with a Q of 18

Type ⊕ = polarized	Pic	Cap Range	ESR Equivalent Series Resistance	Leakage	Voltage Rating	Temp Range	Gen Notes
Ceramic		pF - $\mu$ F	low	med	high	-55° to +125°C	Multipurpose Cheap
Mica (silver mica)		pF - nF	low 0.01-0.1Ω	low	high	-55° to +125°C	For RF filters Expensive Very stable
Plastic Film (polyethylene polystyrene)		few $\mu$ Fs	med	med	high	varies	For low freq Cheap
Tantalum tantalum metal anode		$\mu$ Fs	high 0.5-5.0Ω	low	lowest	-55° to +125°C	Expensive Nonlinear (bad for audio) excellent stability over time
OSCON (Aluminum-Polymer)		$\mu$ Fs	low 0.01-0.5Ω	low	low	-55° to +105°C	Best quality Highest price excellent noise reduction and ripple current
Aluminum Electrolytic		high $\mu$ Fs	high 0.05-2.0Ω	med	low	-40° to +85°C	For low-med frequencies Cheap Hold charge for long time – not for production test

Table 2. Common Capacitor Specifications and Trade-offs

## Capacitor Code Guide

The 3 numbers: It is somewhat similar to the resistor code. The first two are the 1st and 2nd significant digits and the third is a multiplier code. Most of the time the last digit tells you how many zeros to write after the first two digits, but the standard (EIA standard) has a couple of curves that you probably will never see. But just to be complete here it is in a table.

**Table 1** Digit multipliers

Third digit	Multiplier (this times the first two digits gives you the value in Pico-Farads)
0	1
1	10
2	100
3	1,000
4	10,000
5	100,000
6 not used	
7 not used	
8	.01
9	.1

Ex: A capacitor marked 104 is 10 with 4 more zeros or 100,000pF which is otherwise referred to as a .1  $\mu$ F capacitor.

**EIA = Electronic Industrial Association**

<http://xtronics.com/kits/ccode.htm>

## Capacitor Code Guide - EIA Capacitance Code

Table 2 Letter tolerance code


Letter symbol	Tolerance of capacitor
B	+/- 0.10%
C	+/- 0.25%
D	+/- 0.5%
E	+/- 0.5%
F	+/- 1%
G	+/- 2%
H	+/- 3%
J	+/- 5%
K	+/- 10%
M	+/- 20%
N	+/- 0.05%
P	+100% , -0%
Z	+80%, -20%

So a 103J is a 10,000 pF with +/-5% tolerance
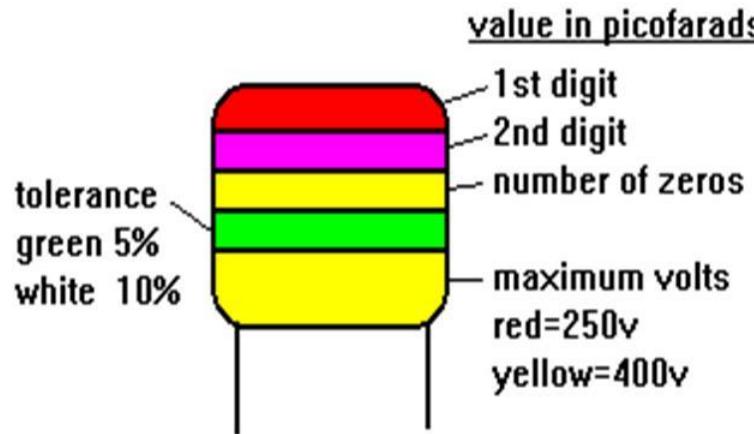
## Capacitor Code Guide – Color code

Some values are indicated with a colour code similar to resistors. There can be some confusion.

A 2200pf capacitor would have three red bands. These merge into one wide red band.



Some values are marked in picofarads using three digit numbers. The first two digits are the base number and the third digit is a multiplier.

For example, 102 is 1000 pF and 104 is 100,000 pF = 100 nF = 0.1 uF.

## Impedance of capacitor:

The ratio of the phasor voltage across a circuit element to the phasor current through that element is called the impedance  $Z$ . For a capacitor, the impedance is given by

$$Z_C = \frac{V_C}{I_C} = \frac{-j}{2\pi f C} = -j X_C,$$

$X_C = \frac{1}{\omega C}$  is the capacitive reactance 

$\omega = 2\pi f$  is the angular frequency


$f$  is the frequency

$C$  is the capacitance F


$j$  is the imaginary unit

# Capacitor Impedance

frequency	frequency approaches	impedance approaches	looks like	called
low	$\rightarrow 0$	$\rightarrow \infty$	---	open circuit
high	$\rightarrow \infty$	$\rightarrow 0$	-----	short

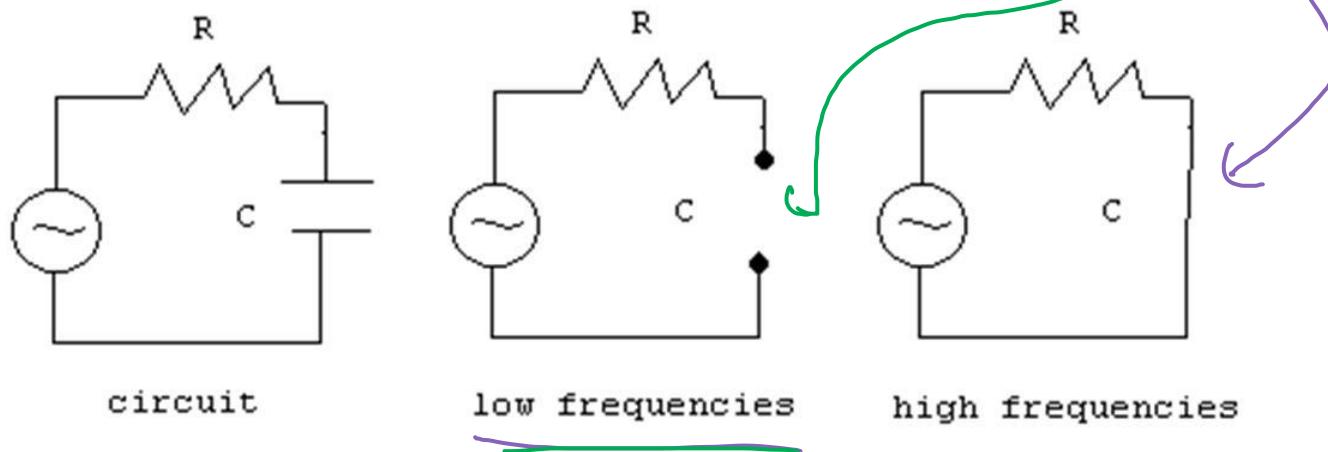

## Series-parallel Combinations

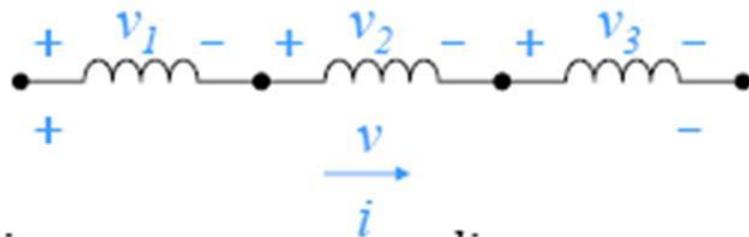


$$v_1 = L_1 \frac{di}{dt}$$

$$v_2 = L_2 \frac{di}{dt}$$


$$v_3 = L_3 \frac{di}{dt}$$

$$v = v_1 + v_2 + v_3 = (L_1 + L_2 + L_3) \frac{di}{dt}$$
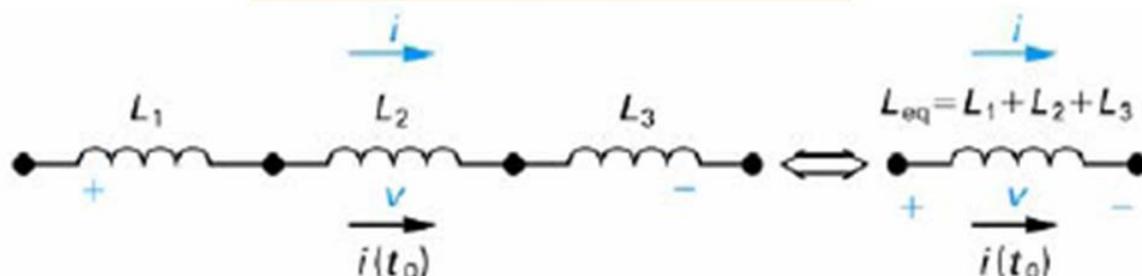
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$



## Series-parallel Combinations

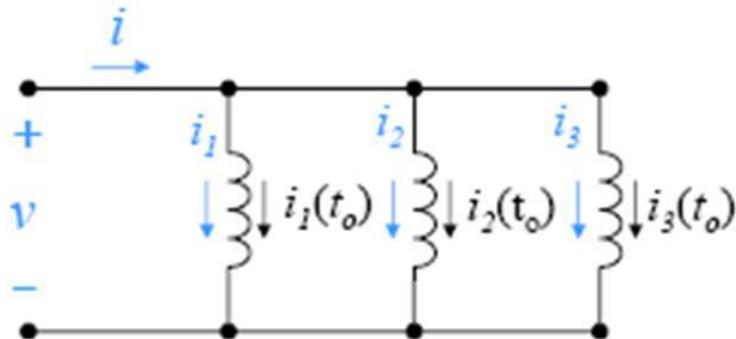

$$i_1(t) = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0)$$

$$i_2(t) = \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0)$$

$$i_3(t) = \frac{1}{L_3} \int_{t_0}^t v dt + i_3(t_0)$$


$$i = i_1 + i_2 + i_3 = \left( \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + i_3(t_0)$$

$$i = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_n}$$


## Series-parallel Combinations

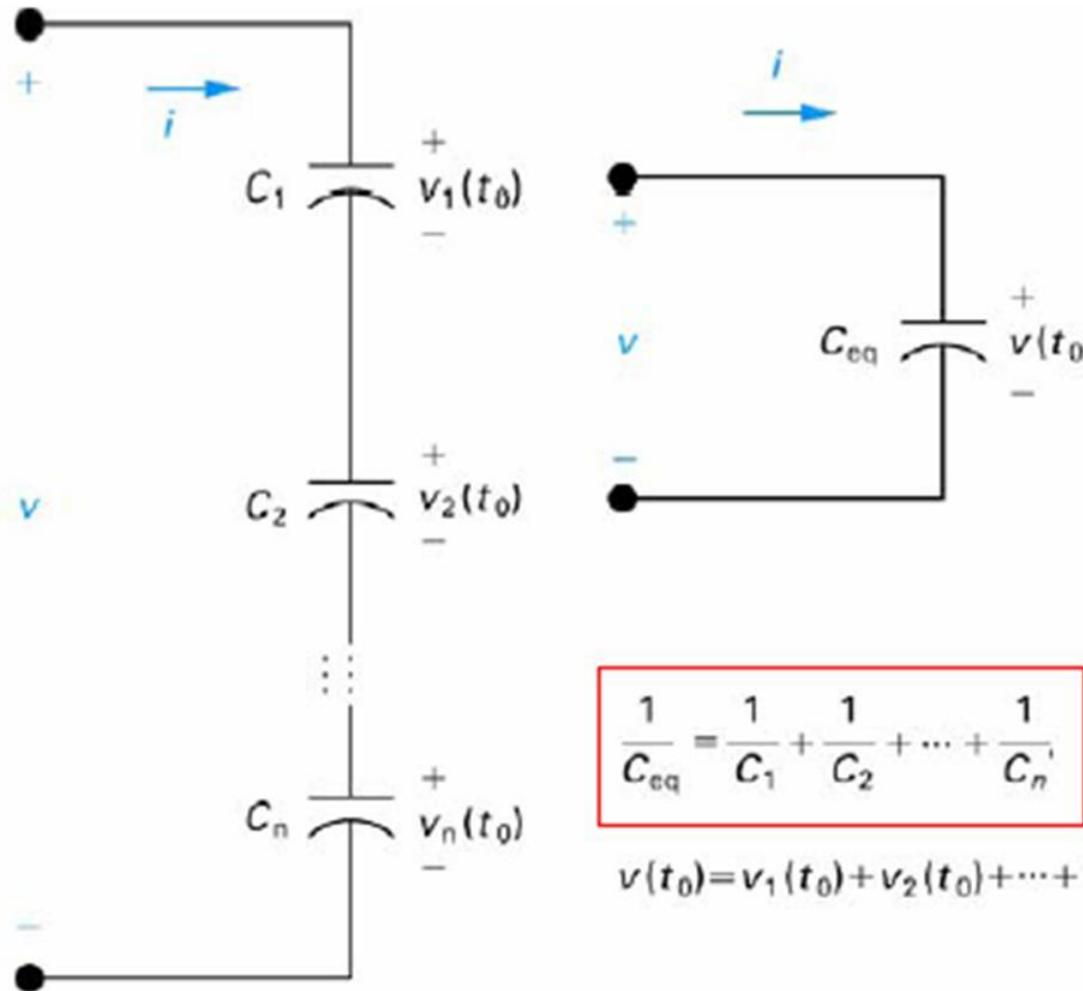


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$

## Series-parallel Combinations

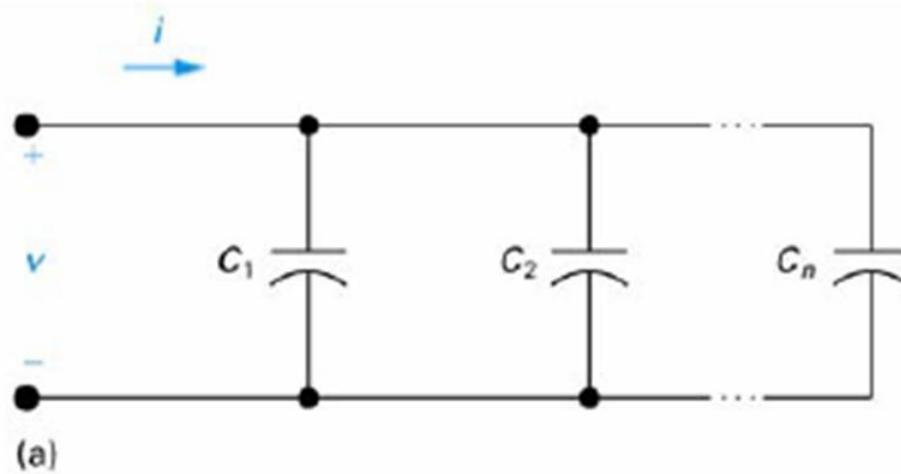

(a)

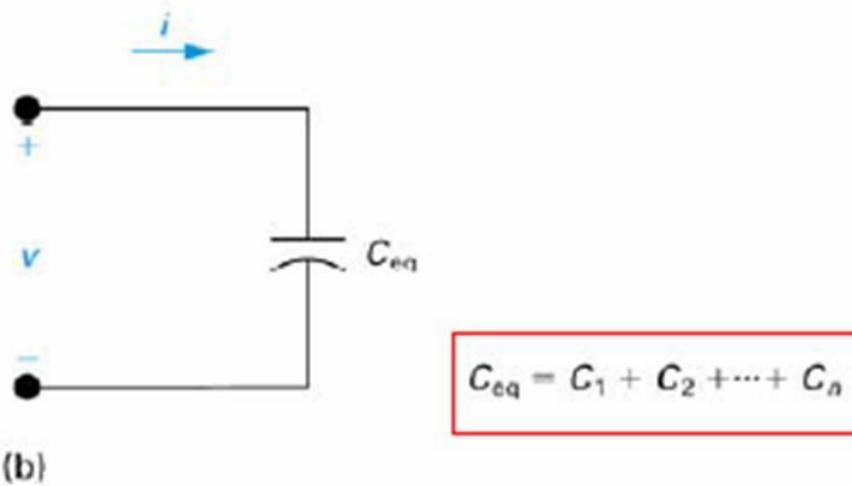

(b)

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

## Problem 1

Find  $L_{ab}$ ?

$$\frac{1}{20} + \frac{1}{30}$$

Ans. :



$$L_{eq1} = 20//30 = 12 \text{ H}$$

$$L_{eq2} = 12 + 8 = 20 \text{ H}$$


$$L_{eq3} = 20//80 = 16 \text{ H} \quad \frac{1}{20} + \frac{1}{80}$$

$$L_{eq4} = 14 + 16 = 30 \text{ H}$$

$$L_{eq5} = 30//60 = 20 \text{ H} \quad \frac{1}{30} + \frac{1}{60}$$

$$L_{eq6} = 10 + 20 = 30 \text{ H}$$

$$L_{eq7} = 30//15 = 10 \text{ H}$$

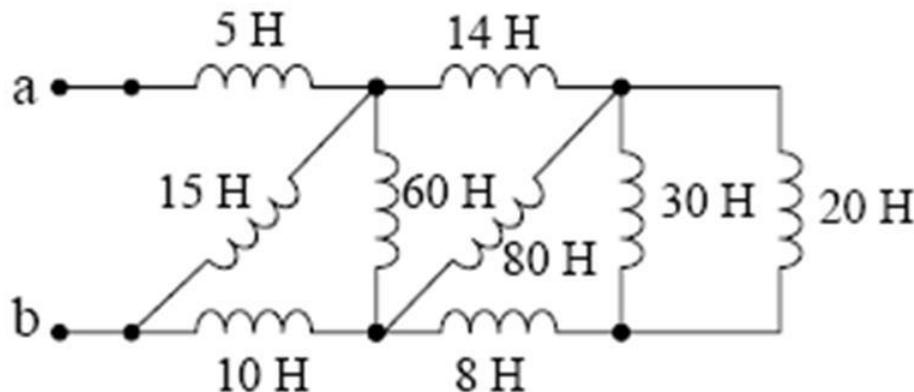

$$L_{ab} = 10 + 5 = 15 \text{ H}$$



## Problem 2

Find  $C_{ab}$ ?

Ans. :

$$8 + 16$$

$$8 \mu\text{F} // 16 \mu\text{F} \rightarrow 24 \mu\text{F}$$

$$6 \mu\text{F} \text{ series } 4 \mu\text{F} \rightarrow \frac{6 \mu\text{F} \times 4 \mu\text{F}}{4 \mu\text{F} + 6 \mu\text{F}} = 2.4 \mu\text{F}$$


$$2.4 + 1.6 = 4$$

$$2.4 \mu\text{F} // 1.6 \mu\text{F} \rightarrow 4 \mu\text{F}$$

$$12 \mu\text{F} \text{ series } 4 \mu\text{F} \rightarrow 3 \mu\text{F}$$

$$5 \mu\text{F} // 3 \mu\text{F} \rightarrow 8 \mu\text{F}$$
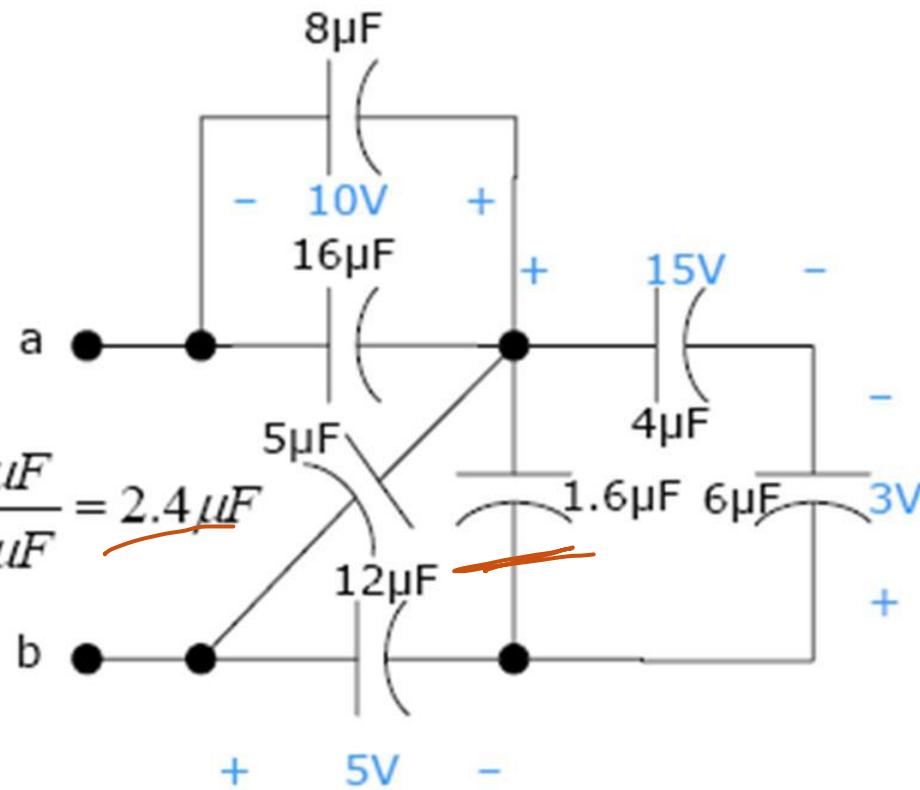
$$24 \mu\text{F} \text{ series } 8 \mu\text{F} \rightarrow 6 \mu\text{F}$$




## Mutual Inductance

The voltage induced in the second circuit can be related to the time-varying current in the first circuit by a parameter known as mutual inductance.

The inductance introduced earlier is known as the self inductance ( $L_1$  &  $L_2$ ).

$M$  is the value of Mutual inductance.

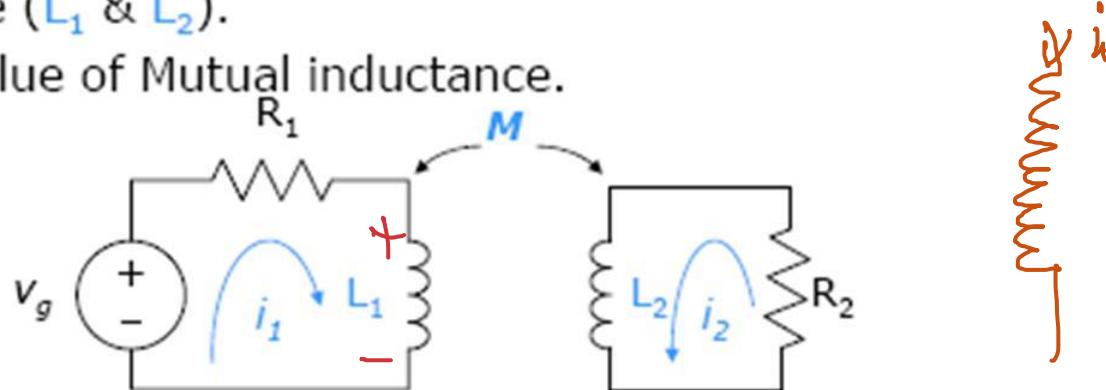

Consider coil 1 (left side)

$$L_1 \frac{di_1}{dt} \text{ (Self Inductance)}$$

?

$$M \frac{di_2}{dt} \text{ (Mutual Inductance)}$$


$$-v_g + i_1 R_1 + L_1 \frac{di_1}{dt} \boxed{\pm} M \frac{di_2}{dt} = 0$$

mutual

XVL
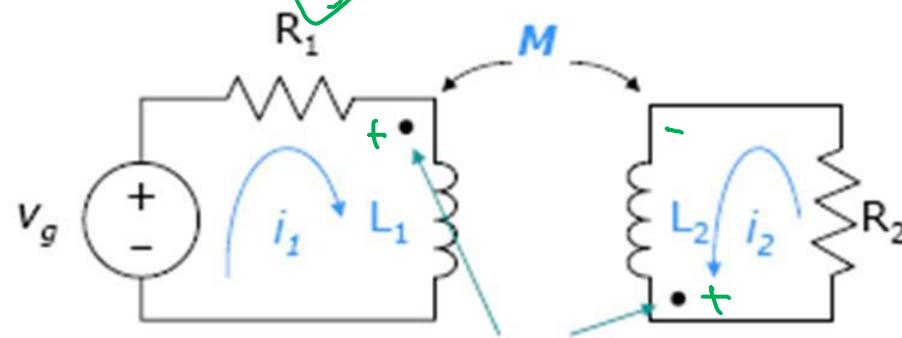
## Mutual Inductance

- The sign of the mutual induced voltage depends on the way the coils are wound in relation to the reference direction of coil currents.




$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$-V_g + i_1 R_1 + L_1 \frac{di_1}{dt}$$

$$-M \frac{di_2}{dt} = 0$$

Enter + ; Leave -

## Mutual Inductance

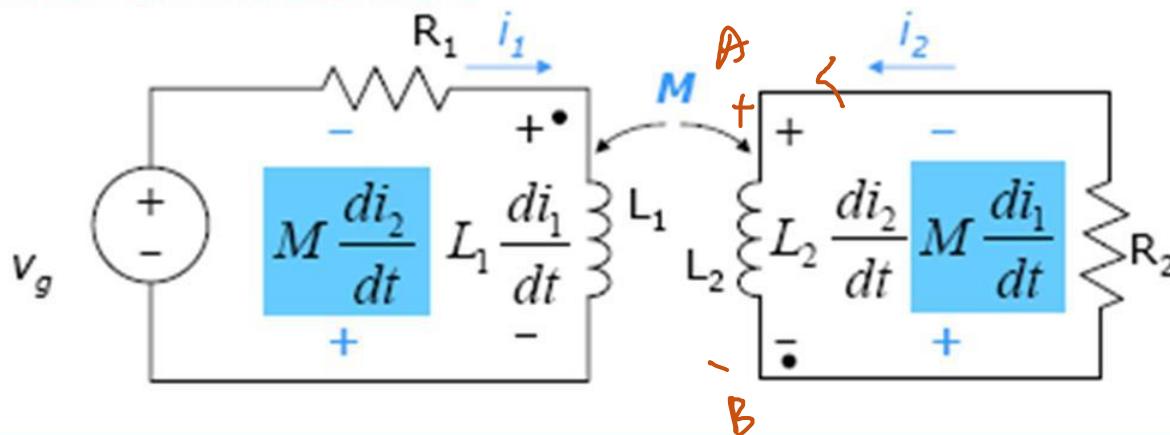

When the reference direction for a current **enters** the dotted terminal of a coil, the **reference polarity** of the voltage that it induces in the other coil is **positive** at its dotted terminal.

When the reference direction for a current **leaves** terminal of a coil, the **reference polarity** of the voltage that it induces in the other coil is **negative** at its dotted terminal.

$$-v_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$$

$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$

## Example 6

Enter + | Leave -

Write mesh equations in terms of  $i_1$  and  $i_2$ .  $M = 8H = K \sqrt{L_1 L_2}$

Ans.:

$$M \frac{di}{dt}$$

Mesh Number #1

$$4 \frac{di_1}{dt} - 8 \frac{d(i_2 - i_g)}{dt} + (i_1 - i_2)20 + (i_1 - i_g)5 = 0$$

Check from 2<sup>nd</sup> L

Mesh Number #2

$$16 \frac{d(i_2 - i_g)}{dt} - 8 \frac{di_1}{dt} + (i_2 - i_1)20 + i_2 60 = 0$$

KVL

$$+ M \frac{di}{dt}$$

