

a. The variable resistor (R_o) in the circuit is adjusted until the power dissipated in the resistor is 100 W. Find the values of R_o that satisfy this condition (use Thevenin equivalent with respect to the terminals R_o).

b. Find the maximum power.


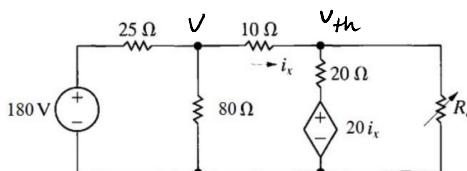


Fig. 1.

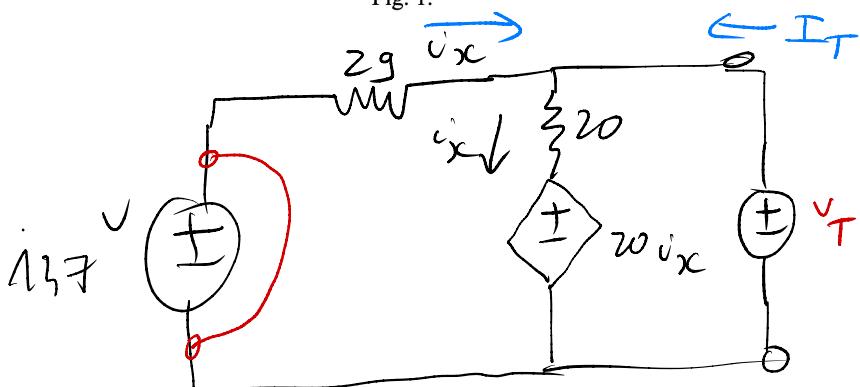

$$a) i_x = \frac{137 - 20i_x}{4g} \rightarrow i_x = 1.99^A$$

$$v_{th} = 20i_x + 20i_x = 79.6 \text{ V}$$

$$b) I_T = \frac{v_T}{2g} + \frac{v_T - 20(-\frac{v_T}{2g})}{20}$$

$$\dots \frac{I_T}{v_T} = \frac{69}{580} \rightarrow R_{th} = 8.4$$



$$c) P = R_o \left(\frac{v_{th}}{R_{th} + R_o} \right)^2 = 100$$

—


Problem 2: Consider the circuit in Fig. 2,

a. Use the principle of superposition to find the voltage v in the circuit.

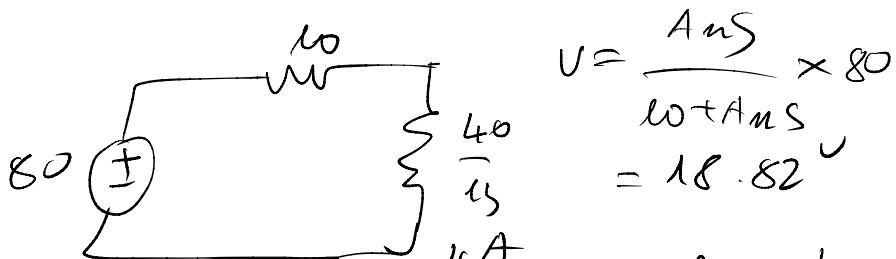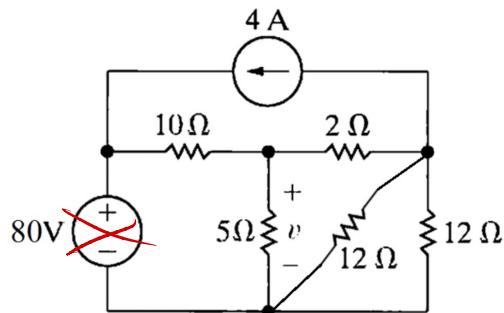b. Find the power dissipated in the 5Ω resistor.



b)


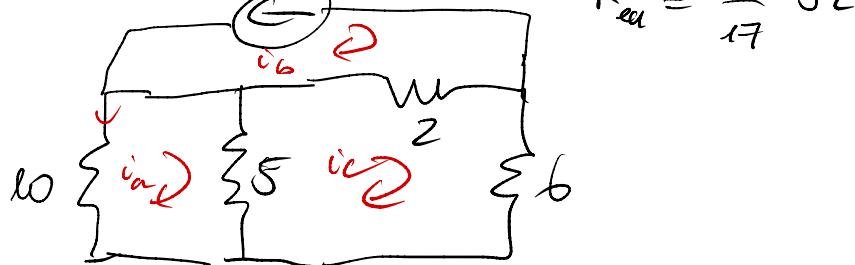


$$10(i_a + 4) + 5(i_a - i_c) = 0$$

$$5(i_c - i_a) + 2(i_c + 4) + 6i_c = 0$$

$$\begin{cases} i_a = -3.3 \\ i_c = -1.88 \end{cases} \Rightarrow v'' = -7 \text{ V}$$

$$\rightarrow v = 11.72 \text{ V}$$

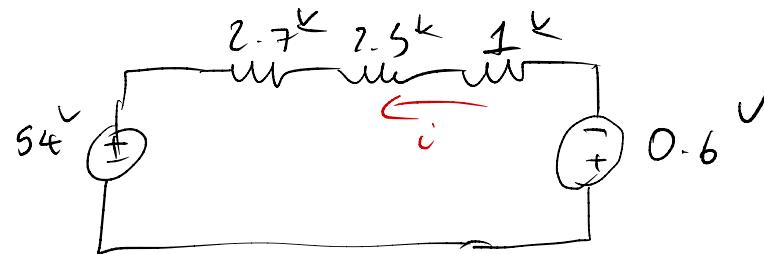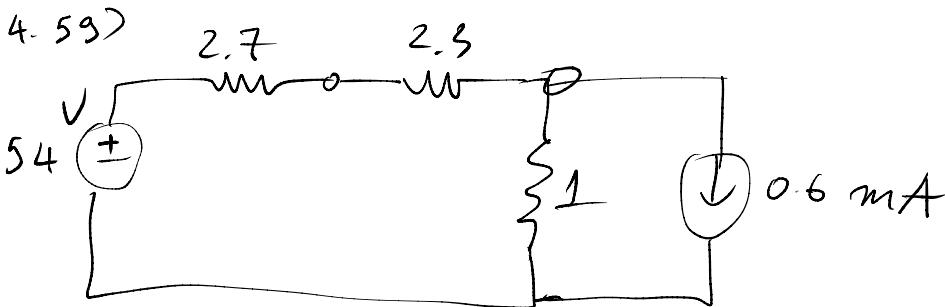


$$54 + 6i_o + 0.6 = 0$$

$$\Rightarrow i_o = -1 \text{ mA}$$

Section 4.9




- 4.59 a) Use a series of source transformations to find the current i_o in the circuit in Fig. P4.59.
PSpice
MULTISIM
- b) Verify your solution by using the node-voltage method to find i_o .

Figure P4.59

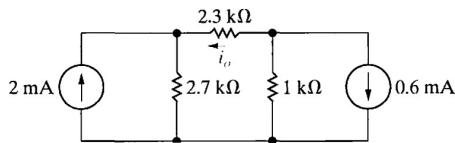

4.62

Figure P4.62

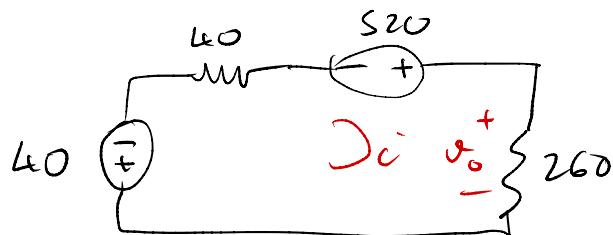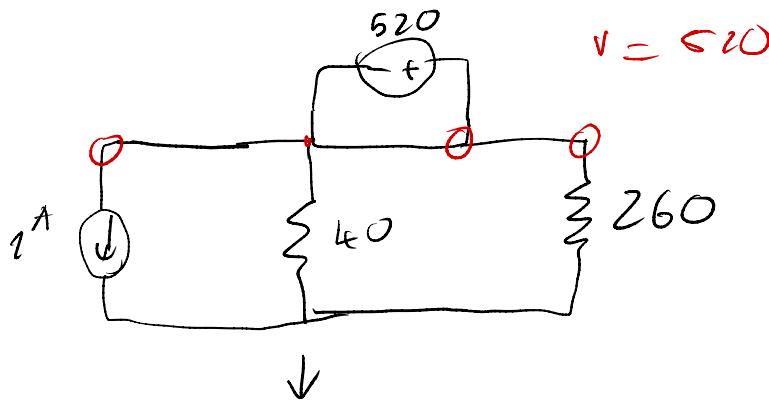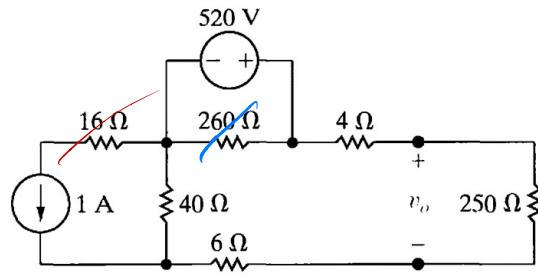


$$40 - 520 + 300i = 0$$

$$\rightarrow i = 1.6 \text{ A}$$

$$v_o = 1.6 \times 250 = 400 \checkmark$$


c) $P = 1 \times 520 = 520 \text{ W}$

4.61

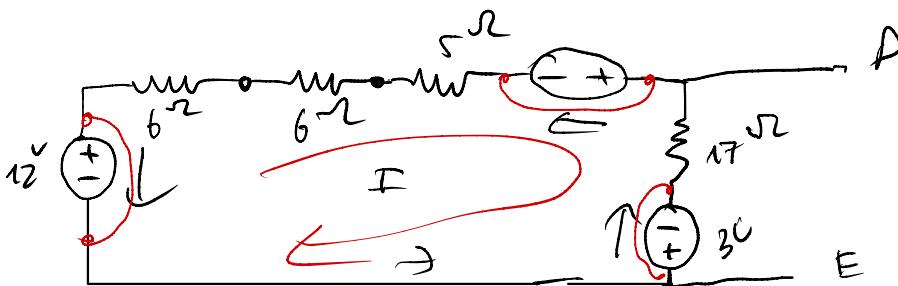

$$I = \frac{-12 - 5 - 34}{34} = -1.5 \text{ A}$$

$$R_{ED} = (6 + 6 + 5) // 17 = 8.5 \Omega$$

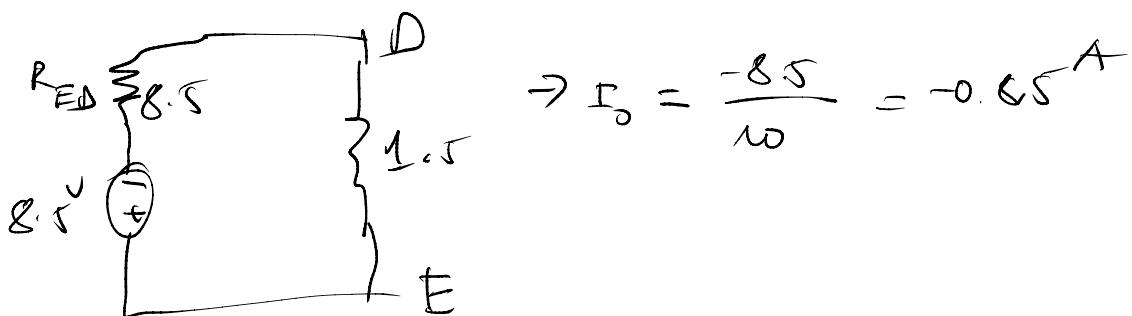




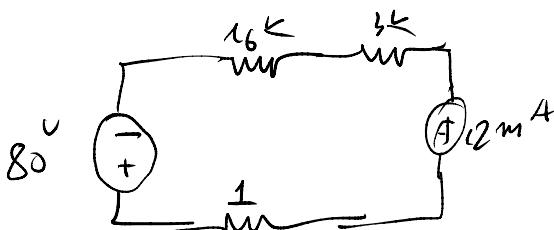
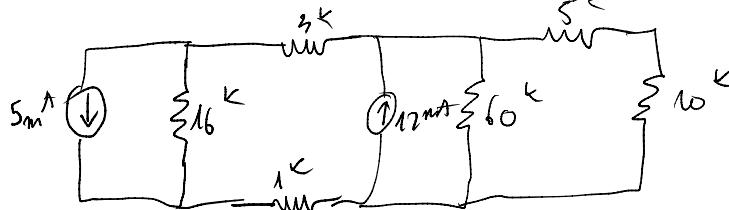
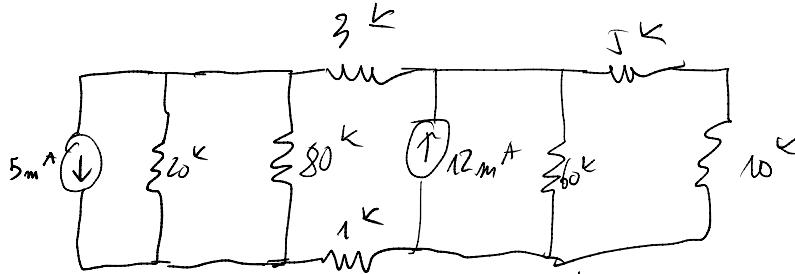
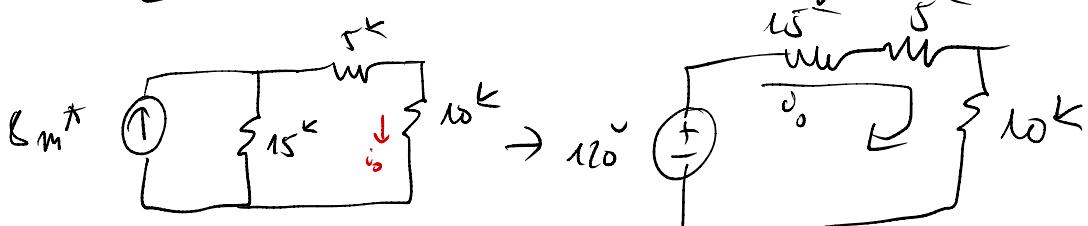
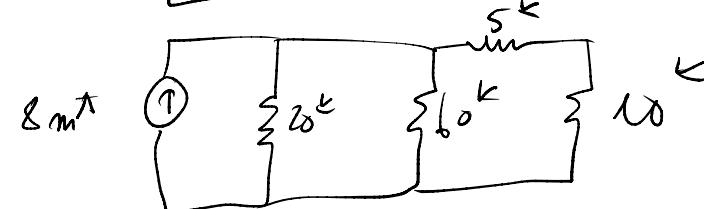
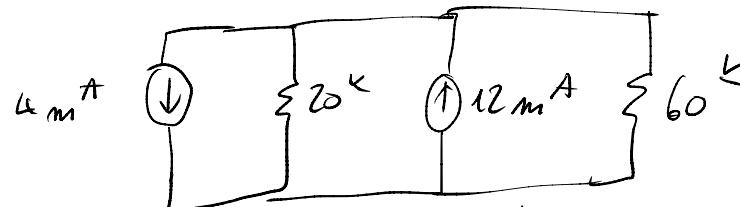
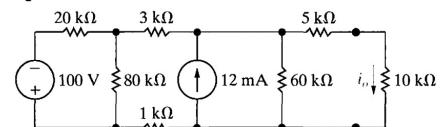
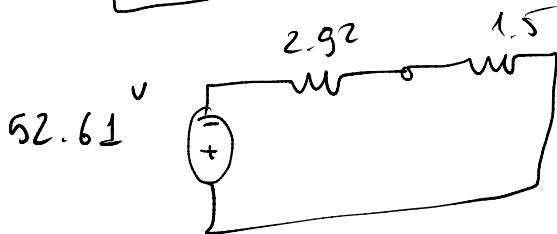
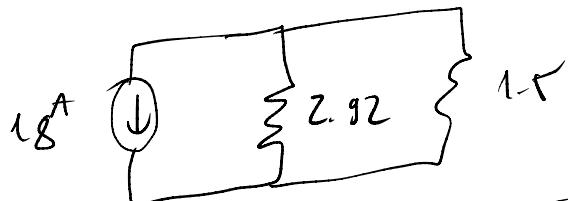


Figure P4.61


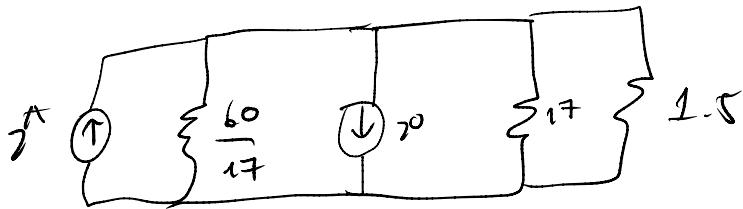


$$i_o = \frac{120}{30k} = 4mA$$

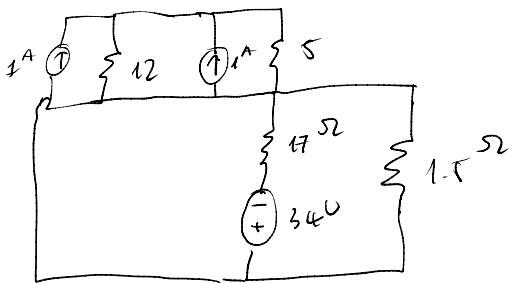




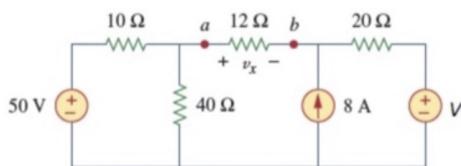


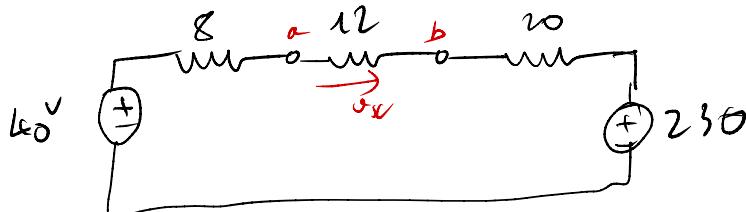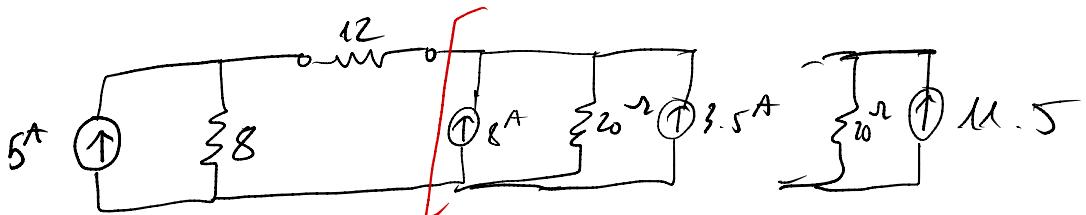The value of v_x in the given circuit is V.






$$I = \frac{40 - 230}{8 + 12 + 20} = -4.75 \text{ A}$$

$$v_x = 12 I = -57 \text{ V}$$

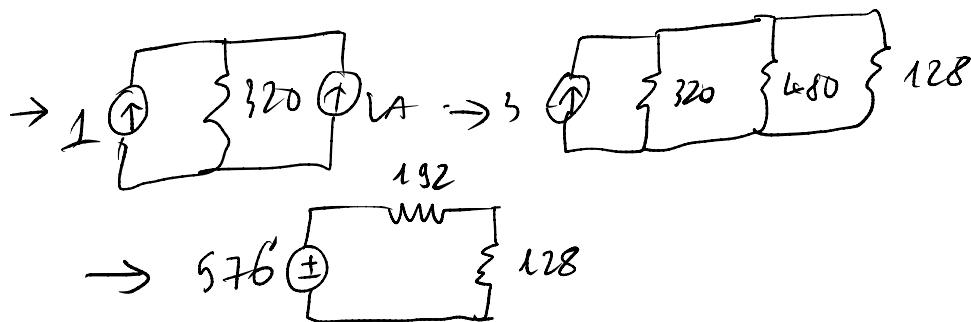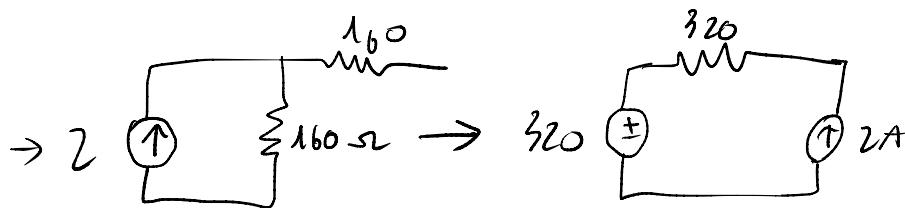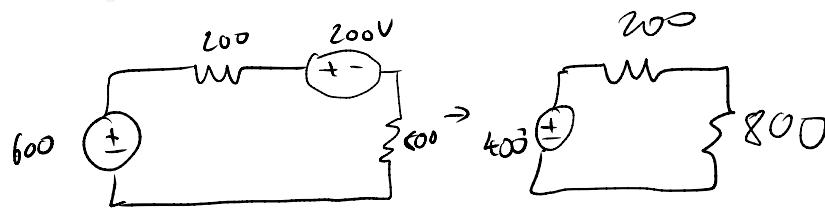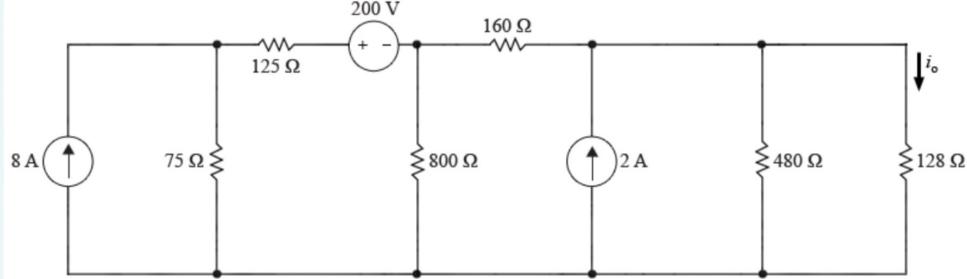
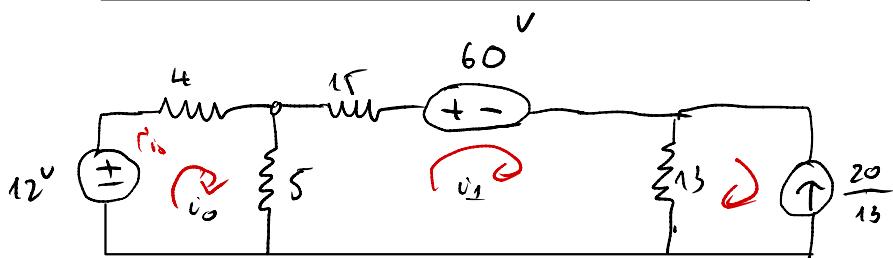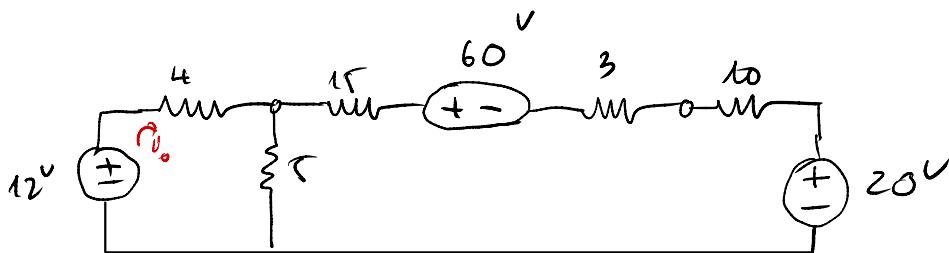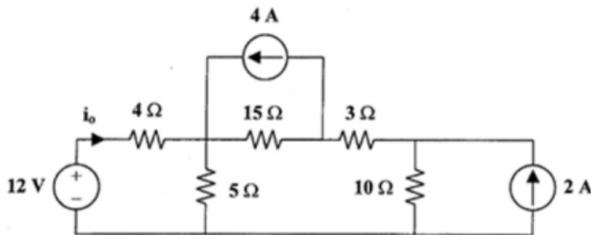
$$i_o = \frac{576}{192 + 128} = 1.8 \text{ A}$$







$$\begin{cases} 4i_0 + 5(i_0 + i_1) = 12 \\ 15i_1 + 5(i_1 - i_0) + 15(i_1 + \frac{20}{15}) = -60 \end{cases}$$

$$\textcircled{+} = \textcircled{-+} \Rightarrow \textcircled{\uparrow} = \textcircled{\rightarrow}$$

$$\textcircled{-} = \textcircled{+-} \Rightarrow \textcircled{\downarrow} = \textcircled{\leftarrow}$$

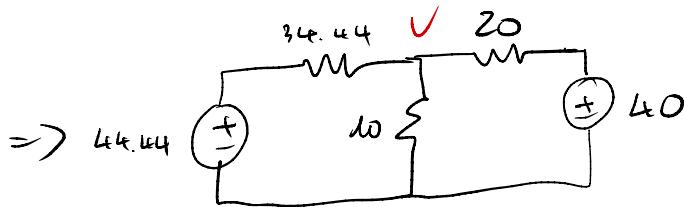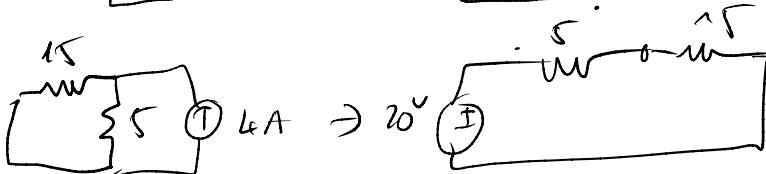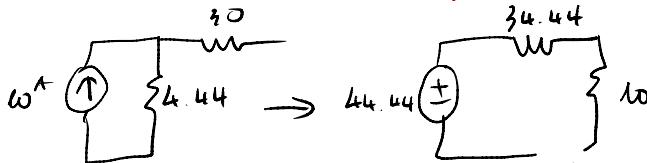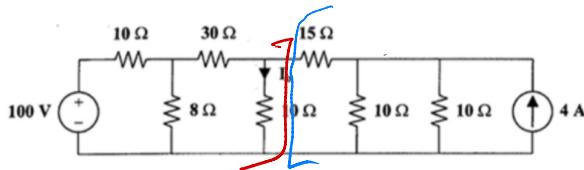P2-Use source transformation to find I_0 in the circuit below.



$$V = 12.8 \rightarrow I = 1.28^A$$

