

AC, DC
MM

Sinusoidal

Steady-State Analysis

We consider circuits energized by time-varying voltage or current sources.

Textbook:


Electric Circuits

James W. Nilsson & Susan A. Riedel

9th Edition.

Outline

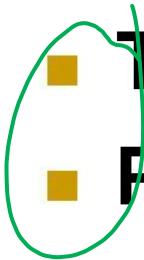- Complex Numbers Tutorial
- Sinusoids
- Phasors
- Techniques of Circuit Analysis
- Phasor Diagrams



Kirchhoff's Laws

The KCL and KVL are still applicable in the frequency domain.

Time domain

Frequency domain

$$\text{KVL} \quad v_1 + v_2 + \cdots + v_n = 0 \quad \Rightarrow \quad \mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0$$

$$\text{KCL} \quad i_1 + i_2 + \cdots + i_n = 0 \quad \Rightarrow \quad \mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_n = 0$$

For **KVL**, let v_1, v_2, \dots, v_n , be the voltages around a closed loop.

$$\Rightarrow v_1 + v_2 + \cdots + v_n = 0$$

In the sinusoidal steady state, each voltage may be written in cosine form.

$$\Rightarrow V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \cdots + V_{mn} \cos(\omega t + \theta_n) = 0$$

This can be written as

$$\text{Re}(V_{m1} e^{j\theta_1} e^{j\omega t}) + \text{Re}(V_{m2} e^{j\theta_2} e^{j\omega t}) + \cdots + \text{Re}(V_{mn} e^{j\theta_n} e^{j\omega t}) = 0$$

$$\Rightarrow \text{Re} \left[\left(V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2} + \cdots + V_{mn} e^{j\theta_n} \right) e^{j\omega t} \right] = 0$$

$$\Rightarrow \text{Re} \left[\left(\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n \right) e^{j\omega t} \right] = 0; \quad (\mathbf{V}_K = V_{mk} e^{j\theta_k})$$

$$\Rightarrow \mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0; \quad (\because e^{j\omega t} \neq 0 \quad \forall t)$$


⇒ KVL holds for phasor!

Similarly, KCL holds for phasor!

Series and Parallel Combination

$$L \rightarrow j\omega L$$
$$C \rightarrow \frac{1}{j\omega C}$$

Series Combination

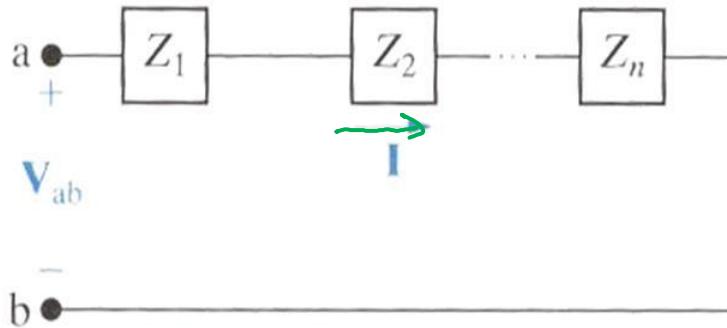


Voltage : KVL

$$\begin{aligned} V_{ab} &= Z_1 I + Z_2 I + \dots + Z_n I \\ &= (Z_1 + Z_2 + \dots + Z_n) I \end{aligned}$$

Equivalent impedance :

$$Z_{ab} = \frac{V_{ab}}{I} = Z_1 + Z_2 + \dots + Z_n$$

Parallel Combination

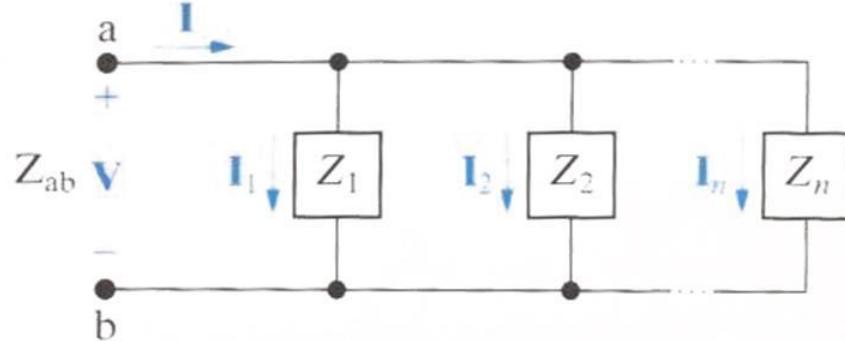


Current :

$$\underline{I = I_1 + I_2 + \dots + I_n = \frac{V}{Z_{ab}}}$$

Equivalent impedance :

$$\frac{1}{Z_{ab}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \quad \left| \quad Z_{ab} = \frac{Z_1 Z_2}{Z_1 + Z_2} \right.$$

Delta-to-Wye Simplifications

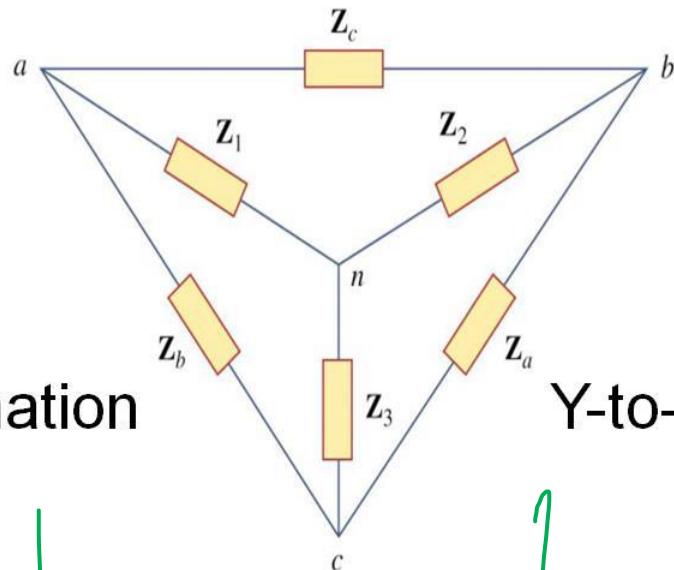

Δ-to-Υ transformation

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

Υ-to-Δ transformation


$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

Ex. 11 Find the input impedance of the circuit. Assume that the circuit operations at $\omega = 50$ rad/s.

transform time domain
→ phasor

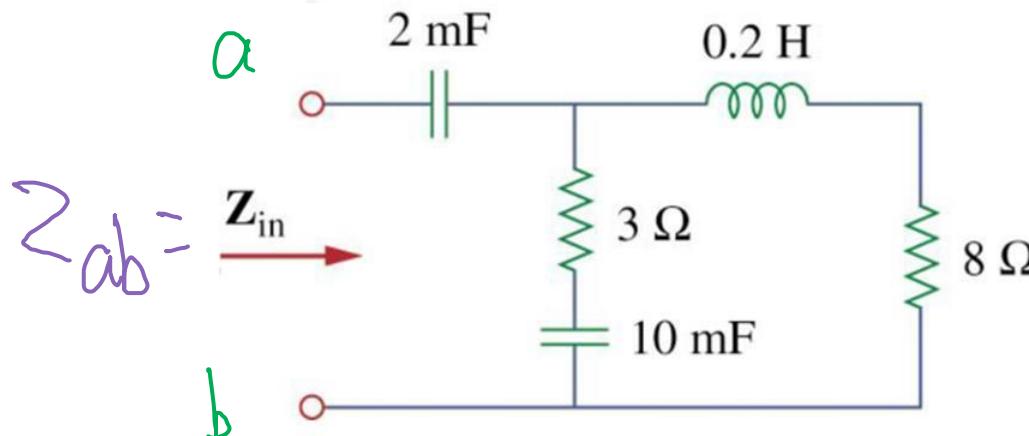

$$\begin{aligned}
 R &\rightarrow R \\
 L &\rightarrow j\omega L \\
 C &\rightarrow \frac{1}{j\omega C} = \frac{1}{\omega C}
 \end{aligned}$$

$$\left\{
 \begin{array}{l}
 R \rightarrow R \quad (\Omega) \\
 L \rightarrow j\omega L \quad (\Omega) \\
 C \rightarrow \frac{1}{j\omega C} \quad (\Omega)
 \end{array}
 \right.$$


Sol. of Ex. 11

$\omega = 50 \text{ rad/s}$

$$\mathbf{Z}_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$\mathbf{Z}_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$
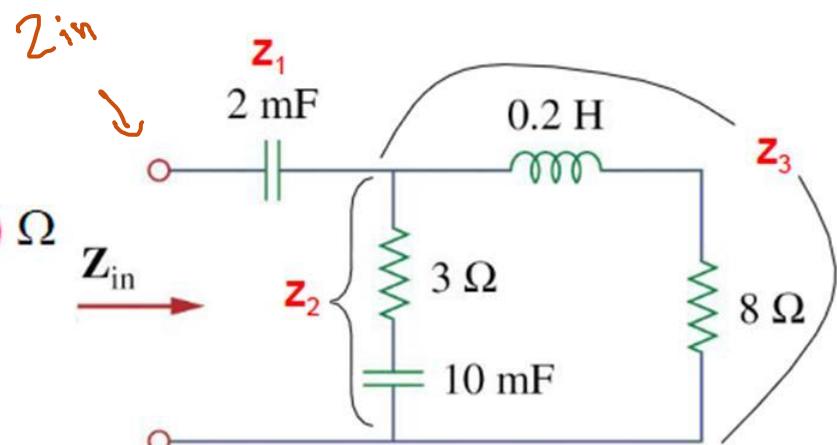
$$\mathbf{Z}_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$




The input impedance is

$$\begin{aligned} \Rightarrow \mathbf{Z}_{in} &= \mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3 = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8} \\ &= -j10 + \frac{(44 + j14)(11 - j8)}{11^2 + 8^2} = -j10 + 3.22 - j1.07 \Omega \\ &= 3.22 - j11.07 \Omega \end{aligned}$$

$$\frac{596 - j198}{185} = 3.22 - j1.07$$


Ex. 12

Determine $v_o(t)$ in the circuit.

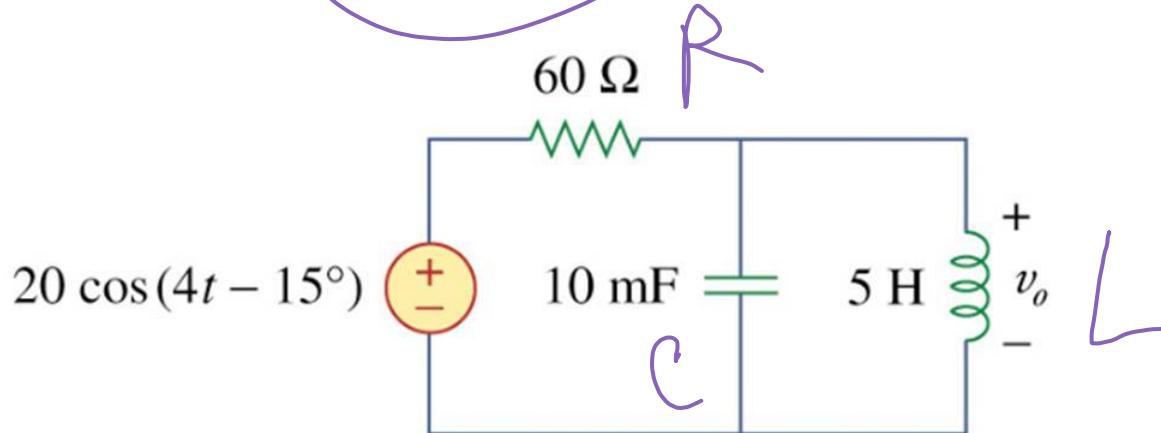

$$v_o(t) = A \cos(4t + \phi)$$

Sol. of Ex. 12

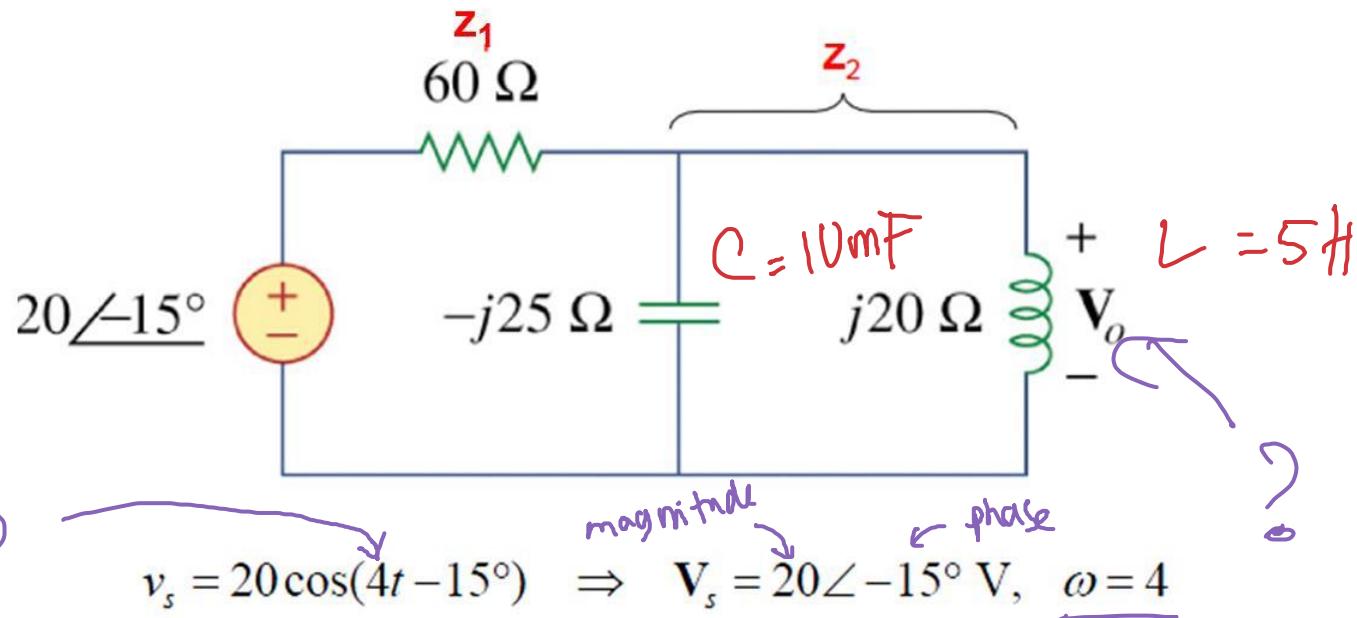

w

$$v_s = 20 \cos(4t - 15^\circ) \Rightarrow V_s = 20\angle-15^\circ \text{ V}, \omega = 4$$

magnitude phase

Find C : 10mF $\Rightarrow \frac{1}{j\omega C} = \frac{1}{j4 \times 10 \times 10^{-3}} = -j25\ \Omega$

Find L : 5 H $\Rightarrow j\omega L = j4 \times 5 = j20\ \Omega$

Let

Z_1 = Impedance of the $60\text{-}\Omega$ resistor; Z_2 = Impedance of the parallel combination of the 10 mF capacitor and the 5-H inductor

Then $Z_1 = 60\ \Omega$ and

$$Z_2 = -j25 \parallel j20 = \frac{-j25 \times j20}{-j25 + j20} = j100\ \Omega$$

$$= \frac{500}{-j5} = \frac{1}{-j} 100 = j100\ \Omega$$

Sol. of Ex. 12 Cont.

By the voltage-division principle,

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{j100}{60 + j100} \times (20 \angle -15^\circ) \rightarrow 116.62 \angle 59.04^\circ = (0.8575 \angle 30.96^\circ) \times (20 \angle -15^\circ) = 17.15 \angle 15.96^\circ \text{ V}$$

$$C = \sqrt{(0.735)^2 + (0.491)^2} \quad \tan^{-1} \frac{0.491}{0.735}$$

Convert this to the time domain and obtain

$$v_o(t) = 17.15 \cos(4t + 15.96^\circ) \text{ V}$$

$$\frac{j100(60 - j100)}{60^2 + 100^2} = \frac{j6000}{13600} + \frac{10000}{13600}$$

$$R = 0.735 + j0.491$$

Techniques of Circuit Analysis

- Techniques of circuit analysis introduced in Lecture 3 – 4 such as:
 - Source transformations
 - The node-voltage method
 - The mesh-current method
 - Superposition
 - Thevenin – Norton equivalent
- also can be applied to frequency-domain circuits.
- The validity of these techniques is followed the same process used in lectures 3-4 except that we substitute impedance (Z) for resistance (R).
- Many examples are shown in textbook.

Techniques of Circuit Analysis

- In steady-state circuit response with sinusoidal excitation, the phasor method enables the R , L , C as an element of impedance whose function is the same as a resistor such that **generalized Ohm's law** can be applied.
- Hence, all circuit **analysis methods** (Nodal, Mesh), **theorems** (Superposition, Source transformation, Thevenin and Norton equivalent circuits) can be applied to analyze ac circuits.


Steps to Analyze AC Circuits

- Steps to Analyze AC Circuits:
 1. Transform the circuit to the **phasor** or **frequency domain**.
 2. Solve the problem using **circuit techniques** (**nodal analysis**, **mesh analysis**, **superposition**, etc.).
 3. Transform the resulting **phasor** to the **time domain**.

Ex. 13 - Nodal Analysis


Find i_x in the circuit using nodal analysis.

transform top hasor first

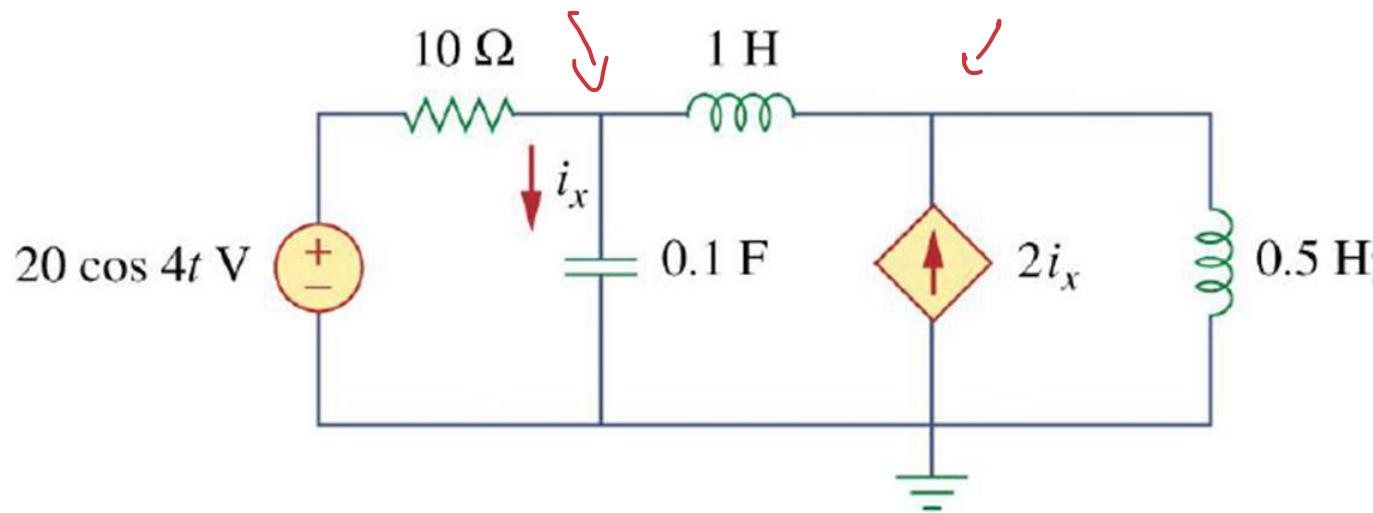

2 nodes \rightarrow 2 equations

Sol. of Ex. 13:

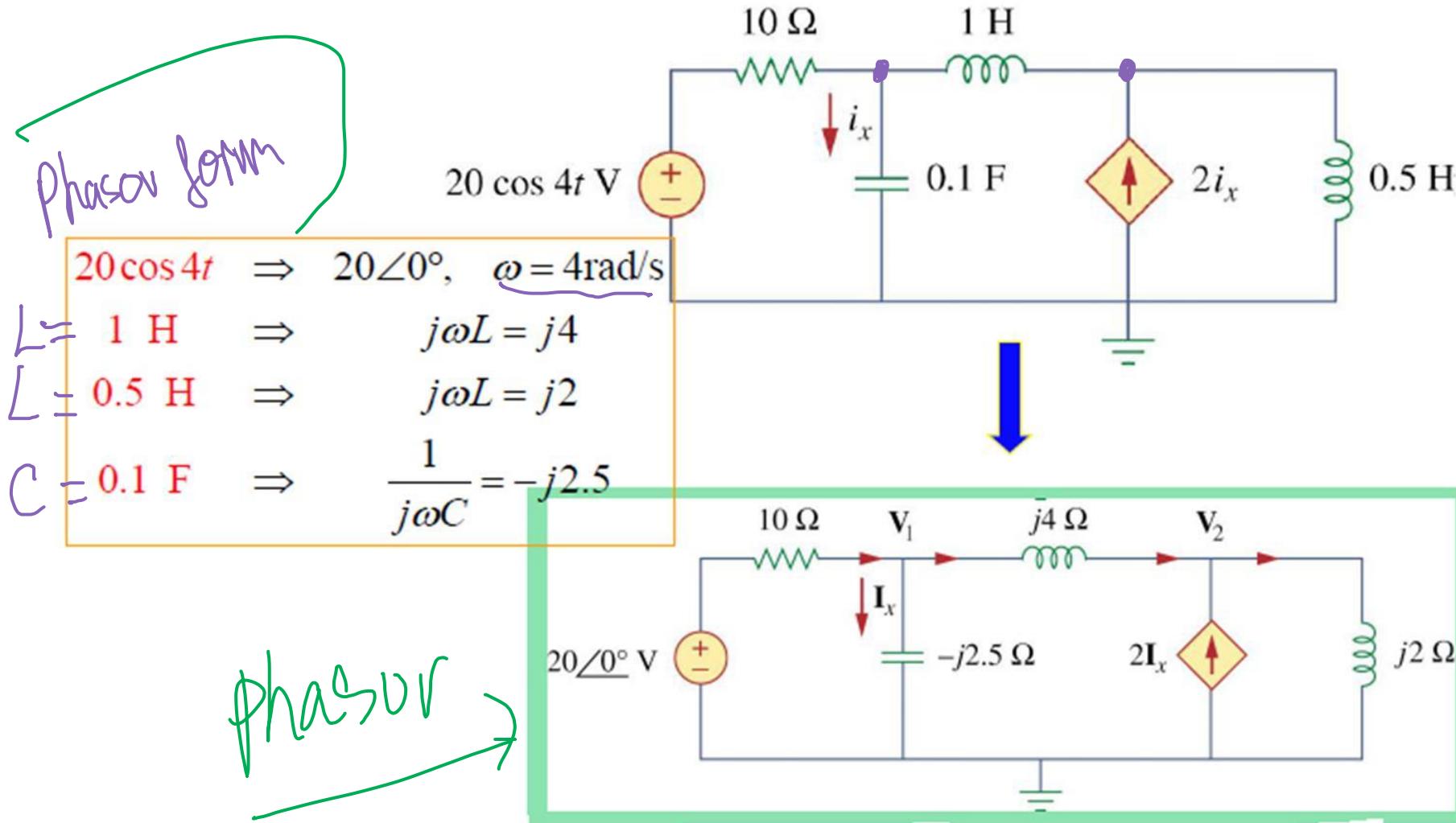

Sol. of Ex. 13:

$$10(20 - V_1) = 40j(V_1) - (V_1 - V_2)25j$$

$$\text{or } 200 - 10V_1 = 40V_1j - 25V_1j + 25V_2j$$


• KCL at node 1

$$\frac{20 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4}$$

$$\Rightarrow (1 + j1.5)V_1 + j2.5V_2 = 20 \cdots (a)$$

• KCL at node 2

$$2I_x = \frac{2V_1}{-j2.5}$$

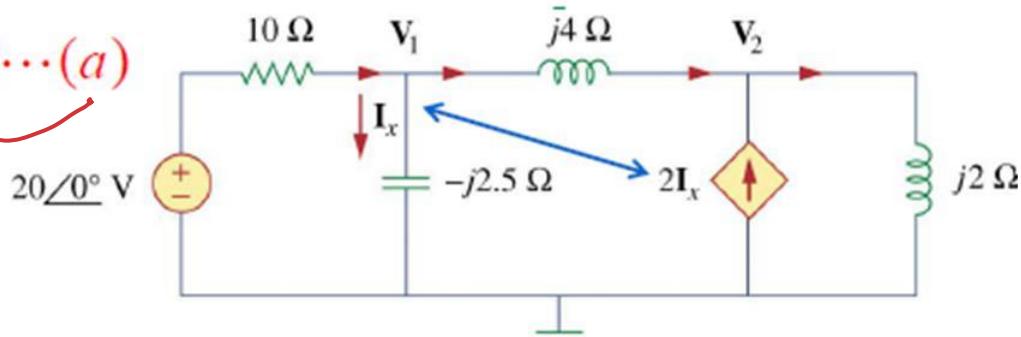


$$2I_x + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}$$

$$\Rightarrow \frac{2V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = \frac{V_2}{j2}; \quad (I_x = V_1 / -j2.5,)$$

$$\Rightarrow 11V_1 + 15V_2 = 0 \cdots (b)$$

Sol. of Ex. 13:
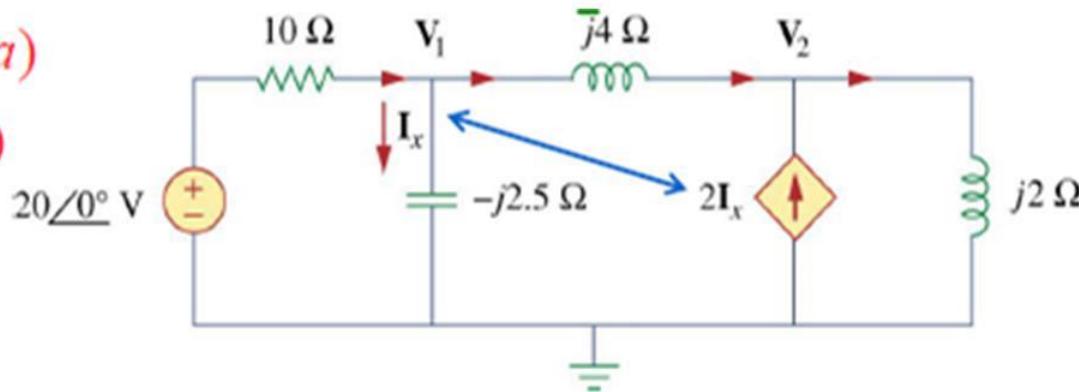
$$\begin{cases} (1+j1.5)V_1 + j2.5V_2 = 20 \dots (a) \\ 11V_1 + 15V_2 = 0 \dots (b) \end{cases}$$



By (a) and (b) \Rightarrow


$$V_1 = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$

$$V_2 = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$

$$I_x = \frac{V_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$

$$\Rightarrow i_x(t) = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

Ex. 14: Compute V_1 & V_2 in the circuit

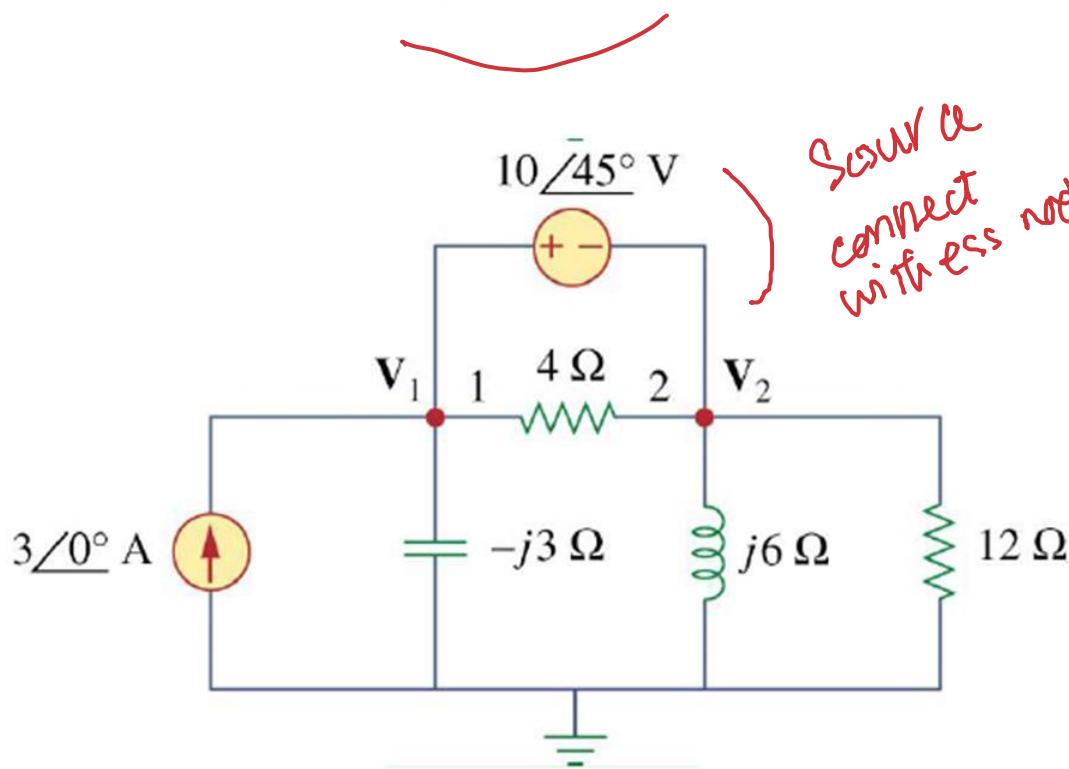

Source & connect with less nodes => Supernode


$\text{V}_0 \text{ is } \omega \Rightarrow \text{find } \text{V}_0$
 $\text{V}_0 \text{ can change}$

Sol. of Ex. 14:

KCL at supernode:

$$3 = \frac{\mathbf{V}_1}{-j3} + \frac{\mathbf{V}_2}{j6} + \frac{\mathbf{V}_2}{12}$$
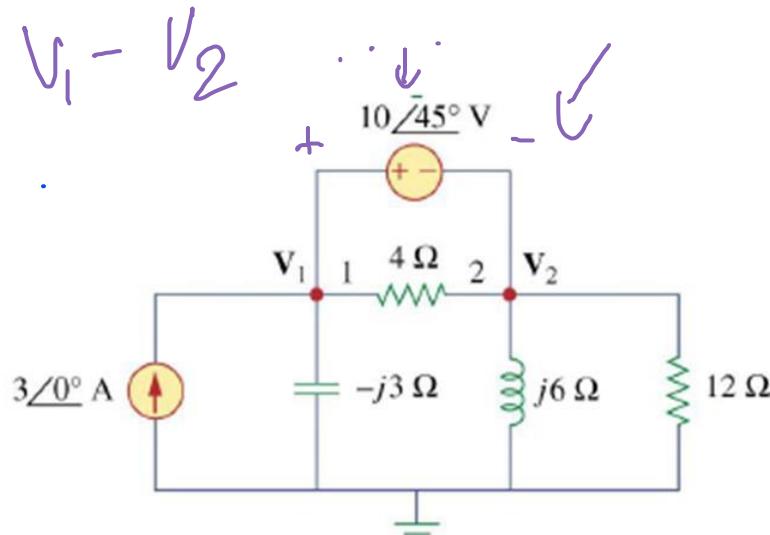
$$\Rightarrow 36 = j4\mathbf{V}_1 + (1 - j2)\mathbf{V}_2 \cdots (a)$$



At supernode:

$$\mathbf{V}_1 = \mathbf{V}_2 + 10\angle 45^\circ \cdots (b)$$

$$V_1 - V_2 = 10 \angle 45^\circ$$


By (a) and (b) \Rightarrow

$$\mathbf{V}_2 = 31.41 \angle -87.18^\circ \text{ V}$$

so,



$$\mathbf{V}_1 = \mathbf{V}_2 + 10\angle 45^\circ$$

$$= 25.87 \angle -70.48^\circ \text{ V}$$

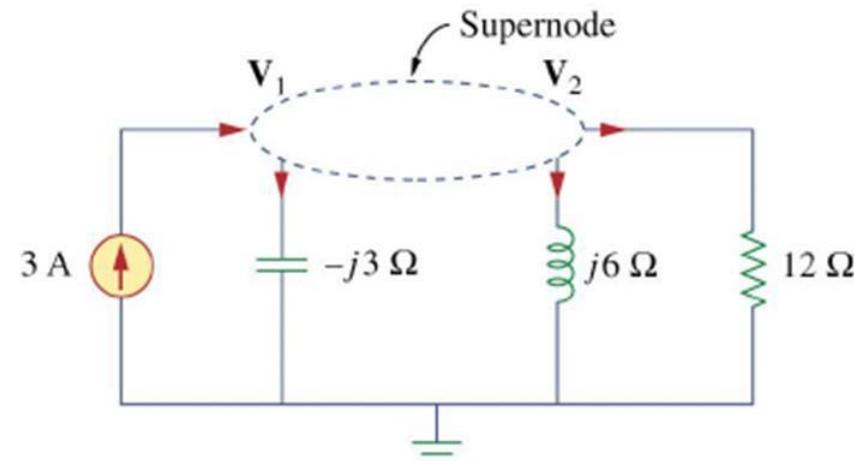

Ex. 15: Mesh Analysis

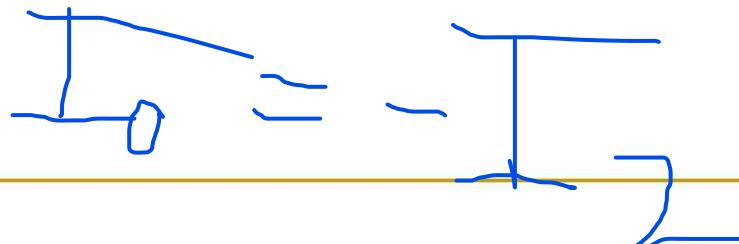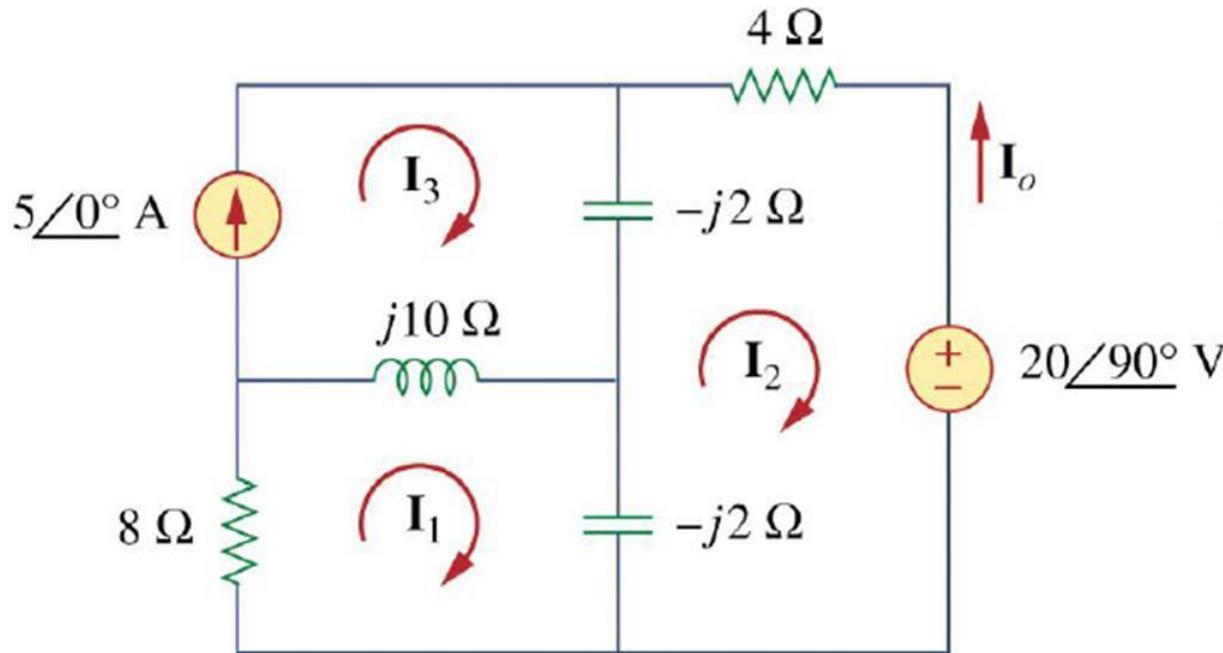Determine current I_o in the circuit using mesh analysis.



Sol. of Ex. 15:

KVL for mesh 1: $(8 + j10 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - j10\mathbf{I}_3 = 0$


KVL for mesh 2: $(4 - j2 - j2)\mathbf{I}_2 - (-j2)\mathbf{I}_1 - (-j2)\mathbf{I}_3 + 20\angle 90^\circ = 0$

For mesh 3: $\mathbf{I}_3 = 5$

$$\Rightarrow \begin{cases} (8 + j8)\mathbf{I}_1 + j2\mathbf{I}_2 = j50 \dots \dots \dots (a) \\ j2\mathbf{I}_1 + (4 - j4)\mathbf{I}_2 = -j20 - j10 \dots (b) \end{cases}$$


$$\Rightarrow \mathbf{I}_2 = 6.12\angle -35.22^\circ \text{ A}$$

$$\mathbf{I}_o = -\mathbf{I}_2 = 6.12\angle 144.78^\circ \text{ A}$$

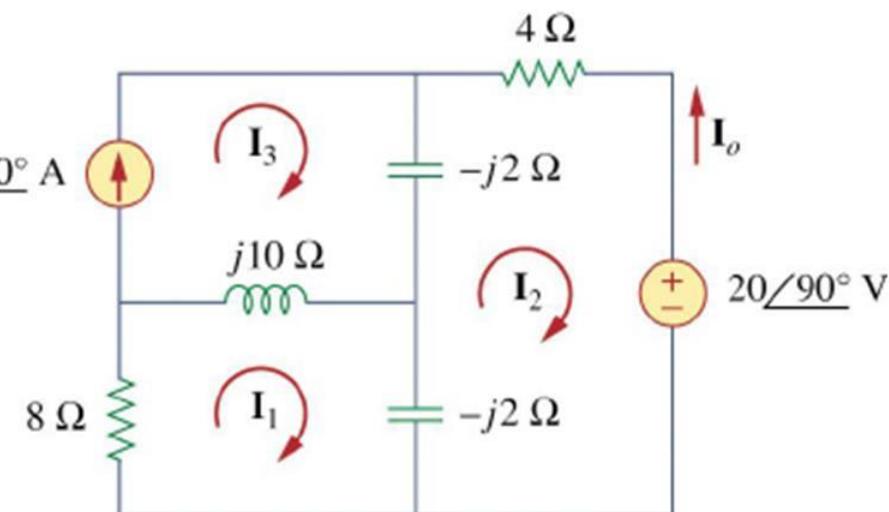

Ex. 16: Mesh Analysis – super mesh

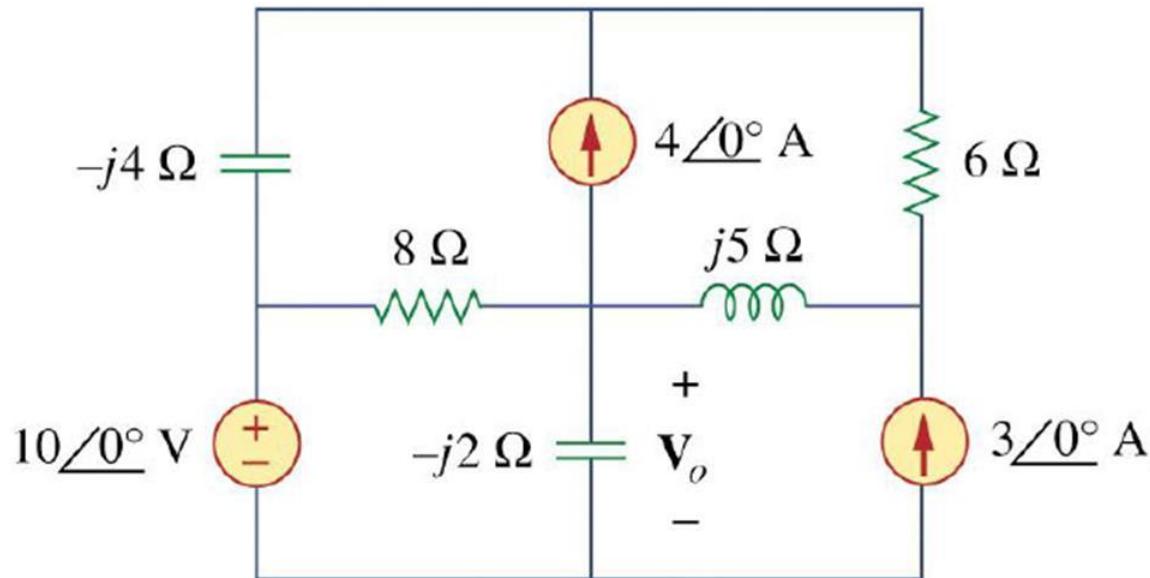Solve V_o in the circuit using mesh analysis



Sol. of Ex. 16:

$$\text{KVL for mesh 1: } -10 + (8 - j2)\mathbf{I}_1 - (-j2)\mathbf{I}_2 - 8\mathbf{I}_3 = 0 \cdots (a)$$

$$\text{KVL for supermesh: } (8 - j4)\mathbf{I}_3 - 8\mathbf{I}_1 + (6 + j5)\mathbf{I}_4 - j5\mathbf{I}_2 = 0 \cdots (b)$$

$$\text{For mesh 2: } \mathbf{I}_2 = -3 \cdots (c)$$


Because of the current source between meshes 3 and 4,
at node $A \Rightarrow \mathbf{I}_4 = \mathbf{I}_3 + 4 \cdots (d)$

By $(a) \sim (d)$

$$\Rightarrow \mathbf{I}_1 = 3.618 \angle 274.5^\circ \text{ A}$$


Hence,

$$\begin{aligned}\mathbf{V}_o &= -j2(\mathbf{I}_1 - \mathbf{I}_2) = -j2(3.618 \angle 274.5^\circ + 3) \\ &= -7.2134 - j6.568 = 9.756 \angle -137.68^\circ \text{ V}\end{aligned}$$

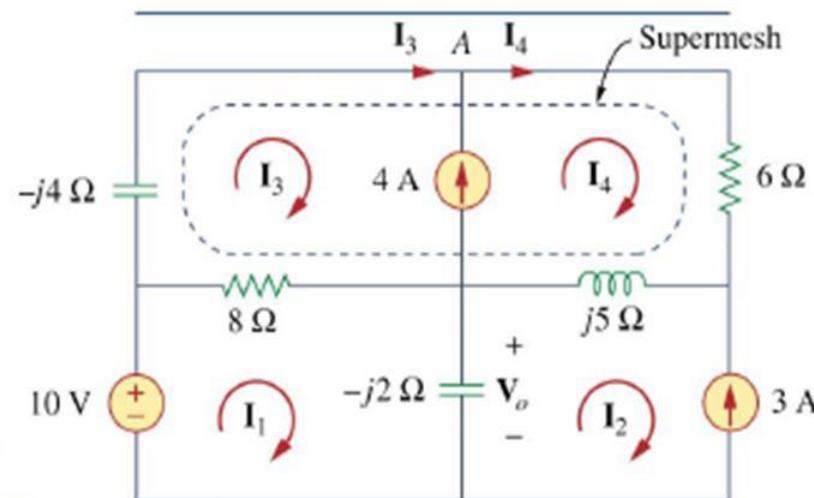


Ex. 17: Superposition Theorem

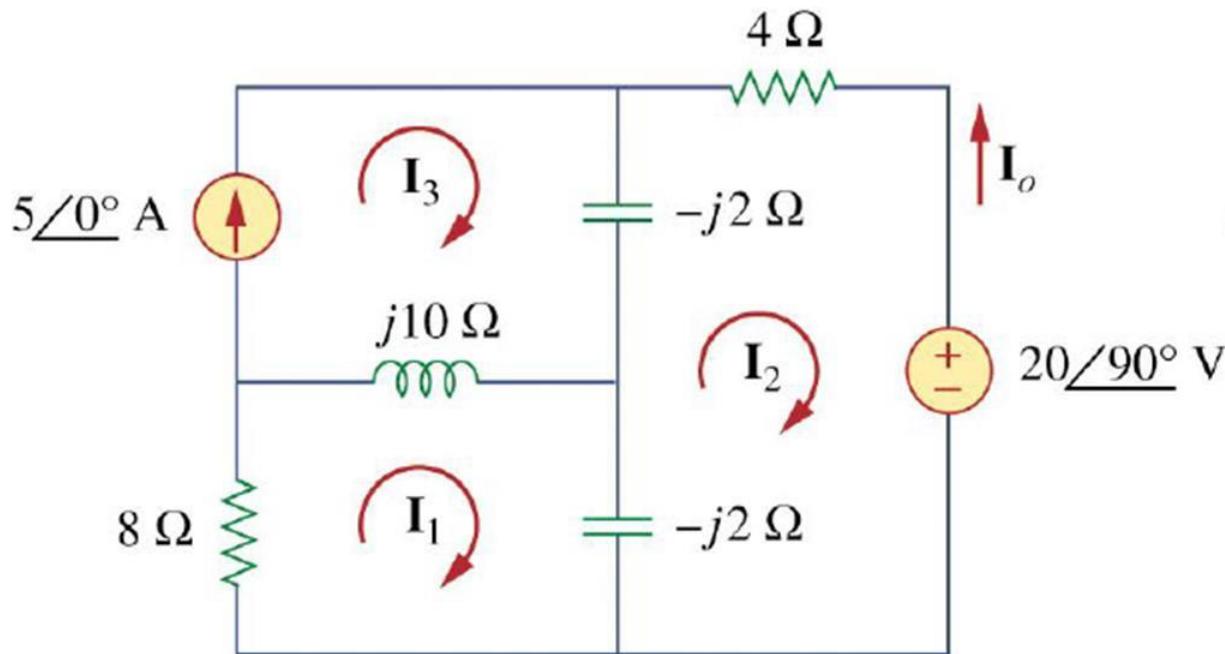Use the superposition theorem to find I_o in the circuit.



Sol. of Ex. 17: Superposition Theorem

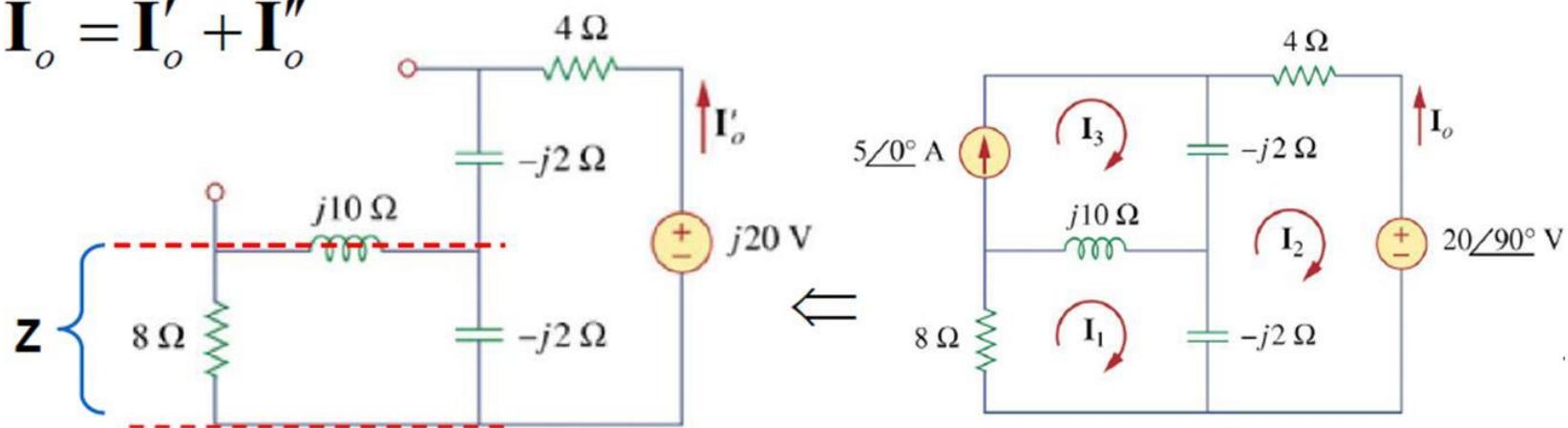
$$\text{Let } \mathbf{I}_o = \mathbf{I}'_o + \mathbf{I}''_o$$



For \mathbf{I}'_o

$$Z = \frac{-j2(8+j10)}{-2j+8+j10} = 0.25 - j2.25$$
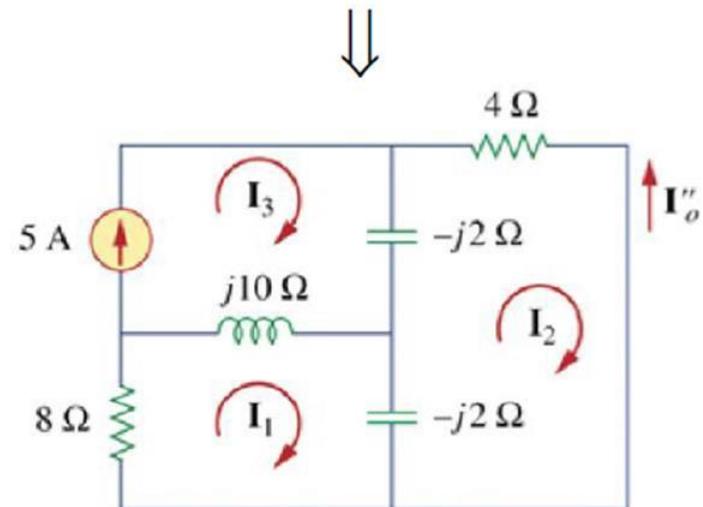
$$\begin{aligned} \mathbf{I}'_o &= \frac{j20}{4 - j2 + Z} = \frac{j20}{4.25 - j4.25} \\ &= -2.353 + j2.353 \end{aligned}$$



Sol. of Ex. 17: cont.

For \mathbf{I}_o''

$$\text{KVL for mesh 1: } (8 + j8)\mathbf{I}_1 - j10\mathbf{I}_3 + j2\mathbf{I}_2 = 0 \cdots (a)$$

$$\text{KVL for mesh 2: } (4 - j4)\mathbf{I}_2 + j2\mathbf{I}_1 + j2\mathbf{I}_3 = 0 \cdots (b)$$


$$\text{For mesh 3: } \mathbf{I}_3 = 5 \cdots (c)$$

$$\Rightarrow \mathbf{I}_2 = \frac{90 - j40}{34} = 2.647 - j1.176$$

$$\mathbf{I}_o'' = -\mathbf{I}_2$$


Hence,

$$\begin{aligned} \mathbf{I}_o &= \mathbf{I}_o' + \mathbf{I}_o'' = -5 + j3.529 \\ &= 6.12 \angle 144.78^\circ \text{ A} \end{aligned}$$

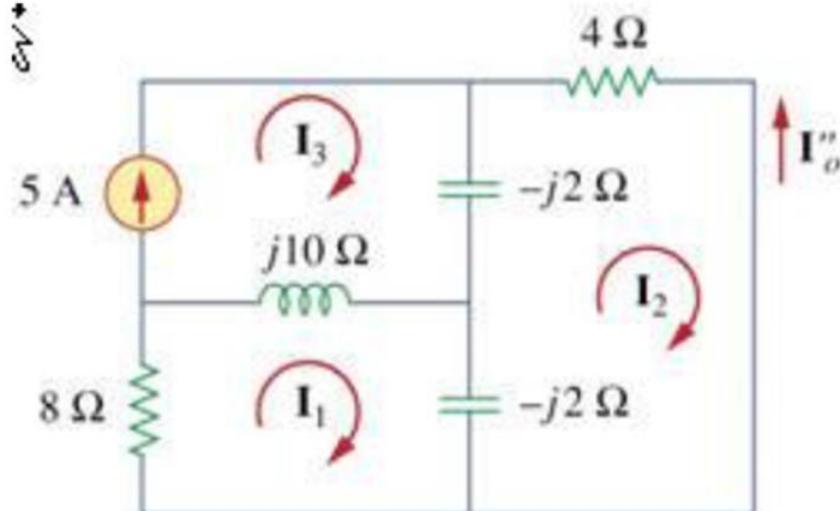

Ex. 18: Superposition Theorem

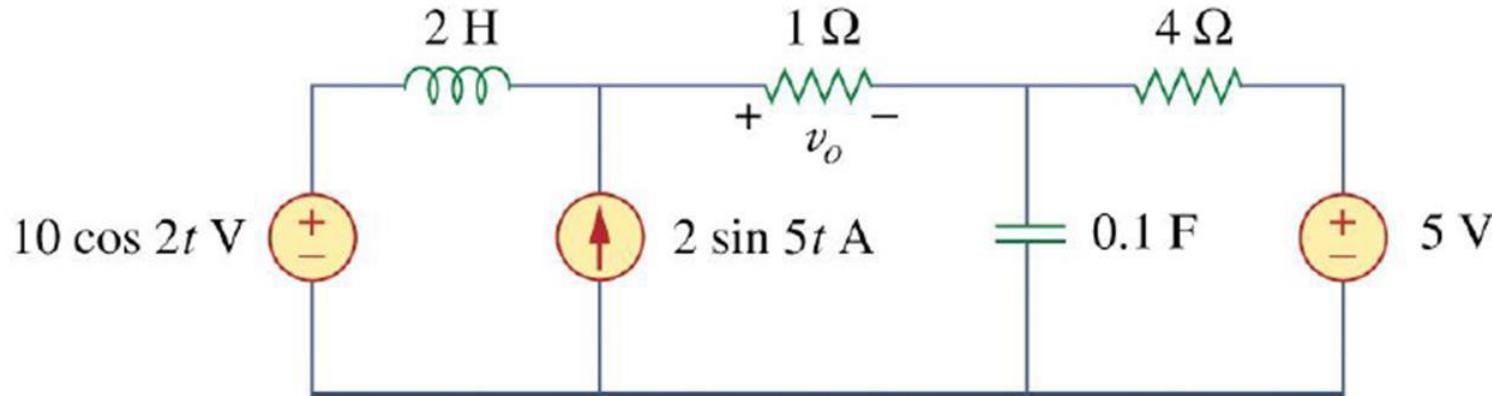Find v_o of the circuit using the superposition theorem.







Sol. of Ex. 18:

Let $v_o = v_1 + v_2 + v_3$

For DC, $j\omega L$, because $\omega = 0 \rightarrow$ short circuit

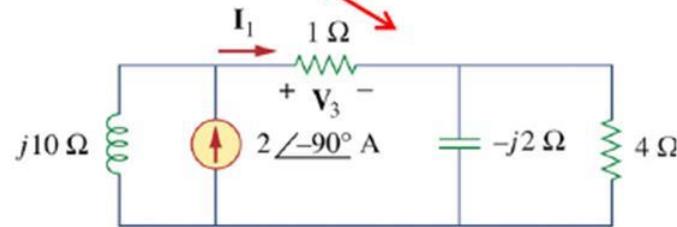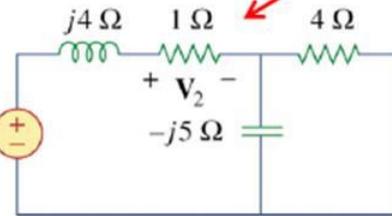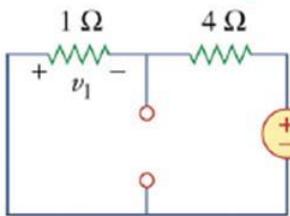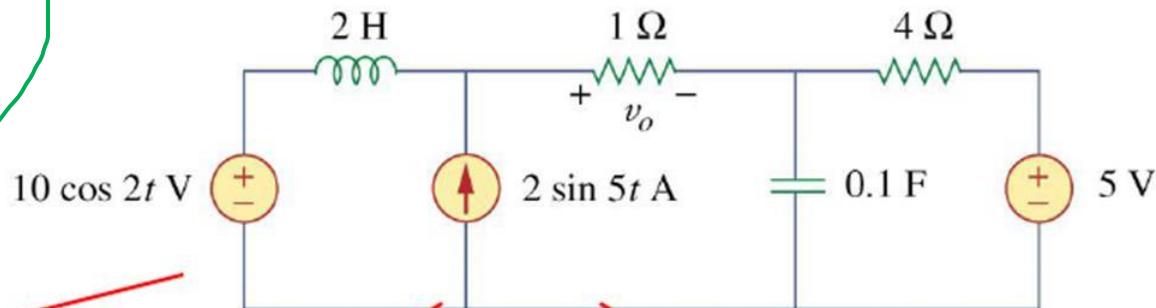For DC, $\frac{1}{j\omega C}$, because $\omega = 0 \rightarrow$ opened



(a)

(b)

(c)

AC

AC


By voltage division $\Rightarrow -v_1 = \frac{1}{1+4} \times 5 = 1 \text{ V}$

Sol. of Ex. 18: cont.

$$10\cos 2t \Rightarrow 10\angle 0^\circ, \omega = 2 \text{ rad/s}$$

$$2 \text{ H} \Rightarrow j\omega L = j4 \Omega$$
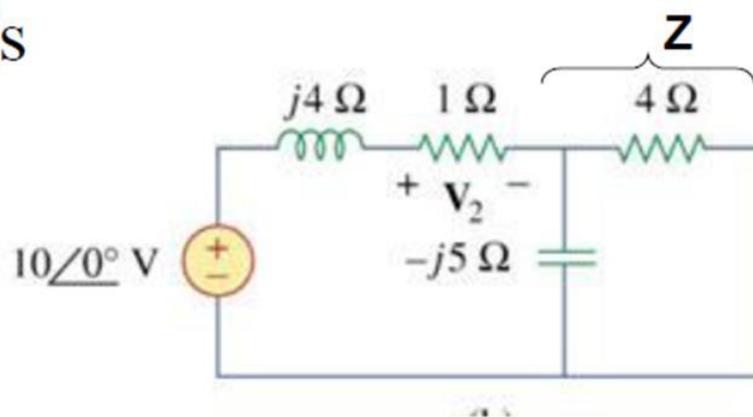
$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega L} = -j5 \Omega$$



- Let

$$Z = -j5 \parallel 4 = \frac{-j5 \times 4}{4 - j5} = 2.439 - j1.951$$

- By division,

$$V_2 = \frac{1}{1 + j4 + Z} (10\angle 0^\circ) = \frac{10}{3.439 + j2.049} = 2.498\angle -30.79^\circ$$

$$v_2 = \underline{2.498 \cos(2t - 30.79^\circ)}$$


Sol. of Ex. 18: cont.

$$2\sin 5t \Rightarrow 2\angle -90^\circ, \omega = 5 \text{ rad/s}$$

$$2 \text{ H} \Rightarrow j\omega L = j10 \Omega$$

$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega L} = -j2 \Omega$$
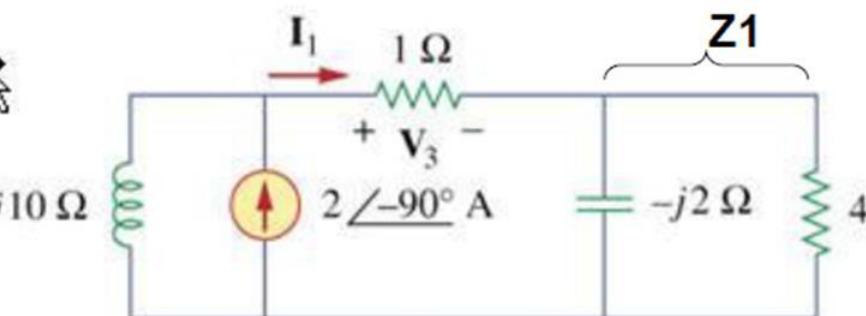
$$\text{Let } \mathbf{Z}_1 = -j2 \parallel 4 = \frac{-j2 \times 4}{4 - j2} = 0.8 - j1.6 \Omega$$



By current division $\mathbf{I}_1 = \frac{j10}{j10 + 1 + \mathbf{Z}_1} (2\angle -90^\circ) \text{ A}$


$$\Rightarrow \mathbf{V}_3 = \mathbf{I}_1 \times 1 = \frac{j10}{1.8 + j8.4} (-j2) = 2.328\angle 80^\circ \text{ V}$$

$$v_3 = 2.33 \cos(5t - 80^\circ) = 2.33 \sin(5t + 10^\circ) \text{ V}$$

$$v_0(t) = -1 + 2.498 \cos(2t - 30.79^\circ) + 2.33 \sin(5t + 10^\circ) \text{ V}$$


Ex. 19: Source Transformation

$$\mathbf{V}_s = \mathbf{Z}_s \mathbf{I}_s \quad \Leftrightarrow \quad \mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}_s}$$

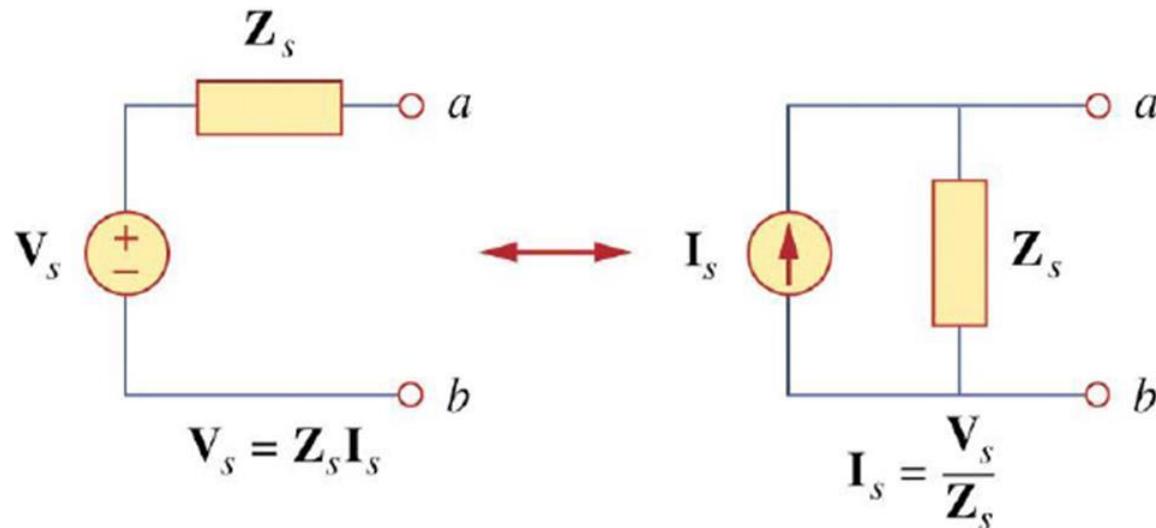


Ex. 19: Source Transformation

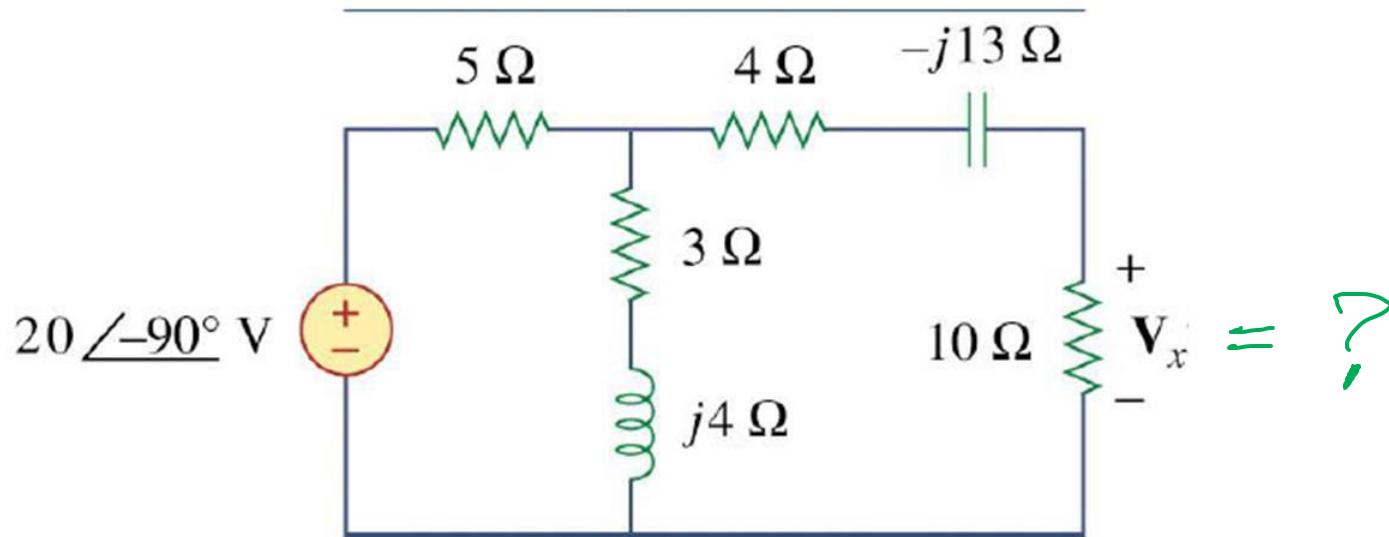Calculate V_x in the circuit using the method of source transformation.



Sol. of Ex. 19:

Find V_1

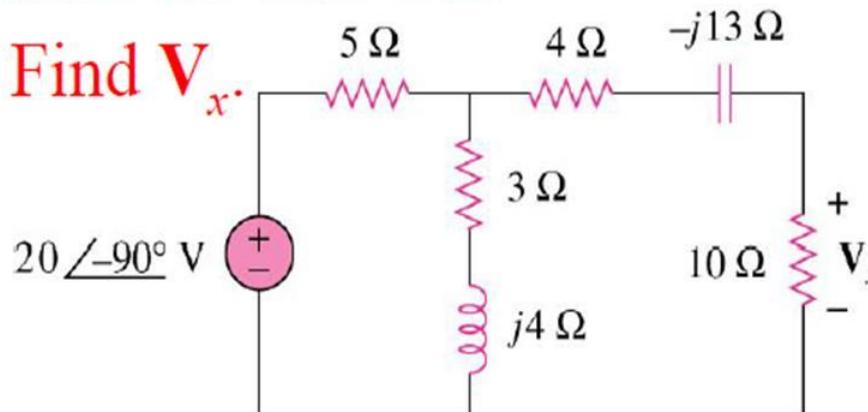



$$\mathbf{I}_s = \frac{20 \angle -90^\circ}{5} = 4 \angle -90^\circ = -j4$$

$$\mathbf{V}_s = \mathbf{I}_s \times (5 \parallel (3 + j4)) = -j4 \frac{5(3 + j4)}{8 + j4} = -j4(2.5 + j1.25) = 5 - j10$$

By voltage division,

$$\mathbf{V}_x = \frac{10}{2.5 + j1.25 + 4 - j13 + 10} (5 - j10)$$



$$= 5.519 \angle -28^\circ \text{ V}$$

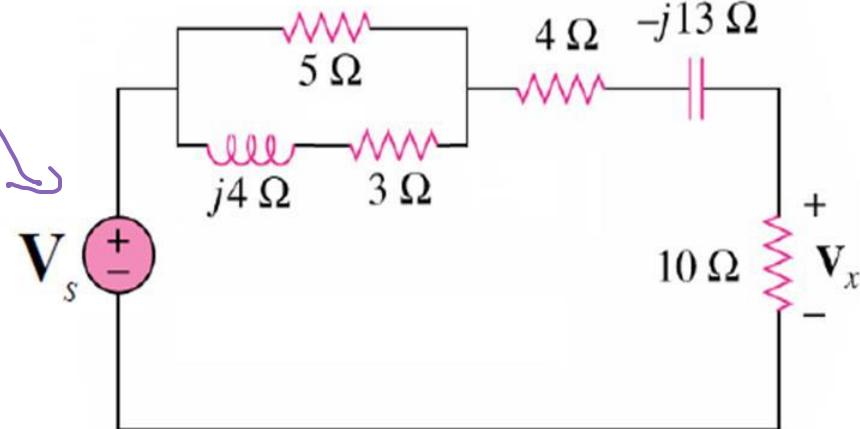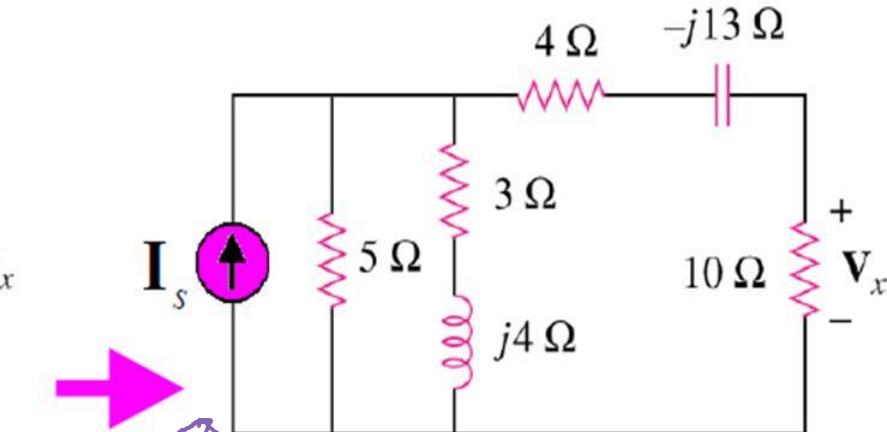



Ex. 20: Thevenin & Norton Equivalent Circuits

$$V_{TH} = Z_N I_N,$$

$$Z_{TH} = Z_N$$

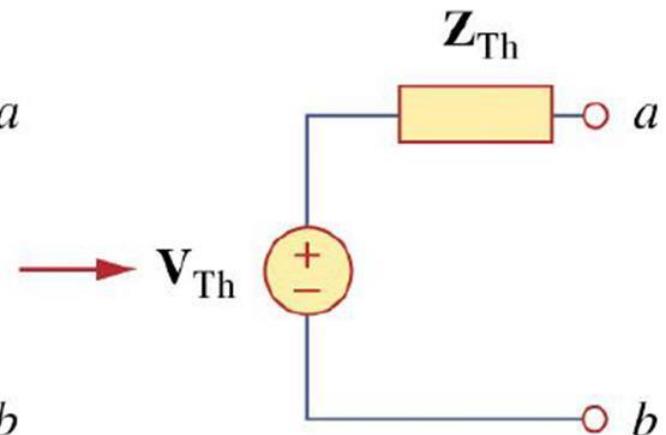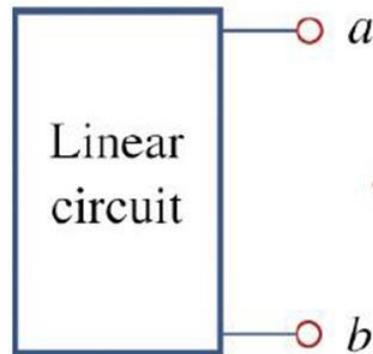


$$Z_{TH} = Z_N = \frac{V_{TH}}{I_N}$$

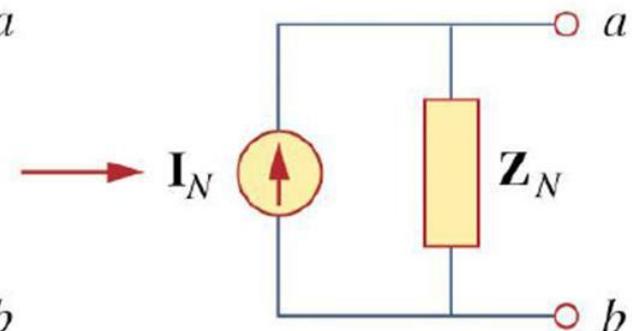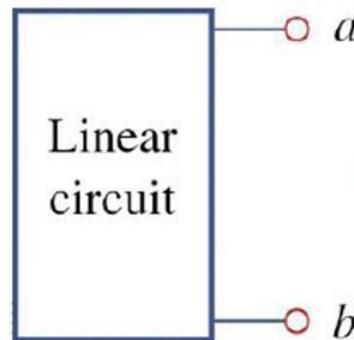


Ex. 20: Thevenin & Norton Equivalent Circuits

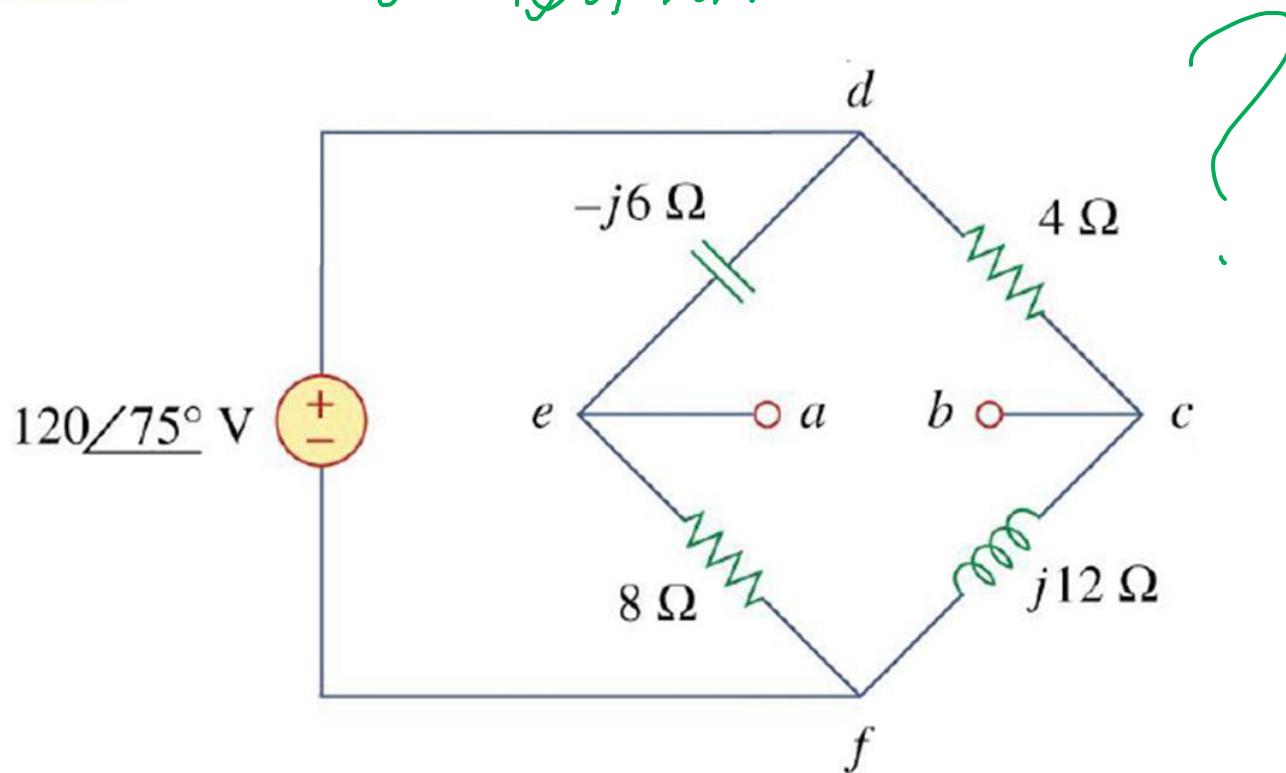Obtain the Thevenin equivalent at terminals $a-b$ of the circuit. *Ko držím kružnici*





Sol. of Ex. 20:

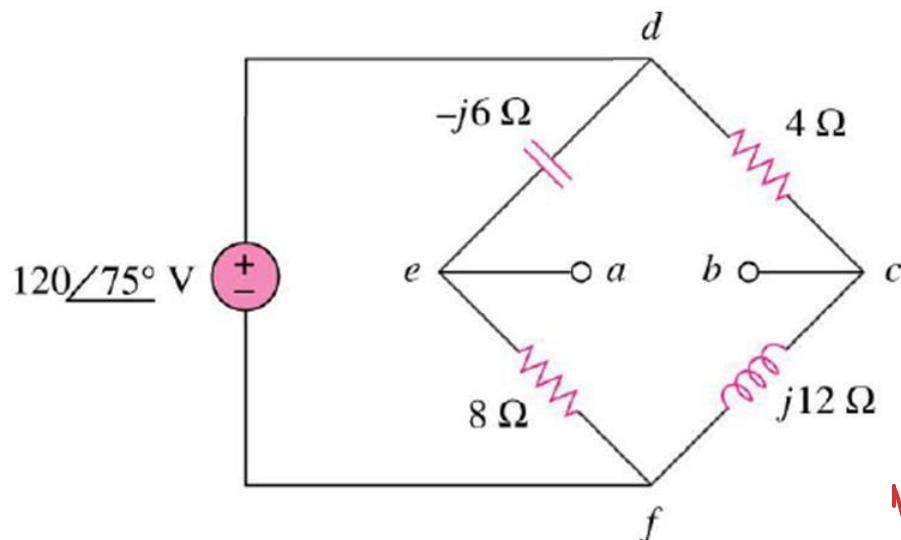


$$\begin{aligned} Z_{Th} &= (8 \parallel -j6) + (4 \parallel j12) \\ &= 6.48 - j2.64 \end{aligned}$$

$$\begin{aligned} V_{Th} &= \left(\frac{8}{8-j6} - \frac{j12}{4+j12} \right) \times 120 \angle 75^\circ \\ &= 37.95 \angle 220.31^\circ \text{ V} \end{aligned}$$

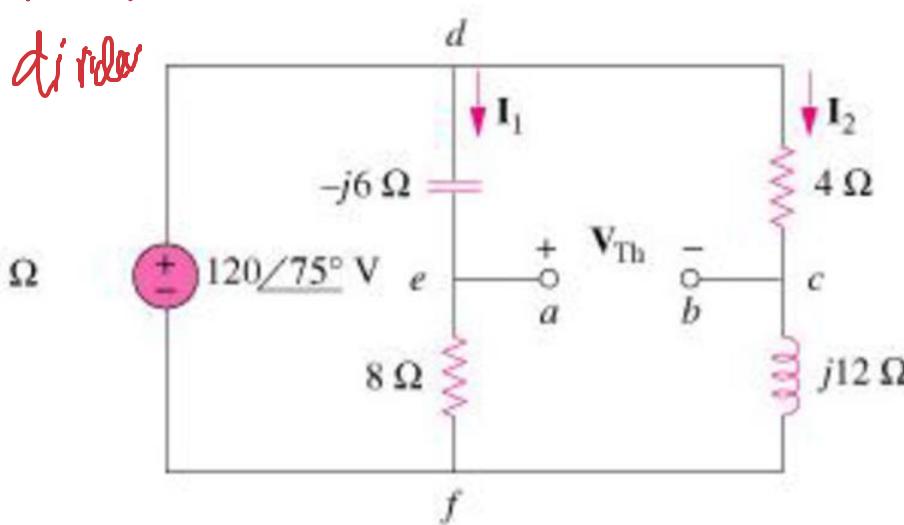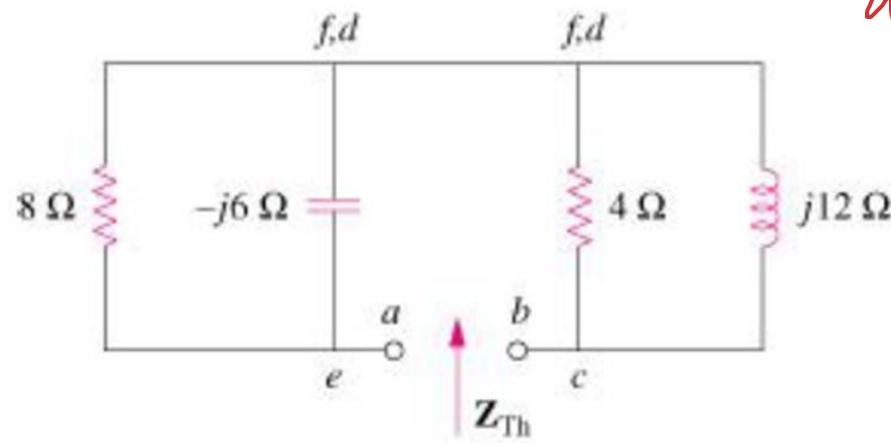


Ex. 21:

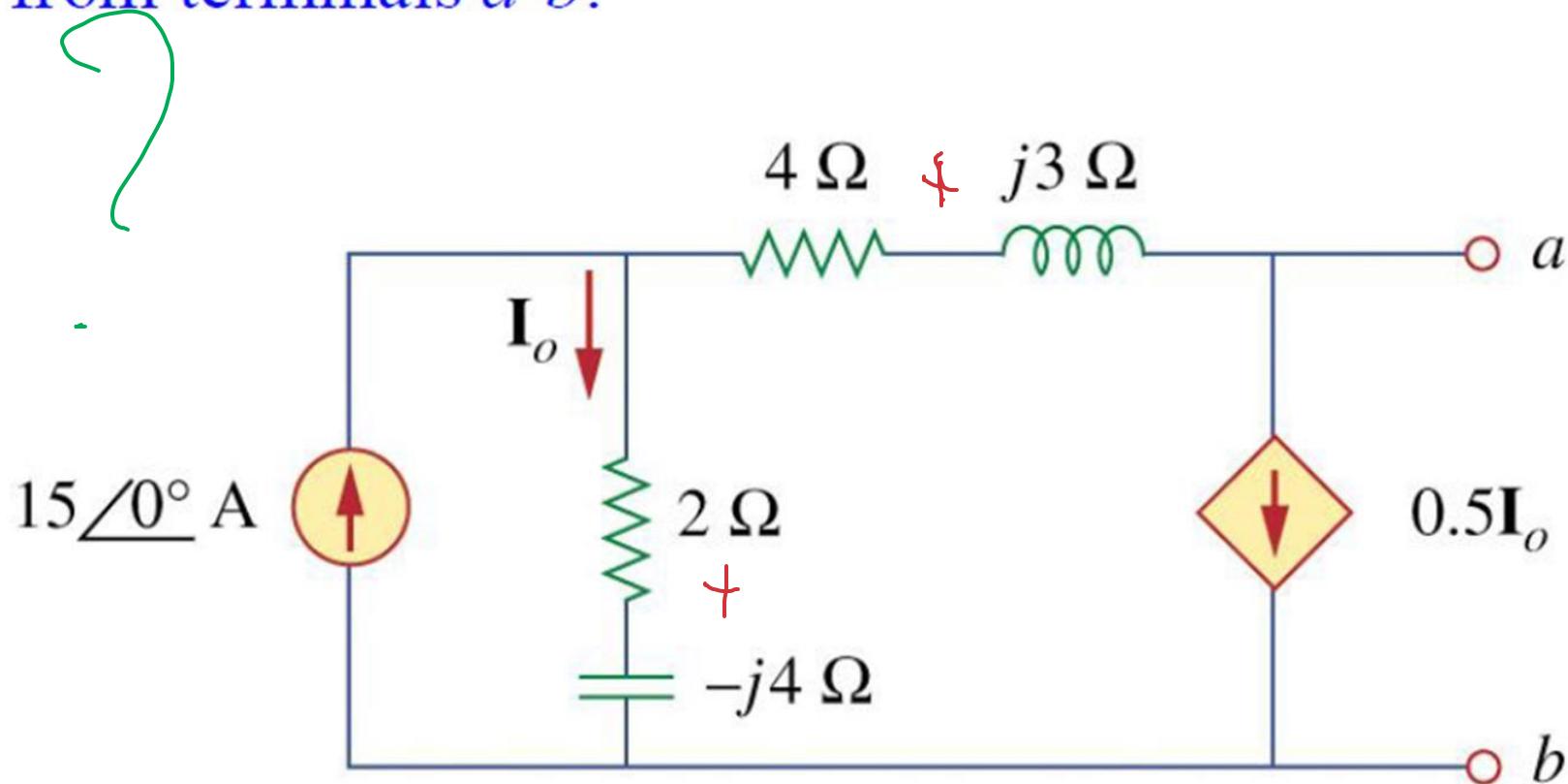
Find the Thevenin equivalent of the circuit as seen from terminals $a-b$.



Sol. of Ex. 21:

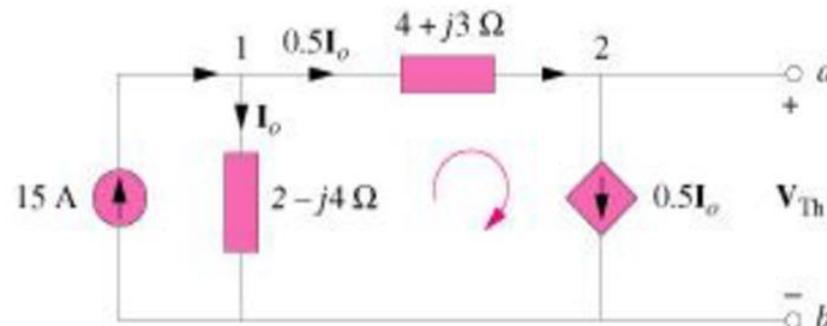

(a)

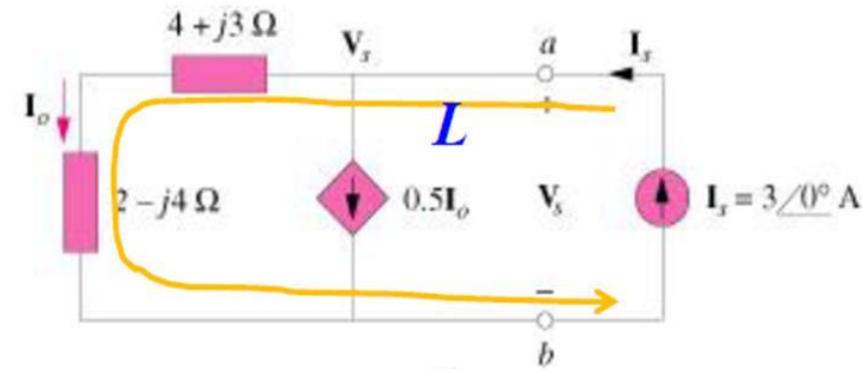

(b)

KCL at node 1:

$$15 = I_o + 0.5I_o \Rightarrow I_o = 10$$

KVL for loop:

$$-I_o(2 - j4) + 0.5I_o(4 + j3) + V_{Th} = 0$$

$$\Rightarrow V_{Th} = 10(2 - j4) - 5(4 + j3)$$

$$= -j55$$

$$= 55\angle -90^\circ V$$

$$\left. \begin{array}{l} 0.5I_o \\ \downarrow \end{array} \right\}$$

Set $I_s = 3$ for simplicity,

KCL at node a:

$$I_s = 3 = I_o + 0.5I_o \Rightarrow I_o = 2$$

KVL for loop L:


$$V_s = I_o(4 + j3 + 2 - j4) = 2(6 - j)$$

$$\Rightarrow Z_{Th} = \frac{V_s}{I_s} = \frac{2(6 - j)}{3}$$


Ex. 22:

Obtain current \mathbf{I}_o using Norton's theorem.

?

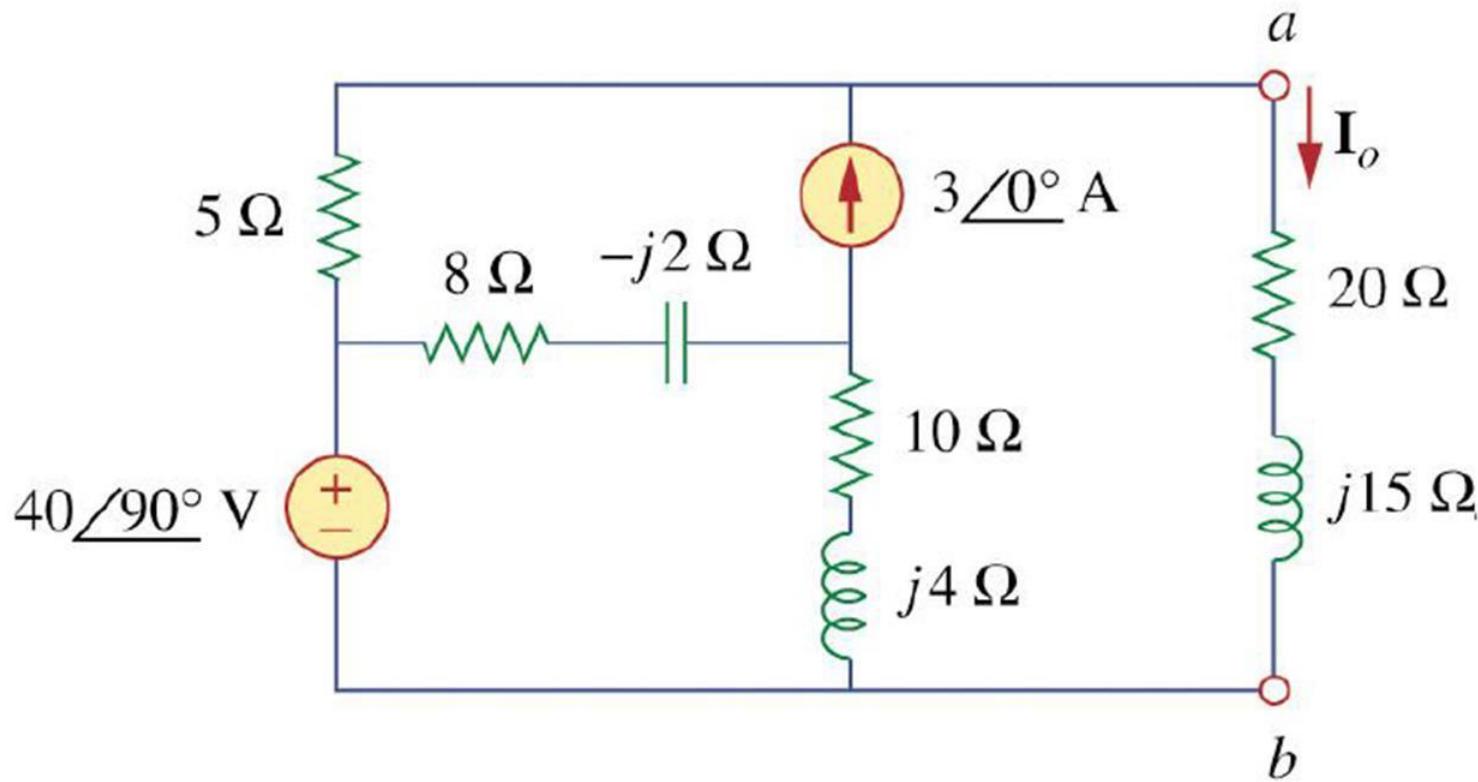

Sol. of Ex. 22:

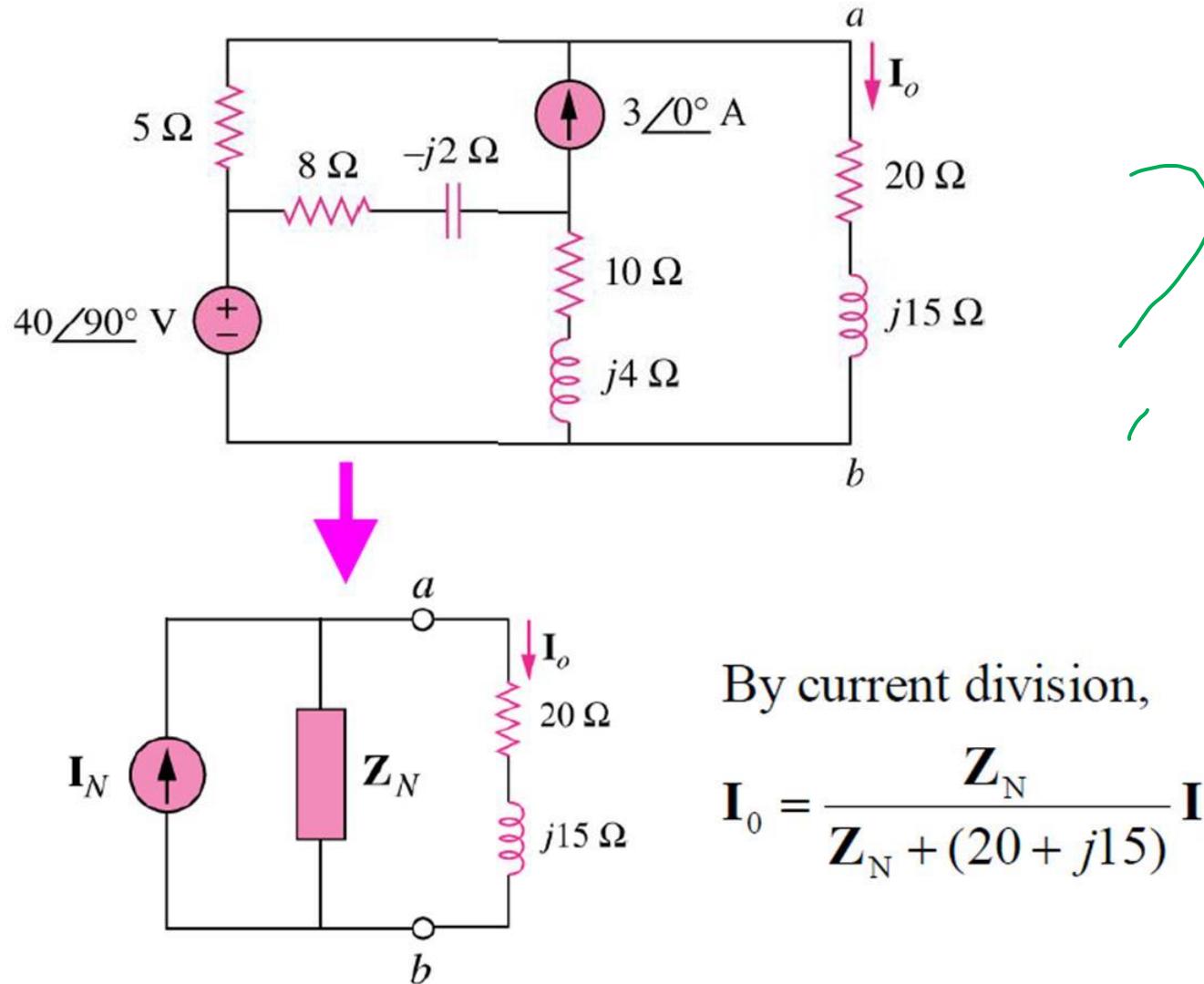

By current division,

$$I_0 = \frac{Z_N}{Z_N + (20 + j15)} I_N$$

Sol. of Ex. 22: cont.

(1) Z_N can be found easily, $Z_N = 5$

(2) Apply mesh analysis to get \mathbf{I}_N .

KVL for mesh 1:

$$-j40 + (18 + j2)\mathbf{I}_1 - (8 - j2)\mathbf{I}_2 - (10 + j4)\mathbf{I}_3 = 0 \cdots (a)$$

KVL for the supermesh:

$$(13 - j2)\mathbf{I}_2 + (10 + j4)\mathbf{I}_3 - (18 + j2)\mathbf{I}_1 = 0 \cdots (b)$$




KCL at node a :

$$\mathbf{I}_3 = \mathbf{I}_2 + 3 \cdots (c)$$

(a) ~ (c) give

$$\mathbf{I}_N = \mathbf{I}_3 = 3 + j8$$

$$\Rightarrow \mathbf{I}_0 = \frac{5}{5 + 20 + j15} \mathbf{I}_N = 1.465 \angle 38.48^\circ \text{ A}$$

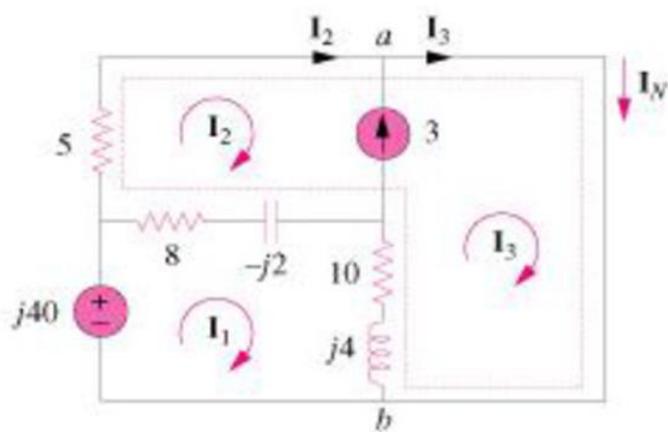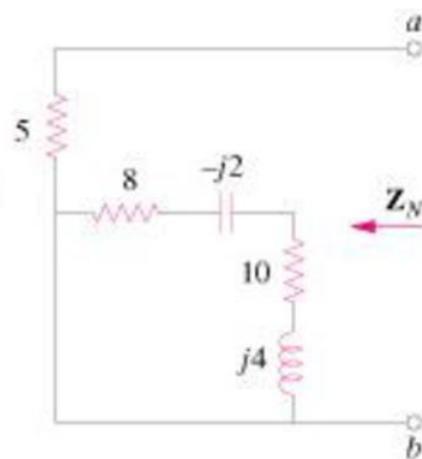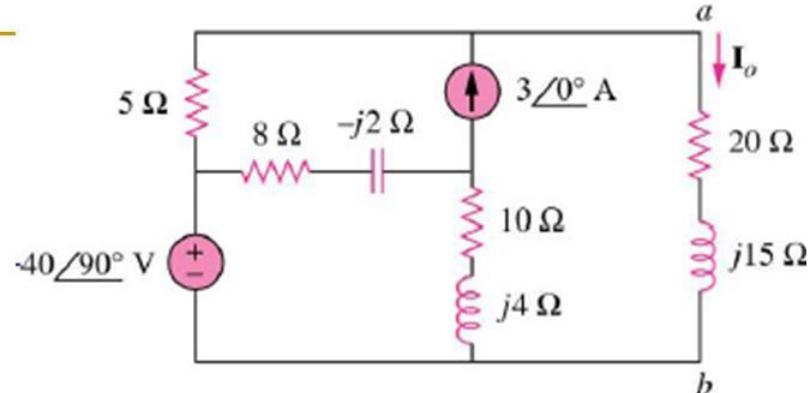

Ex. 23


A 90 Ω resistor, a 32 mH inductor, and a 5 μF capacitor are connected in series across the terminals of a sinusoidal voltage source, as shown in the Fig.



The steady-state expression for the source voltage


$$v_s = 750\cos(5000t + 30^\circ) \text{ V.}$$

- Construct the frequency-domain equivalent circuit.
- Calculate the steady-state current i by the phasor method.

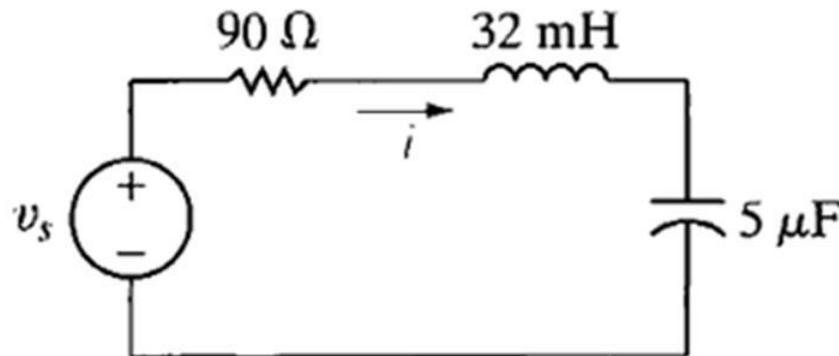

Ex. 23: Sol.


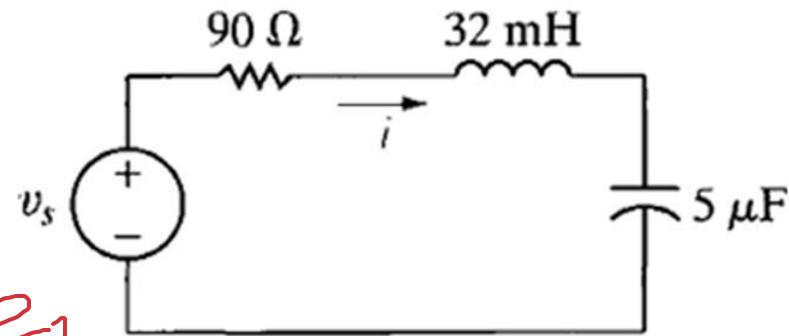
a) From the expression for v_s , we have $\omega = 5000$ rad/s. Therefore the impedance of the 32 mH inductor is $Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \Omega$, $\underline{Z_L}$



and the impedance of the capacitor is $Z_C = j \frac{-1}{\omega C} = -j \frac{10^6}{(5000)(5)} = -j40 \Omega$. $\underline{Z_C}$

The phasor transform of v_s is

$$\underline{V_s} = 750 / 30^\circ \text{ V.}$$

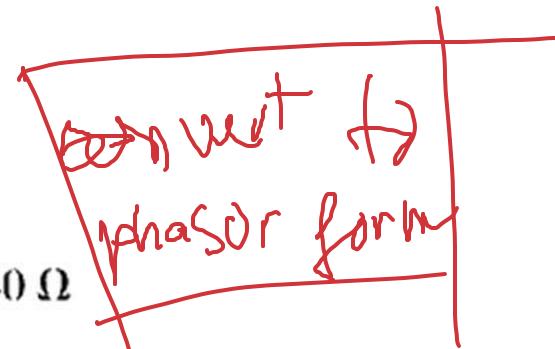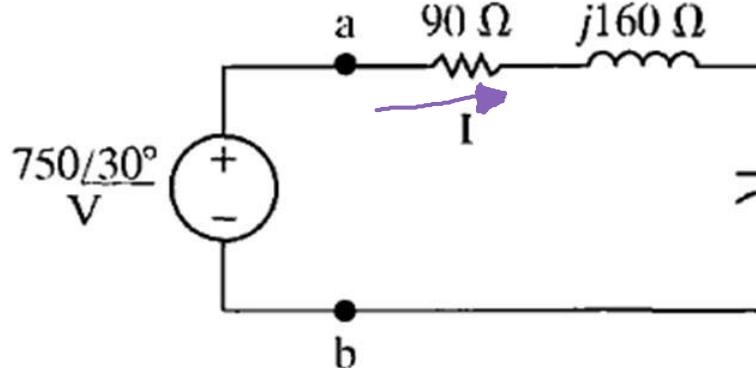

Ex. 23: Sol.

b) We compute the phasor current simply by dividing the voltage of the voltage source by the equivalent impedance between the terminals a, b.

$$\begin{aligned} Z_{ab} &= 90 + j160 - j40 \\ &= 90 + j120 = 150 \angle 53.13^\circ \Omega. \end{aligned}$$


$$\rightarrow I = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A.}$$

Thus, the steady-state expression for i directly:

$$i = 5 \cos(5000t - 23.13^\circ) \text{ A.}$$


Phasor Diagrams

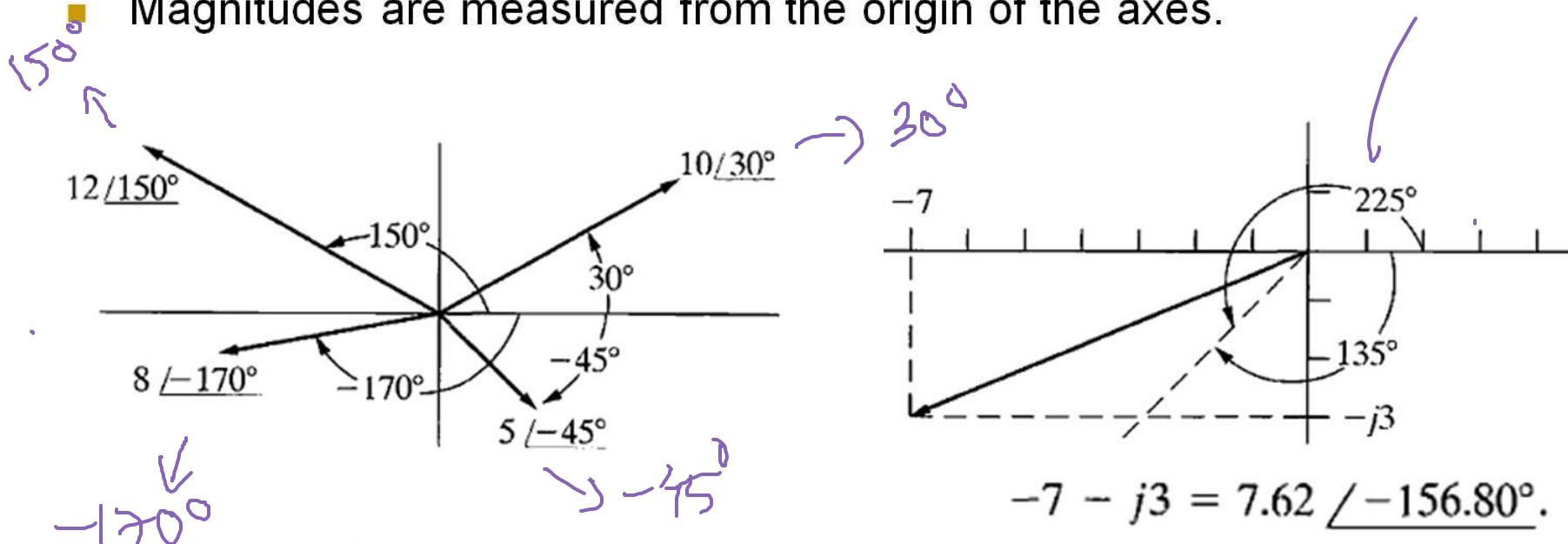- A phasor diagram shows the magnitude and phase angle of each phasor quantity in the complex-number plane.
- Phase angles are measured counterclockwise from the positive real axis.
- Magnitudes are measured from the origin of the axes.



Phasor diagram is useful for checking calculator calculations

Phasor Diagrams – An example

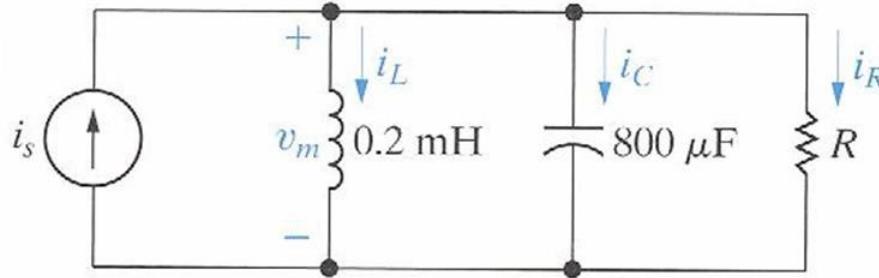

Use a phasor diagram to find the value of R that will cause the current through that resistor, i_R , to lag the source current, i_s , by 45° when $\omega = 5 \text{ krad/s}$


$$I_s = I_L + I_C + I_R$$

$$\text{Assume } V_m = V_m \angle 0^\circ$$

$$I_L = \frac{V_m \angle 0^\circ}{j(5000)(0.2 \times 10^{-3})} = V_m \angle -90^\circ$$

$$I_C = \frac{V_m \angle 0^\circ}{-j/(5000)(800 \times 10^{-6})} = 4V_m \angle 90^\circ$$
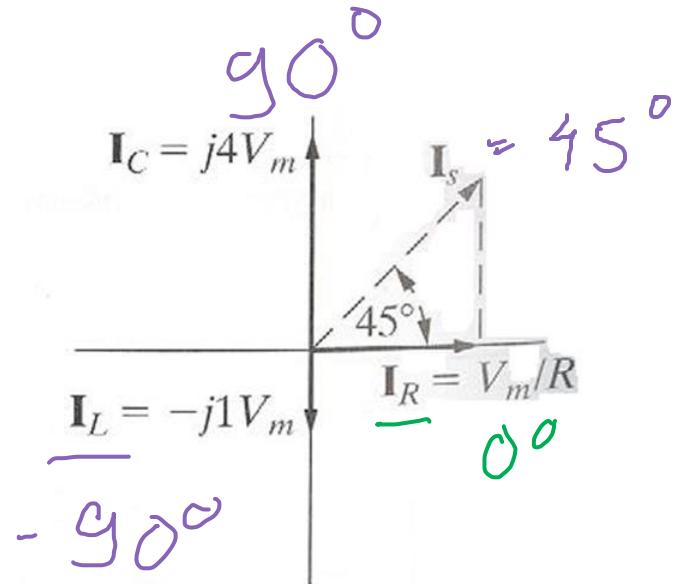
$$I_R = \frac{V_m \angle 0^\circ}{R} = \frac{V_m}{R} \angle 0^\circ$$



From phasor diagram, we have
 $R = 1/3 \Omega$

$$\omega = 5000 \text{ rad/s}$$

$$i_s = 45^\circ$$

Example

